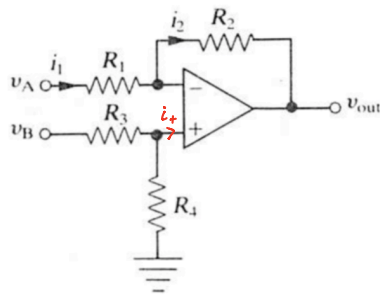


Phys 2610 (2019) Assignment 5 solutions

1. Find a general expression for the output of the following circuit, and show that it reduces to

$$v_{out} = \frac{R_2}{R_1} (v_B - v_A) \text{ when } \frac{R_1}{R_2} = \frac{R_3}{R_4}.$$



Since current entering the op amp is zero, $i_1 = i_2$, so $\frac{v_A - v_-}{R_1} = \frac{v_- - v_{out}}{R_2}$

$$\text{Solving for } v_-: v_- \left(\frac{1}{R_2} + \frac{1}{R_1} \right) = \frac{v_A}{R_1} + \frac{v_{out}}{R_2} \Rightarrow v_- = \left(\frac{v_A}{R_1} + \frac{v_{out}}{R_2} \right) \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

or

$$v_- = \frac{v_A R_2 + v_{out} R_1}{R_1 + R_2}$$

$$\text{Also, since } i_+ = 0, \quad v_+ = v_B \frac{R_4}{R_3 + R_4}$$

Setting the inputs equal, and solving for v_{out} :


$$v_{out} = \left[v_B \left(\frac{R_4}{R_3 + R_4} \right) - v_A \left(\frac{R_2}{R_1 + R_2} \right) \right] \left(\frac{R_1 + R_2}{R_1} \right)$$

$$\text{If } \frac{R_1}{R_2} = \frac{R_3}{R_4}, \text{ then } \frac{R_4}{R_3 + R_4} = \frac{1}{R_3/R_4 + 1} = \frac{1}{R_1/R_2 + 1} = \frac{R_2}{R_1 + R_2}$$

$$v_{out} = (v_B - v_A) \frac{R_2}{R_1}$$

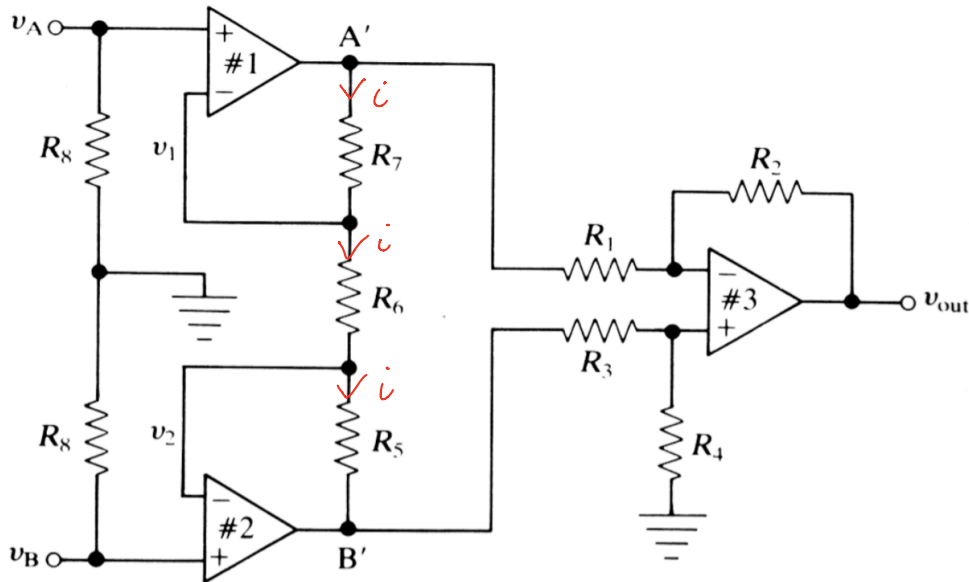2. Show that the gain for the following circuit, with $R_5 = R_7 = R$, and $\frac{R_1}{R_2} = \frac{R_3}{R_4}$ is given by

$$a = \frac{v_{out}}{v_A - v_B} = -\frac{R_2}{R_1} \left(1 + \frac{2R}{R_6} \right)$$



The current through R_6 is determined from $v_{A'}$ and $v_{B'}$ because $i_+ = i_-$.

$$i = \frac{v_{A'} - v_{B'}}{R_6}$$

The same current flows in $R_5 + R_7$ because the current into the op amp is negligible.

$$\therefore i = \frac{v_{A'} - v_{B'}}{R_5 + R_6 + R_7} = \frac{v_{A'} - v_{B'}}{R_6} \Rightarrow v_{A'} - v_{B'} = (v_A - v_B) \left(\frac{R_5 + R_6 + R_7}{R_6} \right)$$


Using $R_5 = R_7 = R$, gives
$$v_{A'} - v_{B'} = (v_A - v_B) \left(1 + \frac{2R}{R_6} \right)$$

We have, from problem 1, $v_{out} = (v_{B'} - v_{A'}) \frac{R_2}{R_1}$ if $\frac{R_2}{R_1} = \frac{R_3}{R_4}$, so

$$= - \left(1 + \frac{2R}{R_6} \right) \frac{R_2}{R_1} (v_A - v_B)$$

$$a = \frac{v_{out}}{v_A - v_B} = - \left(1 + \frac{2R}{R_6} \right) \frac{R_2}{R_1}$$

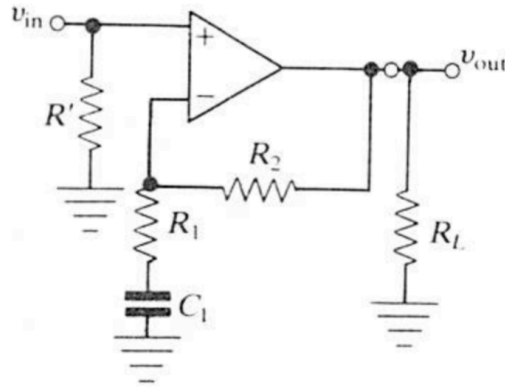3. Find an expression for the complex gain of the following circuit, when $\omega = \omega_1 = 1/(R_1 C_1)$.



Using $v_+ = v_-$, $v_{in} = v_{out} \left(\frac{R_1 + 1/j\omega C_1}{R_2 + R_1 + 1/j\omega C_1} \right)$


Then, for $\omega = 1/R_1 C_1$,

$$a = \frac{v_{out}}{v_{in}} = \frac{R_1 + R_2 + R_1/j}{R_1 + R_1/j} = 1 + \frac{R_2}{R_1} \left(\frac{j}{1+j} \right)$$

$$\text{or } a = 1 + \frac{R_2}{2R_1} (1+j)$$

$$\text{or } a = \left(1 + \frac{R_2}{2R_1} \right) + j \left(\frac{R_2}{2R_1} \right)$$

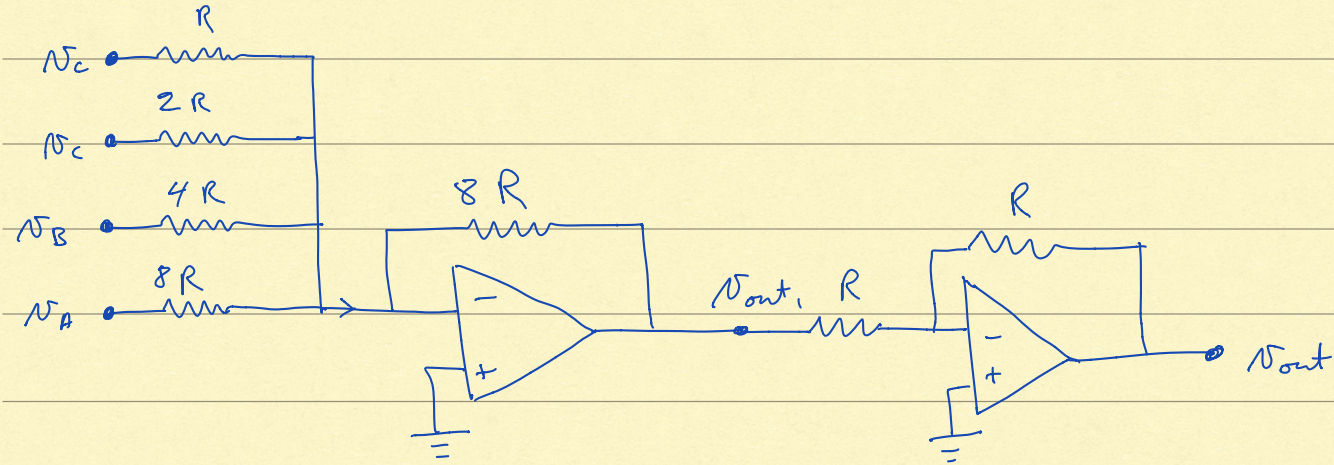4. Design a summing amplifier to sum from inputs v_A, v_B, v_C, v_D and to produce an output of $v_{out} = v_A + 2v_B + 4v_C + 8v_D$.




$$i = \frac{v_A}{8R} + \frac{v_B}{4R} + \frac{v_C}{2R} + \frac{v_D}{R} = -\frac{v_{out,1}}{8R}$$


$$\Rightarrow v_{out,1} = -(v_A + 2v_B + 4v_C + 8v_D)$$

$$\Rightarrow v_{out} = v_A + 2v_B + 4v_C + 8v_D \quad (\text{not req'd for full credit})$$

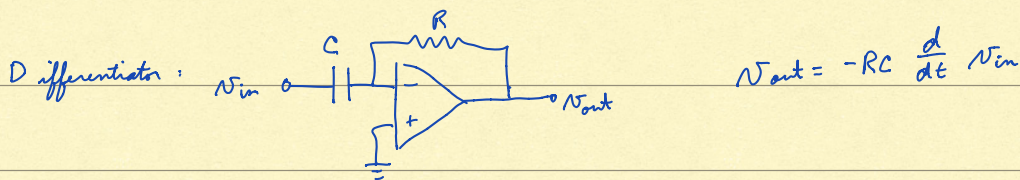5. Design an op amp differentiator with an output given by $v_{out} = -(10^{-6}\text{s}) \frac{d}{dt} v_{in}$. If an input step function rises from 0 to 1 V in $2\mu\text{s}$ and then is constant at 1V, sketch the output.



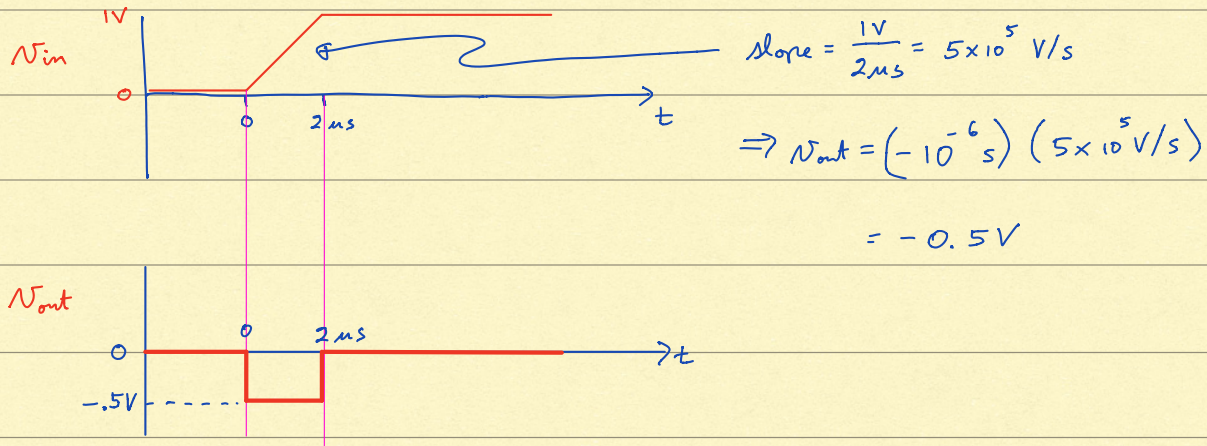
For $RC = 10^{-6}\text{s}$, take $R = 1\text{k}\Omega$ and $C = \frac{10^{-6}\text{s}}{1\text{k}\Omega} = 1\text{mF}$



The output is proportional to the slope, which is zero before $t=0$ and after $t=2\mu\text{s}$.

During the increase, the slope is $5 \times 10^5 \text{ V/s}$, so the output is -0.5V .

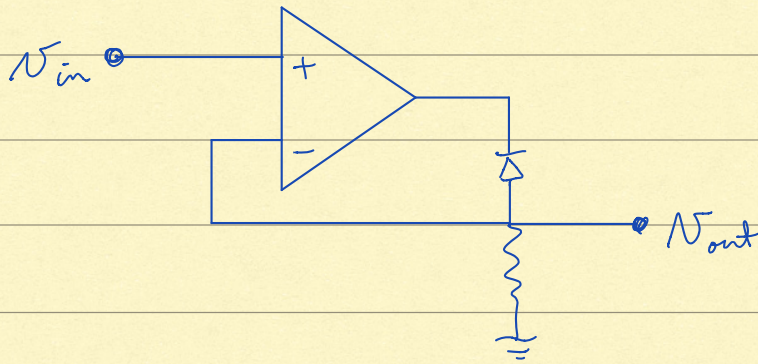6. Design an ideal diode op amp circuit to produce a negative half-waveform from a sinusoidal input.



For $V_{in} > 0$, diode is off $\Rightarrow V_{out} = 0$

For $V_{in} < 0$, diode is on \Rightarrow neg. feedback $\Rightarrow V_{out} = V_{in}$

