

March 4, 2019

MIDTERM EXAM

PAGE NO.: 1

DEPARTMENT &amp; COURSE NO.: PHYS 2610


TIME: 1.5 hours

EXAMINATION: Circuit Theory and Introductory Electronics


EXAMINER: W Ens

*All questions have equal value.*

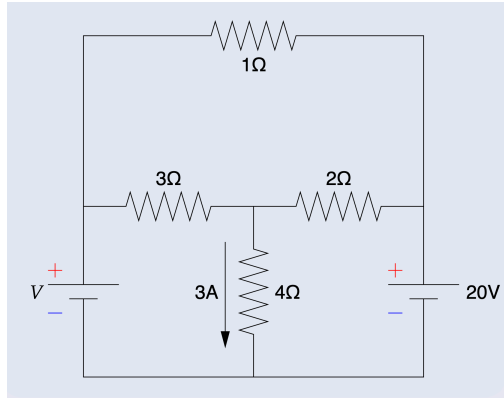
1. For the circuit shown below, with the current through the  $4\ \Omega$  resistor equal to  $3\ \text{A}$  (as indicated), find (a) the current through each of the other resistors, (b) the voltage of the battery on the left, and (c) the power delivered by the  $20\ \text{V}$  battery.



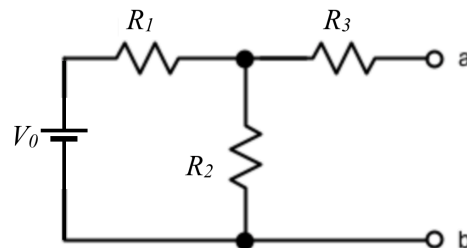2. Using  $R_1 = 60\ \Omega$ ,  $R_2 = 150\ \Omega$ ,  $R_3 = 90\ \Omega$ , and  $V_0 = 10\ \text{V}$ , for the circuit shown below, find the values for Thevenin and Norton equivalent circuits with respect to the terminals a and b. What load resistance connected to the output terminals would give the largest power transfer?



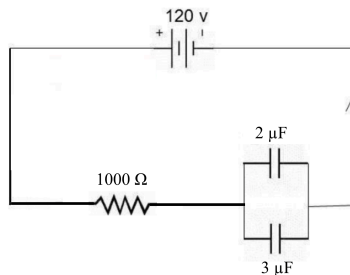3. For the RC circuit below, determine the current delivered by the battery  $2\ \text{ms}$  after the switch closes. Find the charge on each of the capacitors after equilibrium is reached with the switch closed.



March 4, 2019

MIDTERM EXAM

PAGE NO.: 2


DEPARTMENT & COURSE NO.: PHYS 2610

TIME: 1.5 hours


EXAMINATION: Circuit Theory and Introductory Electronics

EXAMINER: W Ens

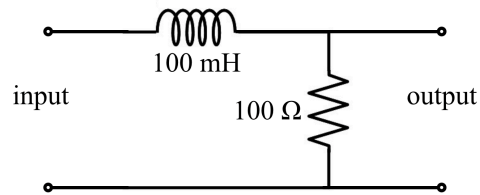4. For the RL circuit below, sketch the output waveform for each of the two input waveforms shown.



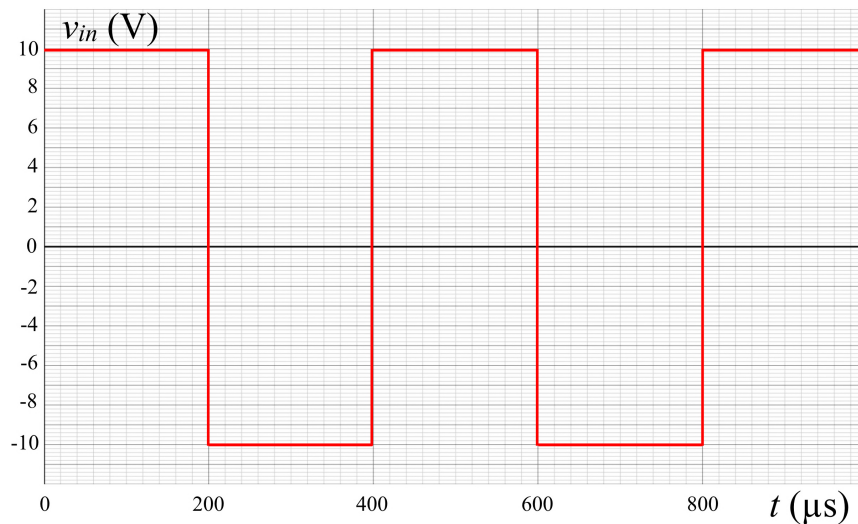(a) A square wave with an amplitude of 10 V and a period of 400  $\mu\text{s}$ .



(b) A sine wave with an amplitude of 10 V and an angular frequency of 1000 rad/s:

$$v_{in} = 10V \sin(1000 s^{-1}t)$$



Make your sketches to scale directly on the diagrams above, and don't forget to hand in this question sheet.

March 4, 2019

MIDTERM EXAM

PAGE NO.: 3

DEPARTMENT &amp; COURSE NO.: PHYS 2610


TIME: 1.5 hours

EXAMINATION: Circuit Theory and Introductory Electronics

EXAMINER: W Ens

---

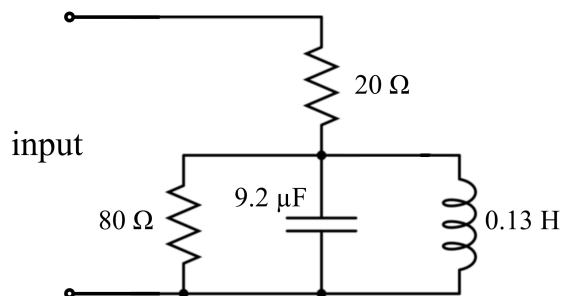
5. Find the magnitude and phase of the impedance across the input for the circuit below. If a sinusoidal input is connected with 160 V amplitude and 250 Hz frequency, find the voltage signal across the 20- $\Omega$  resistor, including the phase with respect to the input.



6. A 10- $\Omega$  resistor, 10-mH inductor, and 10- $\mu\text{F}$  capacitor are connected in series with a 10-kHz sinusoidal voltage source. The rms current through the circuit is 0.20 A. Find the rms voltage drop across each of the 3 elements. What would the rms current be at resonance, if the input rms voltage were the same?

# Phys 2610 (2019) Midterm solutions

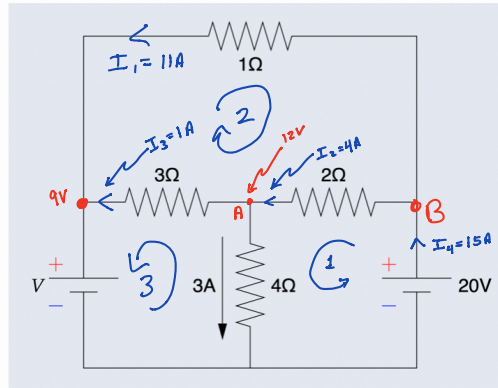1. For the circuit shown below, with the current through the  $4\ \Omega$  resistor equal to  $3\ \text{A}$  (as indicated), find (a) the current through each of the other resistors, (b) the voltage of the battery on the left, and (c) the power delivered by the  $20\ \text{V}$  battery.



(a)

$$\text{Loop 1: } 20\text{V} - I_2(2\ \Omega) - (3\text{A})(4\ \Omega) = 0 \Rightarrow I_2 = \frac{20\text{V} - 12\text{V}}{2\ \Omega} \Rightarrow \boxed{I_2 = 4\text{A}}$$

$$\text{Jctn A: } I_2 = I_3 + 3\text{A} \Rightarrow I_3 = I_2 - 3\text{A} = 1\text{A} \Rightarrow \boxed{I_3 = 1\text{A}}$$

$$\text{Loop 2: } -I_3(3\ \Omega) + I_1(1\ \Omega) - I_2(2\ \Omega) = 0 \Rightarrow I_1 = \frac{I_3(3\ \Omega) + I_2(2\ \Omega)}{1\ \Omega} = \frac{3\text{V} + 8\text{V}}{1\ \Omega} = 11\text{A}$$

$$\Rightarrow \boxed{I_1 = 11\text{A}}$$

(b)

$$\text{Loop 3: } (3\text{A})(4\ \Omega) - I_3(3\ \Omega) - V = 0 \Rightarrow V = 12\text{V} - (1\text{A})(3\ \Omega) = 12\text{V} - 3\text{V} = 9\text{V}$$


$$\Rightarrow \boxed{V = 9\text{V}}$$

(c)


$$\text{Jctn B: } I_4 = I_2 + I_1 = 15\text{A} \rightarrow P = VI = (20\text{V})(15\text{A}) \Rightarrow \boxed{P = 300\text{W}}$$



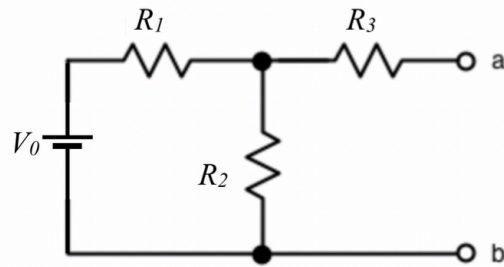2. Using  $R_1 = 60 \Omega$ ,  $R_2 = 150 \Omega$ ,  $R_3 = 90 \Omega$ , and  $V_0 = 10 \text{ V}$ , for the circuit shown below, find the values for Thevenin and Norton equivalent circuits with respect to the terminals a and b. What load resistance connected to the output terminals would give the largest power transfer?




Thevenin:  $V_{th} = \text{open ckt voltage} = V_0 \frac{R_2}{R_1 + R_2} = (10\text{V}) \left( \frac{150}{150 + 60} \right) = 7.14\text{V}$

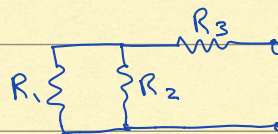$R_{th} = \text{resistance with } V_0 \text{ shorted.}$  

$= R_3 + R_1 // R_2 = 90\Omega + 150\Omega // 60\Omega$

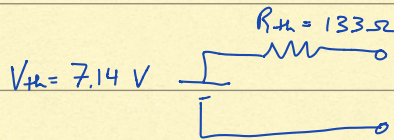
$= 90\Omega + \frac{(150)(60)}{(150 + 60)}\Omega = 133\Omega$   $R_{th} = 133\Omega$



Norton:  $R_N = R_{th} = 133\Omega$

$I_N = \text{closed ckt current} = \frac{V_{th}}{R_{th}} = \frac{7.14}{133} \text{ A} = 53.7 \text{ mA}$

$I_N = 53.7 \text{ mA}$

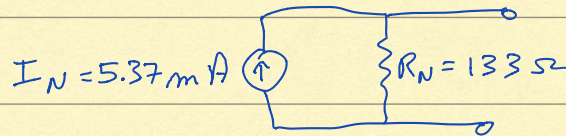

Max power transfer:  $R_L = R_{th} = 133\Omega$




3. For the RC circuit below, determine the current delivered by the battery 2 ms after the switch closes. Find the charge on each of the capacitors after equilibrium is reached with the switch closed.

$$V - iR - q/c = 0 \Rightarrow \frac{di}{dt}R + \frac{i}{C} = 0$$

$$\Rightarrow \frac{di}{dt} + \frac{i}{R} = 0 \Rightarrow i = Ae^{-t/RC}$$

$$\text{Fn } t=0, i = \frac{V}{R} \Rightarrow A = \frac{V}{R} \Rightarrow i = \frac{V}{R} e^{-t/RC}$$
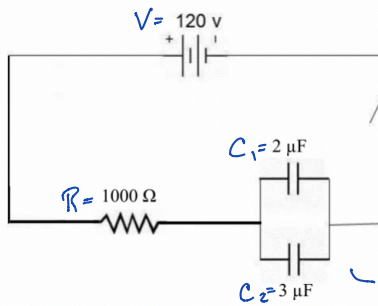
$$\text{or } i = 120 \text{ mA } e^{-t/5 \text{ ms}}$$



$$C = 2 \mu\text{F} + 3 \mu\text{F} = 5 \mu\text{F}$$

or by inspection  $i = \frac{V}{R} e^{-t/\tau}$ , where  $\tau = RC = 1000 \Omega \cdot 5 \mu\text{F} = 5 \text{ ms}$

$$\text{At } t = 2 \text{ ms}, i = \frac{V}{R} e^{-2/5} = 120 \text{ mA } e^{-2/5} = 80.4 \text{ mA}$$


$$\text{At } t \rightarrow \infty, i \rightarrow 0. \therefore V_C = V_{C1} = V_{C2} = V = 120 \text{ V}$$

$$\Rightarrow q_1 = V_{C1} C_1 = 120 \text{ V } (2 \mu\text{F}) = 240 \mu\text{C}$$


$$q_2 = V_{C2} C_2 = 120 \text{ V } (3 \mu\text{F}) = 360 \mu\text{C}$$



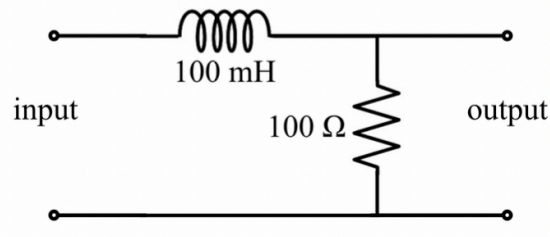4. For the RL circuit below, sketch the output waveform for each of the two input waveforms shown.



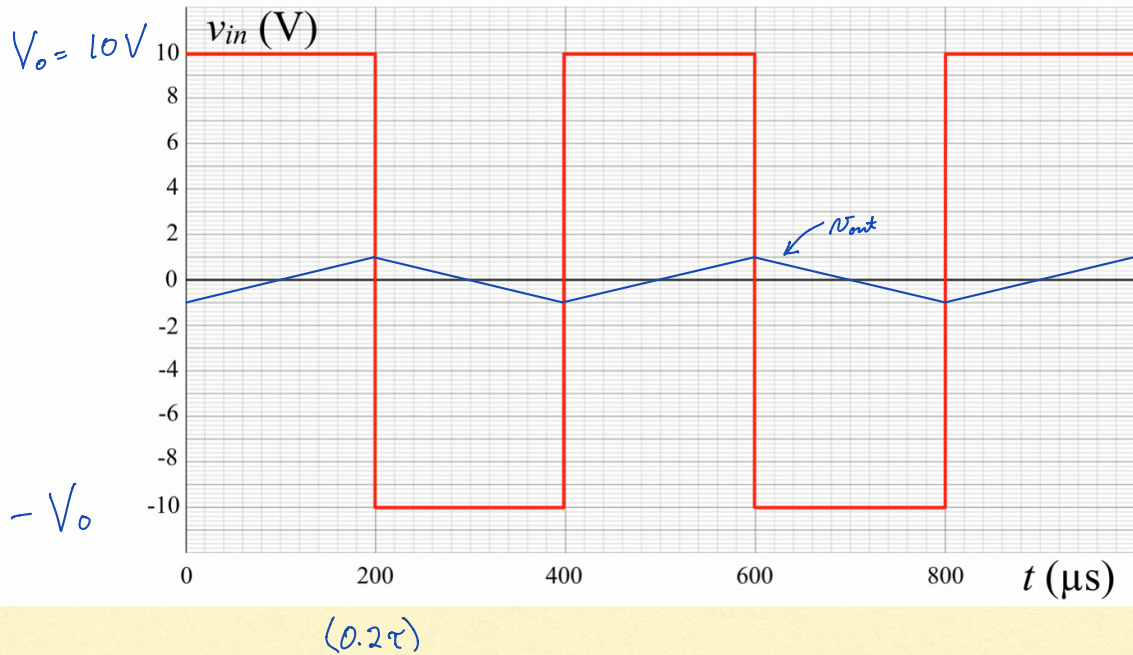(a) A square wave with an amplitude of 10 V and a period of 400  $\mu\text{s}$ .



For a step voltage from zero to  $\pm V_o$ , as  $t \rightarrow \infty$ ,  $v_{out} \rightarrow \pm V_o$  :

$$v_{out} = \pm V_o (1 - e^{-t/\tau}) \quad \text{with } \tau = L/R \quad [1]$$

Here  $\tau = \frac{L}{R} = 1\text{ms}$ , so  $t_{max} = 200\mu\text{s} \ll \tau$ .

For  $t \ll \tau$ ,  $|v_{out}| \ll V_o$  (so the step is always from near zero to  $\pm V_o$ )

$$\text{Then } v_{out} \cong \pm V_o (1 - (1 - t/\tau)) = \pm V_o t/\tau \quad [2]$$

This is a straight line with slope  $\pm V_o/\tau = \frac{\pm 10\text{V}}{1\text{ms}} = \frac{\pm 2\text{V}}{200\mu\text{s}}$

After many cycles  $v_{out}$  is symmetric about zero, so the result is a triangular

wave for  $-1\text{V} \rightarrow +1\text{V} \rightarrow -1\text{V} \dots$  [3]



## Notes for Question 4b

[1] This result can be obtained by inspection, or from

$$\pm V_0 - L \frac{di}{dt} - iR = 0 \rightarrow \frac{di}{dt} + \frac{iR}{L} = \pm \frac{V_0}{L} \rightarrow i = A_1 e^{-t/\tau} \pm \frac{V_0}{R}$$
$$\rightarrow v_{out} = iR = A e^{-t/\tau} \pm V_0 *$$

If  $v_{out} = 0$  at  $t = 0$ ,  $0 = A \pm V_0 \rightarrow A = \mp V_0$  so  $v_{out} = \pm V_0 (1 - e^{-t/\tau})$

Since  $v_{out}$  is not exactly zero when the input steps to  $\pm V_0$  (at  $t = 0$ ), better boundary conditions on  $*$  are:

For a symmetric output,  $v_{out}(t=0) = -v_{out}(t=0.2\tau)$

$$\rightarrow A \pm V_0 = -(0.82 A \pm V_0)$$

$$\rightarrow A(1+0.82) = \mp 2V_0 \rightarrow A = \mp 1.1V_0$$

Then  $v_{out} = \pm V_0 (1 - 1.1 e^{-t/\tau})$

and  $v_{out}(t=0) = -v_{out}(t=0.2\tau) = \pm V_0 (1 - 1.1) = \pm V_0 (-0.1) = \mp 0.1V$

again giving triangular wave:  $-0.1V \rightarrow +0.1V \rightarrow -0.1V \dots$

[2] This result is also obtained by recognizing that the circuit integrates

if  $v_{out} \ll v_{in}$ :  $v_{in} - L \frac{di}{dt} = v_{out} \Rightarrow i = \frac{1}{L} \int (v_{in} - v_{out}) dt \cong \frac{1}{L} \int v_{in} dt$   
(for  $v_{out} \ll v_{in}$ )

$$\Rightarrow v_{out} = iR \cong \frac{R}{L} \int v_{in} dt = \frac{1}{\tau} \int \pm V_0 dt = \frac{1}{\tau} (\pm V_0 t + \text{const.})$$

$$= \pm V_0 \left(\frac{t}{\tau}\right) + \text{const.} \quad (\text{Here, to give a symmetric result, const.} = -1V)$$



[3] If a symmetric output is not assumed, and  $v_{out}(t=0) = 0$  is taken for first half-cycle, then  $v_{out} = V_0(1 - e^{-t/\tau})$  applies and  $v_{out}(t=200\mu s) = 2V$ .

For the second half-cycle,  $v_{out}(t=0) = 2V$ , so  $*$  becomes

$$2V = A - V_0 \Rightarrow A = 12V \text{ so } v_{out} = 12V e^{-t/\tau} - V_0$$

$$\text{At } t = 200\mu s, v_{out}(200\mu s) = 12V e^{-.2} - 10V = -0.18V$$

For the third half-cycle,  $v_{out}(t=0) = -0.18V$ , so  $*$  becomes


$$-0.18V = A + V_0 \Rightarrow A = -10.18V \Rightarrow v_{out} = -10.18V e^{-t/\tau} + V_0$$

$$\text{At } t = 200\mu s, v_{out}(200\mu s) = -10.18V e^{-.2} + 10V = 1.67V$$

For the fourth,  $v_{out}(200\mu s) = -0.45V$

fifth,  $v_{out}(200\mu s) = 1.3V$

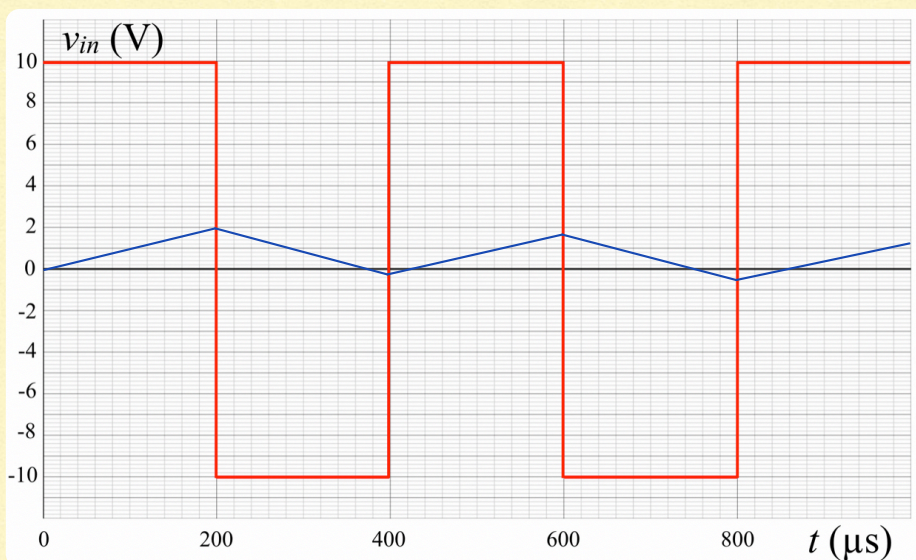
(The results converge to  $\pm 1V$  after about 20 cycles.)





(b) A sine wave with an amplitude of 10 V and an angular frequency of 1000 rad/s:

$$v_{in} = 10V \sin(1000 s^{-1}t)$$

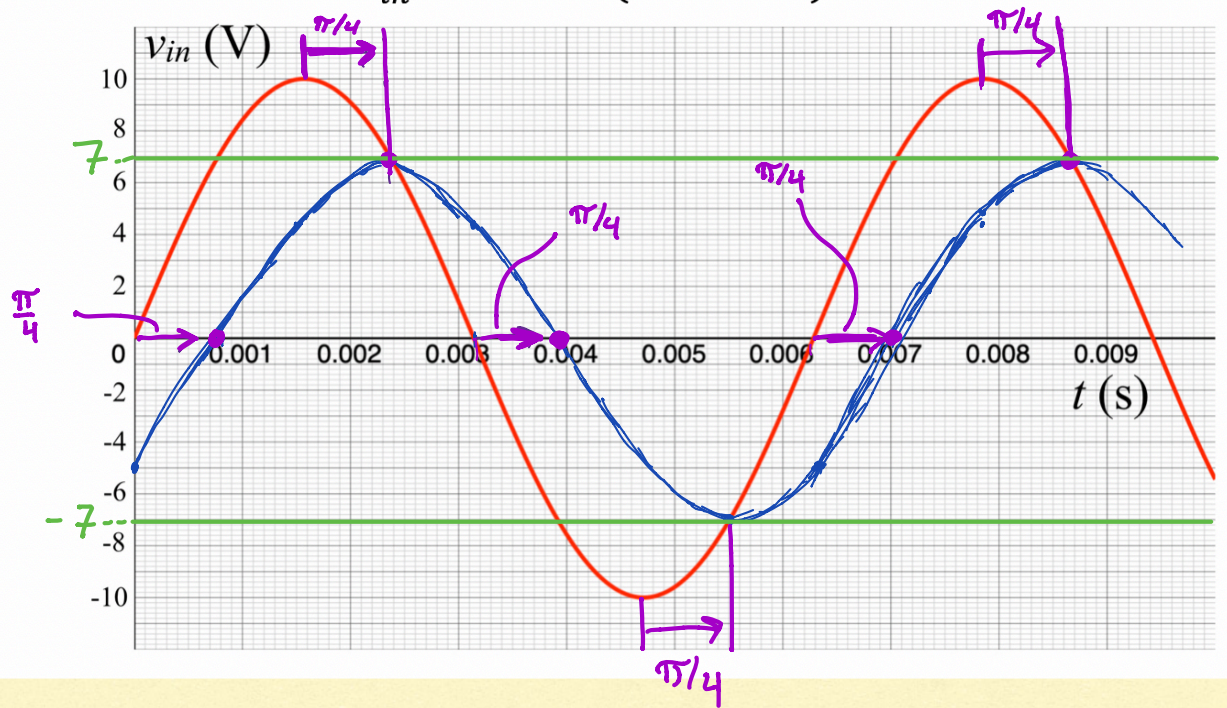

Here  $\omega = 1000 \text{ rad/s} = \frac{1}{\tau} = \frac{R}{L} = \omega_B \rightarrow 3\text{dB attenuation, phase shift} = -\pi/4$

$$\rightarrow v_{out} = \frac{V_{in}}{\sqrt{2}} \sin(\omega t - \pi/4) = (7V) \sin((1000s^{-1})t - \pi/4) \quad [1]$$

Neg. phase shift corresponds to a shift to the right.  $\therefore$  peaks + zero crossings

shift  $\pi/4$  to the right  $\rightarrow \Delta t \cong .0008 \text{ s}$  (Note:  $f_n t = 0, v_o = 7V \sin(-\pi/4) = -5V$ )

[1] For sinusoidal input  $v_{in}$ :

$$v_{out} = iR = \frac{v_{in}}{Z} R \quad \text{with } Z = R + j\omega L = \sqrt{R^2 + (\omega L)^2} e^{j\theta} \quad \text{and } \tan\theta = \frac{\omega L}{R}$$


$$\rightarrow v_{out} = \frac{v_{in} R}{\sqrt{R^2 + (\omega L)^2}} e^{j\theta} = \frac{v_{in}}{\sqrt{R^2 + (\omega L)^2}} e^{-j\theta} \quad (\text{phase shift is } -\theta)$$

$$\text{For } \omega = 1000 \text{ rad/s, } \frac{\omega L}{R} = \frac{(1000)(.1)}{100} = 1 \quad (\text{i.e. } \omega = \omega_B = R/L)$$

$$\text{Then } \frac{1}{\sqrt{1 + (\omega L/R)^2}} = \frac{1}{\sqrt{2}} \quad \text{and } \tan\theta = 1 \Rightarrow \theta = \pi/4 \Rightarrow \text{phase shift} = -\pi/4$$



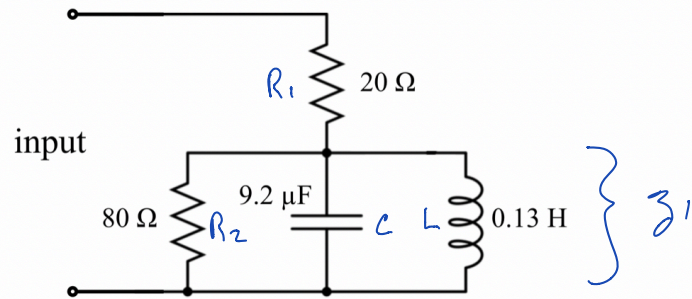5. Find the magnitude and phase of the impedance across the input for the circuit below. If a sinusoidal input is connected with 160 V amplitude and 250 Hz frequency, find the voltage signal across the 20-Ω resistor, including the phase with respect to the input.



Component impedances at 250 Hz

[1]

$$Z_C = \frac{1}{j\omega C} = -j \frac{1}{2\pi \cdot 250 \cdot (9.2 \times 10^{-6})} \Omega = -j 69.2 \Omega$$

$$Z_L = j\omega L = j(2\pi \cdot 250)(0.13) \Omega = j 204 \Omega$$

Then,

$$Z_{11} = \left( \frac{1}{R_2} + \frac{1}{Z_C} + \frac{1}{Z_L} \right)^{-1} = \left( \frac{1}{80} + \frac{1}{(-j69.2)} + \frac{1}{(j204)} \right)^{-1} \Omega = \frac{1}{\left( \frac{1}{80} + j(0.00954) \right)} \frac{1}{\left( \frac{1}{80} - j(0.00954) \right)}$$

$$= \frac{\frac{1}{80} - j(0.00954)}{\left( \frac{1}{80} \right)^2 + (0.00954)^2} \Omega = 404 \left( \frac{1}{80} - j(0.00954) \right) \Omega = 50 - j 39 \Omega$$

Total impedance:  $Z_{total} = R_1 + Z_{11} = (70 - j 39) \Omega = |Z| e^{j\theta}$

where  $|Z| = \sqrt{70^2 + 39^2} \Omega = 80 \Omega$

and  $\tan \theta = \frac{-39}{70} \Rightarrow \theta = -0.51 \text{ rad} = -29^\circ$

Voltage across 20 Ω resistor:  $V_{R_1} = i R_1$ , where  $i = \frac{V_{in}}{Z_{total}} = \frac{V_{in} e^{j\omega t}}{|Z| e^{j\theta}} = \frac{V_{in}}{|Z|} e^{j(\omega t - \theta)}$

$$\Rightarrow V_{R_1} = \frac{V_{in} R_1}{|Z|} e^{j(\omega t - \theta)} = \frac{(160)(20)}{80} V e^{j(\omega t + 0.5 \text{ rad})}$$


$$= 40 V e^{j(\omega t + 0.5 \text{ rad})}$$

$\Rightarrow$  amplitude: 40V, phase = 0.5 rad = 29°



## Note for question 5

[1] Full credit for the numerical solution, but algebraic solution is given below:
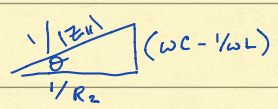
$$Z_{||} = \left( \frac{1}{R_2} + j\omega C + \frac{1}{j\omega L} \right)^{-1} = \frac{1}{\frac{1}{R_2} + j(\omega C - \frac{1}{\omega L})} = \frac{1}{\sqrt{\left(\frac{1}{R_2}\right)^2 + (\omega C - \frac{1}{\omega L})^2}} e^{j\theta} \quad \text{where } \tan \theta = R_2(\omega C - \frac{1}{\omega L})$$
$$= |Z_{||}| e^{-j\theta} \quad \text{with } |Z_{||}| = \frac{1}{\sqrt{\left(\frac{1}{R_2}\right)^2 + (\omega C - \frac{1}{\omega L})^2}}$$


Then

$$Z = R_1 + Z_{||} = \left( R_1 + |Z_{||}| \cos \theta \right) - j \left( |Z_{||}| \sin \theta \right) \quad \text{where } \cos \theta = \frac{|Z_{||}|}{R_2} + \sin \theta = |Z_{||}| (\omega C - \frac{1}{\omega L})$$
$$= \left( R_1 + \frac{|Z_{||}|^2}{R_2} \right) - j \left( |Z_{||}|^2 (\omega C - \frac{1}{\omega L}) \right)$$

or, explicitly (without simplification):

$$Z = \left[ R_1 + \frac{1}{R_2 \left( \left(\frac{1}{R_2}\right)^2 + (\omega C - \frac{1}{\omega L})^2 \right)} \right] - j \frac{(\omega C - \frac{1}{\omega L})}{\left( \left(\frac{1}{R_2}\right)^2 + (\omega C - \frac{1}{\omega L})^2 \right)}$$


Using  $R_1 = 20 \Omega$ ,  $R_2 = 80 \Omega$ ,  $C = 9.2 \mu\text{F}$ ,  $L = 0.13 \text{H}$ ,  $f = 250 \text{Hz} \rightarrow \omega = 2\pi f = 1571 \text{s}^{-1} \rightarrow (\omega C - \frac{1}{\omega L}) = 9.56 \times 10^{-3} \Omega^{-1}$

$$\rightarrow \left(\frac{1}{R}\right)^2 + (\omega C - \frac{1}{\omega L})^2 = 2.48 \times 10^{-4} \Omega^{-2}$$


$$Z = \left( 20 + \frac{1}{80(2.48 \times 10^{-4})} \right) - j \frac{9.56 \times 10^{-3}}{2.48 \times 10^{-4}} \Omega = (20 + 50) - j39 \Omega = 70 - j39 \Omega$$



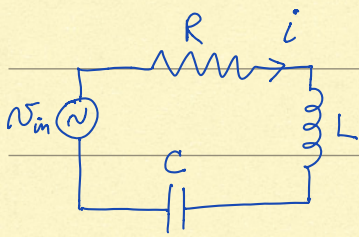6. A  $10\text{-}\Omega$  resistor,  $10\text{-mH}$  inductor, and  $10\text{-}\mu\text{F}$  capacitor are connected in series with a  $10\text{-kHz}$  sinusoidal voltage source. The rms current through the circuit is  $0.20\text{ A}$ . Find the rms voltage drop across each of the 3 elements. What would the rms current be at resonance, if the input rms voltage were the same?



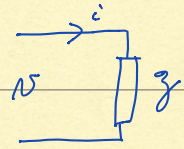Voltage across arbitrary impedance  $z$ :  $v = i z$



$$\Rightarrow V_p e^{j\omega t} = I_p e^{j(\omega t + \phi)} |Z| e^{j\theta} \Rightarrow V_p = I_p |Z| \Rightarrow V_{rms} = I_{rms} |Z|$$

Resistor:  $V_{R_{rms}} = I_{rms} R = (0.2\text{ A})(10\ \Omega) \Rightarrow V_{R_{rms}} = 2\text{ V}$

Capacitor:  $V_{C_{rms}} = I_{rms} X_C = \frac{I_{rms}}{\omega C} = \frac{0.2\text{ A}}{2\pi(10\text{ kHz})(10\ \mu\text{F})} \Rightarrow V_{C_{rms}} = 0.32\text{ V}$

Inductor:  $V_{L_{rms}} = I_{rms} X_L = I_{rms} \omega L = (0.2\text{ A})2\pi(10\text{ kHz})(10\text{ mH}) \Rightarrow V_{L_{rms}} = 126\text{ V}$

rms current at resonance (same voltage)

First, find voltage from current at  $10\text{ kHz}$ :

$V_{rms} = I_{rms} |Z|$ . At  $10\text{ kHz}$ ,  $I_{rms} = 0.2\text{ A}$ , and

$$|Z| = \sqrt{R^2 + (\omega L - 1/\omega C)^2} = \sqrt{10^2 + [2\pi \cdot 10^4(10^{-2}) - 1/(2\pi \cdot 10^4 \cdot 10^{-6})]^2} = 627\ \Omega$$

$$\Rightarrow V_{rms} = (0.2\text{ A})(627\ \Omega) = 125\text{ V}$$

Then find current at resonance

At resonance,  $\omega L - 1/\omega C = 0 \Rightarrow |Z| = R$ , so  $I_{rms} = \frac{V_{rms}}{R} = \frac{125\text{ V}}{10\ \Omega} = 12.5\text{ A}$