

March 5, 2018

MIDTERM EXAM

PAGE NO.: 1

DEPARTMENT & COURSE NO.: PHYS 2610


TIME: 3 hours

EXAMINATION: Circuit Theory and Introductory Electronics


EXAMINER: W Ens

All questions have equal value.

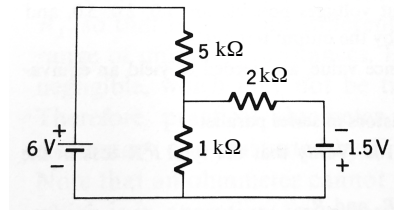
1. For the circuit shown, calculate the current through each resistor and the power delivered by the 6 V battery.



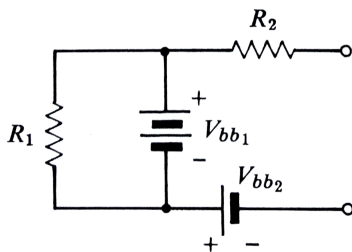2. Give the Thevenin and Norton equivalent circuits for the circuit below. What load resistance connected to the output terminals would give the largest power transfer?



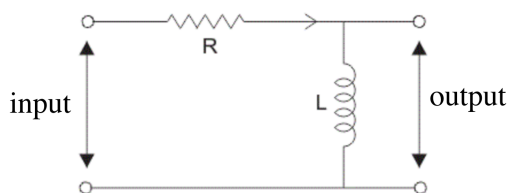3. In the RL circuit below, determine the output voltage as a function of time if the input is stepped from zero to V_o at time $t = 0$. What is the current at very long times?



4. Show that the circuit of question 3 acts as a differentiating circuit under certain conditions, and give the conditions.

March 5, 2018

MIDTERM EXAM

PAGE NO.: 2


DEPARTMENT & COURSE NO.: PHYS 2610

TIME: 3 hours

EXAMINATION: Circuit Theory and Introductory Electronics

EXAMINER: W Ens

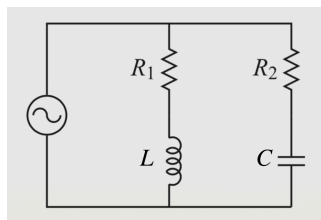5. Give an expression for the complex impedance connected to the signal generator below. If the input is given by $v = V_0 \sin(\omega t)$, give an expression for the current through R_1 .



6. Consider a series RLC circuit with $R = 10 \Omega$, $L = 100 \text{ mH}$, and $C = 10 \mu\text{F}$. What is the Q-value of the circuit? What are the two frequencies for which the voltage across the resistor drops by 3 dB from its maximum value?

PHYS 2610: Midterm Formula Sheet 2018

Current: $i = \frac{dq}{dt} = \int \mathbf{J} \cdot \overrightarrow{d\mathbf{a}}$ Steady state: $\frac{di}{dt} = 0$; $\oint \mathbf{J} \cdot \overrightarrow{d\mathbf{a}}$

Ohm's law: $\mathbf{J} = \sigma \mathbf{E} = \frac{\mathbf{E}}{\rho} \Rightarrow v = iR$ with $R = \rho \ell / A$ Current density: $\mathbf{J} = ne\vec{v}_d$

Gauss's law: $\oint \mathbf{E} \cdot \overrightarrow{d\mathbf{a}} = q_{net} / \epsilon_0$

Electric potential and potential energy: $V = U/q$; $dU = qdV$

Potential difference and emf: $\int_a^b \mathbf{E} \cdot \overrightarrow{d\mathbf{l}} = -(V_b - V_a)$; $\oint \mathbf{E} \cdot \overrightarrow{d\mathbf{l}} = 0$

Power: $P = vi$

Capacitor: $q = CV$, $U = q^2 / (2C)$

Solution to $\frac{dy}{dx} + ax = b$ has the form $y = Ae^{-ax} + b/a$

Faraday's law: $\mathcal{E}_{ind} = \int_a^b \mathbf{E} \cdot \overrightarrow{d\mathbf{l}} = -\frac{d}{dt} \int \mathbf{B} \cdot \overrightarrow{d\mathbf{a}} = -L \frac{di}{dt}$

Inductor: $\mathcal{E} = L \frac{di}{dt}$

Magnetic field of ideal solenoid: $B = \mu_0 nI$

Euler's formula: $e^{j\theta} = \cos\theta + j\sin\theta$

Complex impedance: $Z = R + jX = |Z|e^{j\phi}$; $\tilde{v} = Z\tilde{i}$; $v = \text{Re}(\tilde{v}) = V\cos\omega t$

Capacitive impedance: $Z_C = -jX_C = \frac{1}{j\omega C}$ Inductive impedance: $Z_L = jX_L = j\omega L$

Series impedance: $Z = \sum Z_i$ Parallel impedance: $\frac{1}{Z} = \sum \frac{1}{Z_i}$


Complex voltage gain: $a = \frac{\tilde{v}_{out}}{\tilde{v}_{in}}$

Gain in dB: $G_{dB} = 20 \log \left| \frac{\tilde{v}_2}{\tilde{v}_1} \right|$

Q Factor: $Q = \omega_0 L / R$

Phys 2610 (2018) Midterm Solution

①

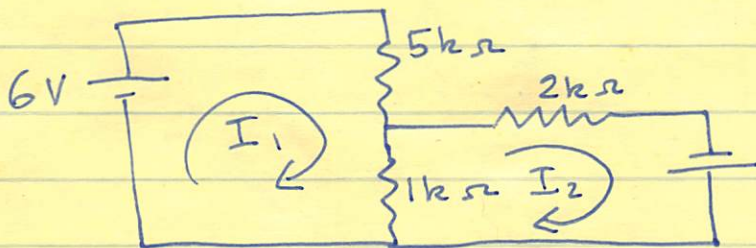

$$\begin{aligned} \text{loop 1: } 6V - I_1(5k\Omega) - (I_1 - I_2)(1k\Omega) &= 0 \\ \rightarrow I_1(-6k\Omega) + I_2(1k\Omega) &= -6V \quad \text{--- ①} \end{aligned}$$

$$\begin{aligned} \text{loop 2: } 1.5V - (I_2 - I_1)(1k\Omega) - I_2(2k\Omega) &= 0 \\ \rightarrow I_1(1k\Omega) + I_2(-3k\Omega) &= -1.5V \end{aligned}$$


$$\begin{aligned} \text{①} + 6\text{②} \rightarrow 0 + I_2(1k\Omega - 18k\Omega) &= (-6V - 9V) \\ \rightarrow I_2 = \frac{-15V}{-17k\Omega} &= 0.88 \text{ mA} \end{aligned}$$

$$\text{①} \rightarrow I_1 = \frac{-6V - I_2(1k\Omega)}{-6k\Omega} = 1.15 \text{ mA}$$


$$\begin{aligned} \text{Current through } 5k\Omega: \quad I_1 &= \underline{1.15 \text{ mA}} \\ 2k\Omega: \quad I_2 &= \underline{0.88 \text{ mA}} \\ 1k\Omega: \quad I_1 - I_2 &= \underline{0.27 \text{ mA}} \end{aligned}$$

$$\begin{aligned} \text{Power delivered by 6V battery: } P &= V \cdot I_1 = (6V)(1.15 \text{ mA}) \\ &= \underline{6.9 \text{ mW}} \end{aligned}$$

②

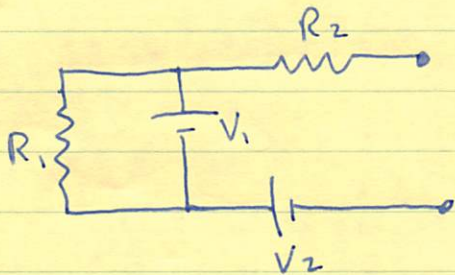

Thevenin

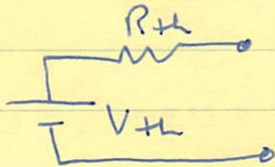


V_{th} = open ckt voltage

$$\rightarrow V_{th} = V_1 + V_2$$


(since no current flows in R_2)

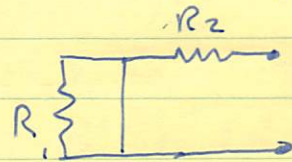R_{th} is resistance with batteries shorted:



$$R_{th} = R_1 // 0 + R_2 \rightarrow R_{th} = R_2$$

Norton

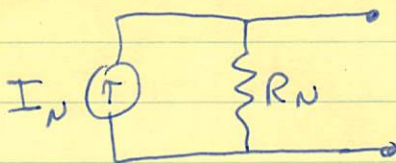

$$R_N = R_{th} \rightarrow R_N = R_2$$

I_N = short circuit current \rightarrow

$$I_N = \frac{V_1 + V_2}{R_2}$$

Power


Max power transfer \Rightarrow

$$R_L = R_{th} = R_2$$

Recall $P = I^2 R_L = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 R_L = V_{th}^2 \left(\frac{R_L}{(R_{th} + R_L)^2} \right)$

and $\frac{d}{dR_L} \frac{R_L}{(R_{th} + R_L)^2} = 0 \Rightarrow R_L = R_{th}$

③

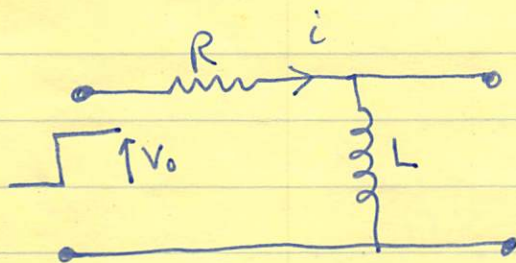

Kirchhoff's rule: $V_0 - iR - L \frac{di}{dt} = 0$

$$\frac{di}{dt} + \frac{R}{L} i = \left(\frac{1}{L}\right) V_0$$

$$\rightarrow i = A e^{-Rt/L} + \frac{V_0}{R}$$

Boundary condition: At $t=0$, $i=0$ ($L \frac{di}{dt}$ is max)

$$\rightarrow 0 = A + \frac{V_0}{R} \rightarrow A = -\frac{V_0}{R}$$


$$\rightarrow i = \frac{V_0}{R} (1 - e^{-Rt/L})$$

For $t \rightarrow \infty$, $i \rightarrow \frac{V_0}{R}$

Output Voltage: $V_L = L \frac{di}{dt} = L \frac{V_0}{R} (-e^{-Rt/L}) \cdot \left(\frac{-R}{L}\right)$

$$V_L = V_0 e^{-Rt/L}$$

4

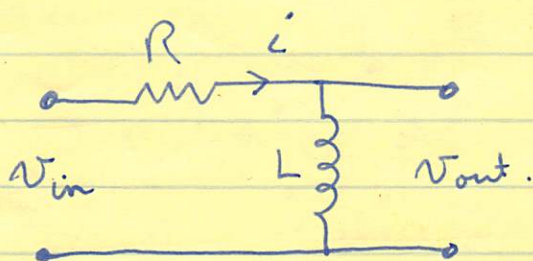

$$V_{out} = L \frac{di}{dt}$$

but $i = \frac{V_{in} - V_{out}}{R}$, so

$$V_{out} = \frac{L}{R} \frac{d}{dt} (V_{in} - V_{out})$$

If $V_{out} \ll V_{in}$,


$$V_{out} = \frac{L}{R} \frac{d}{dt} V_{in}$$

For harmonic voltage, $V_{out} \ll V_{in}$ corresponds to $\omega L \ll R$

or

$$\frac{\omega L}{R} \ll 1$$

(5)

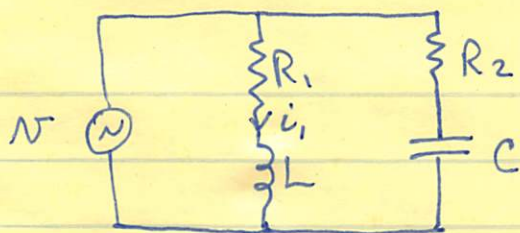

Impedance: $Z = Z_1 // Z_2 = (R_1 + j\omega L) // (R_2 + \frac{1}{j\omega C})$

$$Z = \frac{|Z_1| e^{j\theta_1} |Z_2| e^{j\theta_2}}{(R_1 + R_2) + j(\omega L - \frac{1}{\omega C})} = \frac{|Z_1| |Z_2| e^{j(\theta_1 + \theta_2 - \theta_3)}}{|Z_3|} \quad (\text{polar})$$

where $|Z_1| = \sqrt{R_1^2 + (\omega L)^2}$, $|Z_2| = \sqrt{R_2^2 + (1/\omega C)^2}$,

$$|Z_3| = \sqrt{(R_1 + R_2)^2 + (\omega L - 1/\omega C)^2}, \quad \tan \theta_1 = \omega L / R_1,$$

$$\tan \theta_2 = 1/\omega R C, \quad \tan \theta_3 = \frac{\omega L - 1/\omega C}{R_1 + R_2}$$

Current through R_1 :

Complex impedance in R_1 branch: $Z_1 = R_1 + j\omega L$

$$\text{or } Z_1 = |Z_1| e^{j\theta} = \sqrt{R_1^2 + (\omega L)^2} e^{j\theta}; \quad \tan \theta = \omega L / R_1$$

Then, since $\tilde{i}_1 = \frac{\tilde{v}}{Z_1}$, if $v = V_0 \sin \omega t$

$$i_1 = \frac{V_0}{\sqrt{R_1^2 + (\omega L)^2}} \sin(\omega t - \theta); \quad \tan \theta = \omega L / R_1$$

Note 1: Rectangular representation of Z :

$$\begin{aligned} Z &= \frac{(R_1 + j\omega L)(R_2 + \frac{1}{j\omega C})}{(R_1 + R_2) + j(\omega L - \frac{1}{\omega C})} = \frac{(R_1 R_2 + L/C) + j(R_2 \omega L - R_1/\omega C)}{(R_1 + R_2) + j(\omega L - \frac{1}{\omega C})} \\ &= \frac{[(R_1 R_2 + L/C) + j(R_2 \omega L - R_1/\omega C)][(R_1 + R_2) - j(\omega L - \frac{1}{\omega C})]}{(R_1 + R_2)^2 + (\omega L - \frac{1}{\omega C})^2} \\ &= \left\{ \frac{[(R_1 R_2 + L/C)(R_1 + R_2) + (R_2 \omega L - R_1/\omega C)(\omega L - \frac{1}{\omega C})] + j[(R_1 R_2 + L/C)(\frac{1}{\omega C} - \omega L) + (R_2 \omega L - \frac{R_1}{\omega C})(R_1 + R_2)]}{(R_1 + R_2)^2 + (\omega L - \frac{1}{\omega C})^2} \right\} \end{aligned}$$

(rect)

Note 2: $v = V_0 \sin \omega t = \operatorname{Re}(\tilde{v})$ with $\tilde{v} = V_0 e^{j(\omega t - \pi/2)}$

$$\underline{i} = \operatorname{Im}(\tilde{i}) \text{ with } \tilde{i} = V_0 e^{j\omega t}$$

Then $\tilde{i} = \frac{\tilde{v}}{Z_1} = \frac{\tilde{v}}{\sqrt{R_1^2 + (\omega L)^2}} e^{-j\theta}$


and

$$i = \operatorname{Re}\left(\frac{V_0 e^{j(\omega t - \pi/2 - \theta)}}{|Z_1|}\right) \rightarrow \boxed{i = \frac{V_0 \sin(\omega t - \theta)}{|Z_1|}}$$

i

$$\underline{i} = \operatorname{Im}\left(\frac{V_0 e^{j(\omega t - \theta)}}{|Z_1|}\right) \rightarrow \boxed{i = \frac{V_0 \sin(\omega t - \theta)}{|Z_1|}}$$

⑥

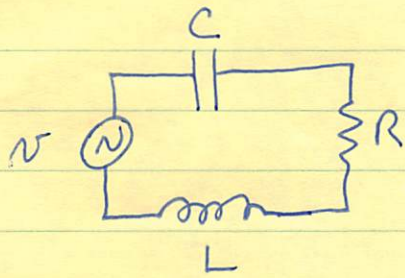

$$L = 100 \text{ mH}$$

$$C = 10 \mu\text{F}$$


$$R = 10 \Omega$$

$$v = V_0 e^{j\omega t}$$

Resonant freq: $\omega_0 = \frac{1}{\sqrt{LC}} = 1000 \text{ rad/s}$

Q-factor: $Q = \omega_0 L / R = 10$

but $Q = \frac{\omega_0}{\Delta\omega}$

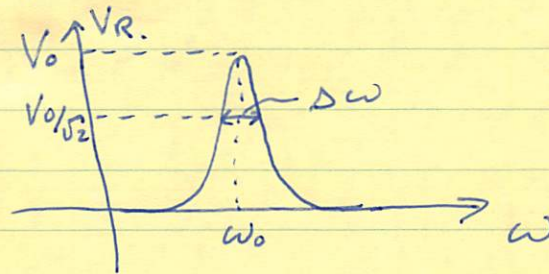

Where $\omega_0 \pm \frac{\Delta\omega}{2}$ represent 3dB attenuation points: $\left(\frac{V_R}{V_0} = \frac{1}{\sqrt{2}}\right)$

Then $\Delta\omega = \omega_0 / Q = 100 \text{ rad/s}$, so

$$\omega_{3dB} = \left(1000 \pm \frac{100}{2}\right) \text{ rad/s} = 950, 1050 \text{ rad/s}$$

Also $v_R = iR = \frac{R}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}} V_0 e^{j(\omega t - \theta)}$

$$\text{So } \frac{V_R}{V_0} = \frac{R}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}} = \frac{1}{\sqrt{1 + (\omega L - 1/\omega C)^2 / R^2}}$$

$$\therefore \frac{V_R}{V_0} = \frac{1}{\sqrt{2}} \quad \text{When } (\omega L - 1/\omega C)^2 = R^2$$

$$\Rightarrow \omega L - 1/\omega C = \pm R \Rightarrow \omega^2 L \pm \omega R - 1/C = 0$$

$$\Rightarrow \omega = \frac{\pm R \pm \sqrt{R^2 + 4L/C}}{2L} = \pm 950 \text{ rad/s}, \pm 1050 \text{ rad/s}$$

(physical values are positive)