
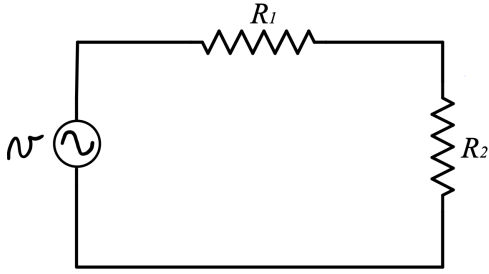


Phys2610 (2019) Assignment 2
Due Thursday, Feb 7, 2019

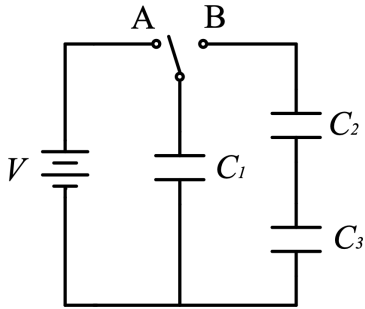
1. For the circuit below, if v is a sinusoidal voltage with an amplitude of 8 V, $R_1 = 5.6 \text{ k}\Omega$, and $R_2 = 2.8 \text{ k}\Omega$, calculate the peak, the rms, and the average voltage across R_2 . What is the maximum instantaneous power dissipated by the R_2 ? What is the average power dissipated by R_2 ? What is the average power supplied by the signal generator?



2. In the circuit below, the capacitors are initially uncharged. The switch is first put in position A for a long time, and then switched to position B. Find the final charges on the 3 capacitors after equilibrium is established.



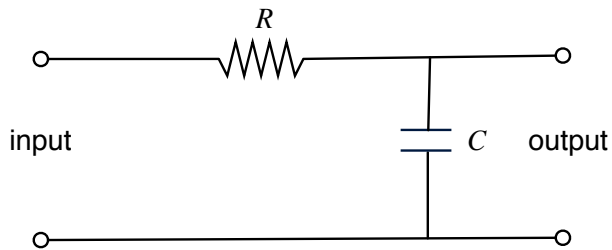3. Determine the output voltage as a function of time for the circuit shown below if the input is a step function from -1 V to $+6 \text{ V}$, for $R = 1 \text{ M}\Omega$, and $C = 100 \text{ }\mu\text{F}$. Sketch the voltage to scale as a function of time from zero to 4 time constants.



4. For the circuit below, with $V_0 = 10 \text{ V}$, $R = 10 \text{ }\Omega$, and $L = 100 \text{ mH}$, what is the current after the circuit reaches equilibrium? How long does it take for the current to increase from 0.1 A to 0.9 A ?

