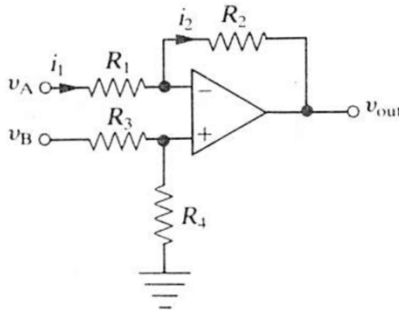



**Phys2610 (2019) Assignment 5**  
**Due 2 April 2019**

1. Find a general expression for the output of the following circuit, and show that it reduces to  $v_{out} = \frac{R_2}{R_1}(v_B - v_A)$  when  $\frac{R_1}{R_2} = \frac{R_3}{R_4}$ .




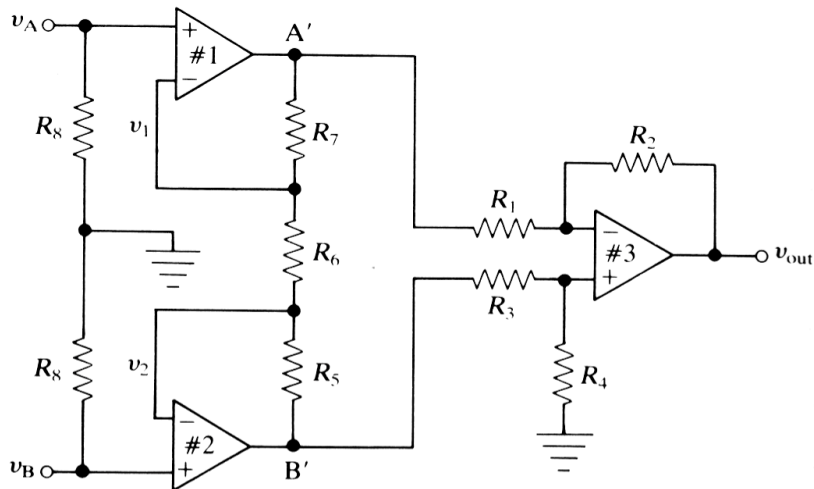2. Show that the gain for the following circuit, with  $R_5 = R_7 = R$ , and  $\frac{R_1}{R_2} = \frac{R_3}{R_4}$  is given by

$$a = \frac{v_{out}}{v_A - v_B} = -\frac{R_2}{R_1} \left( 1 + \frac{2R}{R_6} \right)$$



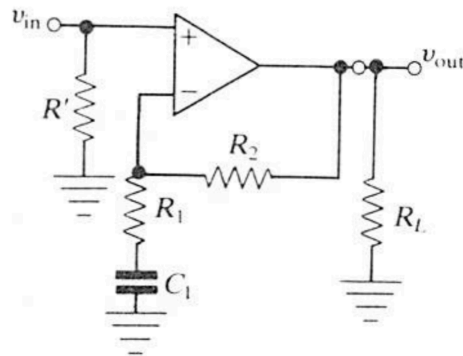3. Find an expression for the complex gain of the following circuit, when  $\omega = \omega_1 = 1/(R_1 C_1)$ .



4. Design a summing amplifier to sum from inputs  $v_A, v_B, v_C, v_D$  and to produce an output of  $v_{out} = v_A + 2v_B + 4v_C + 8v_D$ .

5. Design an op amp differentiator with an output given by  $v_{out} = -(10^{-6}\text{s}) \frac{d}{dt} v_{in}$ . If an input step function rises from 0 to 1 V in  $2 \mu\text{s}$  and then is constant at 1V, sketch the output.

6. Design an ideal diode op amp circuit to produce a negative half-waveform from a sinusoidal input.