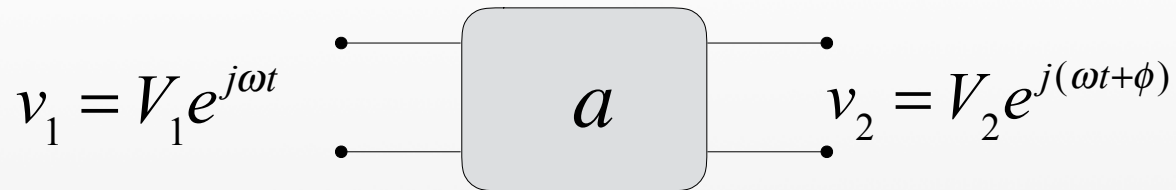


6) RC filters and gain in dB




Complex gain:
$$a = \frac{v_2}{v_1} = \frac{V_2 e^{j(\omega t + \phi)}}{V_1 e^{j\omega t}} = \frac{V_2}{V_1} e^{j\phi}$$

Magnitude:
$$|a| = \left| \frac{v_2}{v_1} \right| = \frac{V_2}{V_1}$$

Phase:
$$\phi$$

Gain in dB:
$$G_{dB} = 20 \log \left(\frac{V_2}{V_1} \right)$$

(a) High pass filter

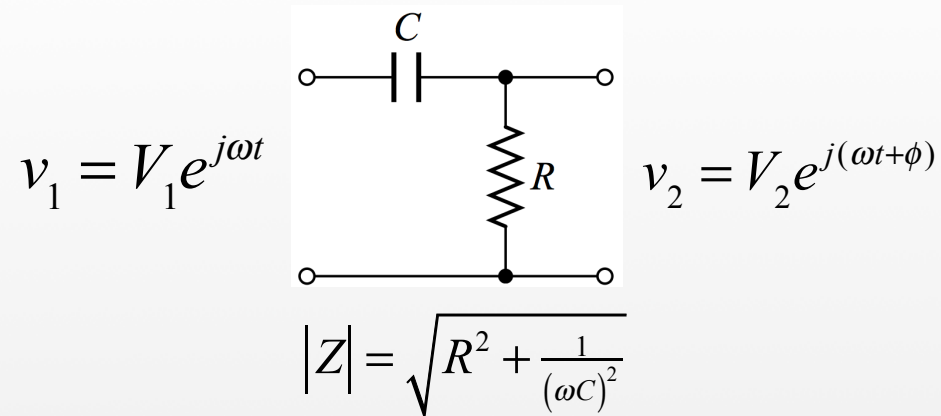

$$\frac{V_2}{V_1} = \frac{R}{|Z|} = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

$$\left\{ \begin{array}{l} \approx \omega RC \quad \text{for small } \omega \\ = \frac{1}{\sqrt{2}} \quad \text{for } \omega = \frac{1}{RC} \\ \approx 1 \quad \text{for large } \omega \end{array} \right.$$

$$G_{dB} = 20 \log(RC) + 20 \log(\omega)$$

$$G_{dB} = -3dB$$

$$G_{dB} = 0$$

$$\frac{V_2}{V_1} = \frac{R}{|Z|} = \frac{\omega RC}{\sqrt{1+(\omega RC)^2}}$$



$$\approx \omega RC$$

for small ω

$$G_{dB} = 20\log(RC) + 20\log(\omega)$$

$$= \frac{1}{\sqrt{2}}$$

for $\omega = 1/RC$


$$G_{dB} = -3dB$$

$$\approx 1$$

for large ω

$$G_{dB} = 0$$


G_{dB}

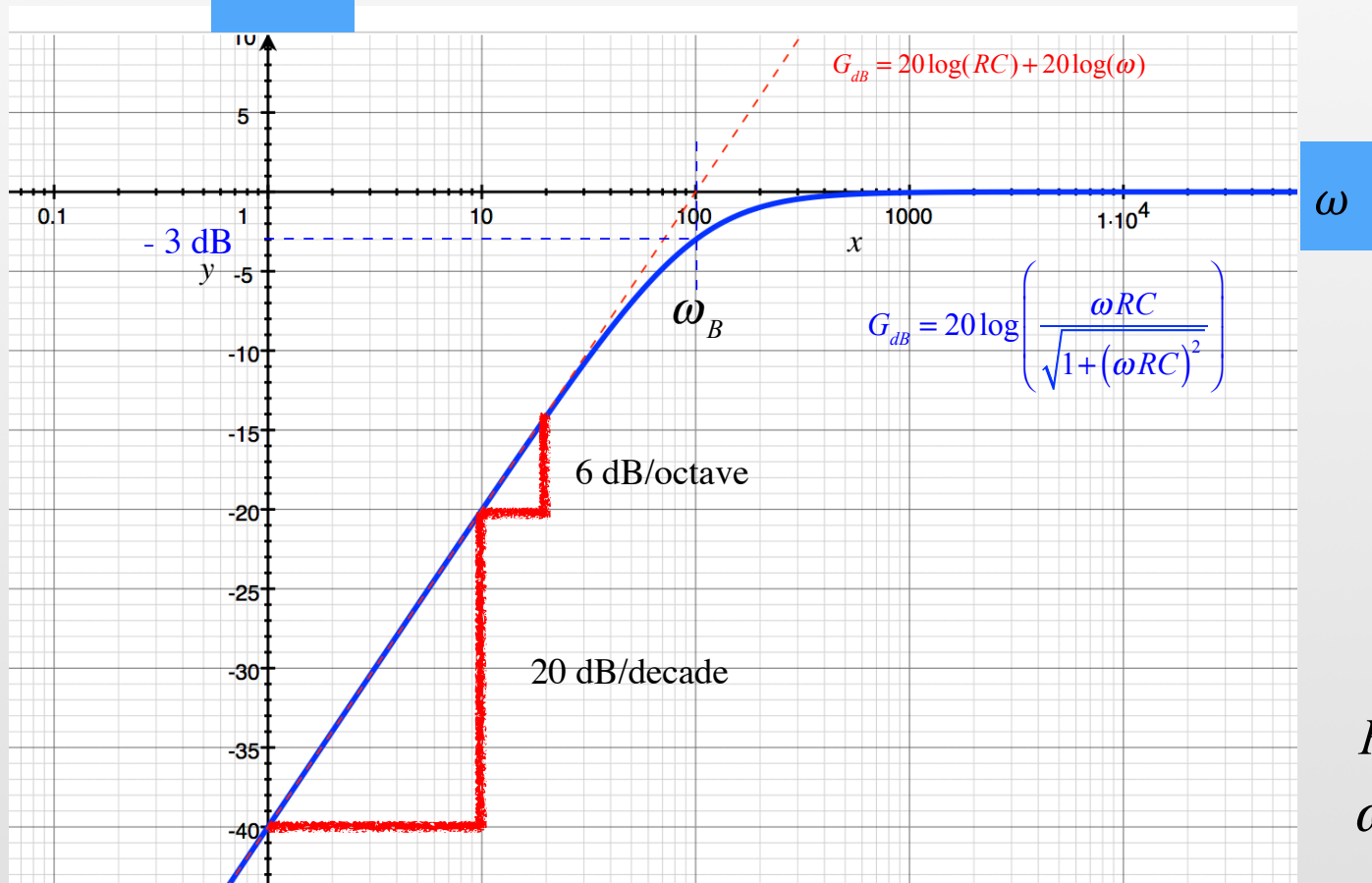

$$RC = 0.01s$$

$$\omega_B = 100\text{rad/s}$$

(b) Low pass filter

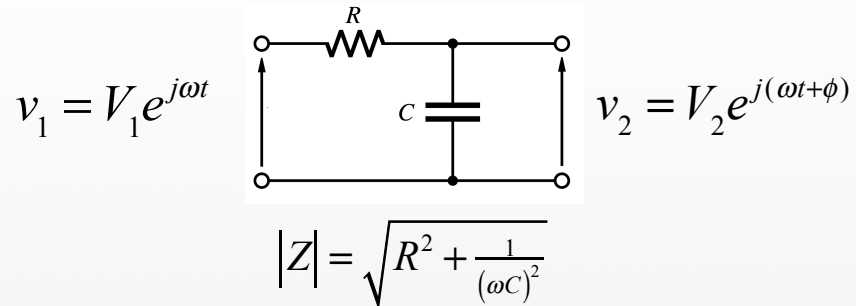

$$\frac{V_2}{V_1} = \frac{1/\omega C}{|Z|} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\left\{ \begin{array}{ll} \approx \frac{1}{\omega RC} & \text{for large } \omega \\ = \frac{1}{\sqrt{2}} & \text{for } \omega = 1/RC \\ \approx 1 & \text{for small } \omega \end{array} \right.$$

$$G_{dB} = -20 \log(RC) - 20 \log(\omega)$$

$$G_{dB} = -3dB$$

$$G_{dB} = 0$$

$$\frac{V_2}{V_1} = \frac{1/\omega C}{|Z|} = \frac{1}{\sqrt{1+(\omega RC)^2}}$$



$\approx \frac{1}{\omega RC}$ for large ω


$$G_{dB} = -20 \log(RC) - 20 \log(\omega)$$

$= \frac{1}{\sqrt{2}}$ for $\omega = 1/RC$

$$G_{dB} = -3dB$$

≈ 1 for small ω

$$G_{dB} = 0$$

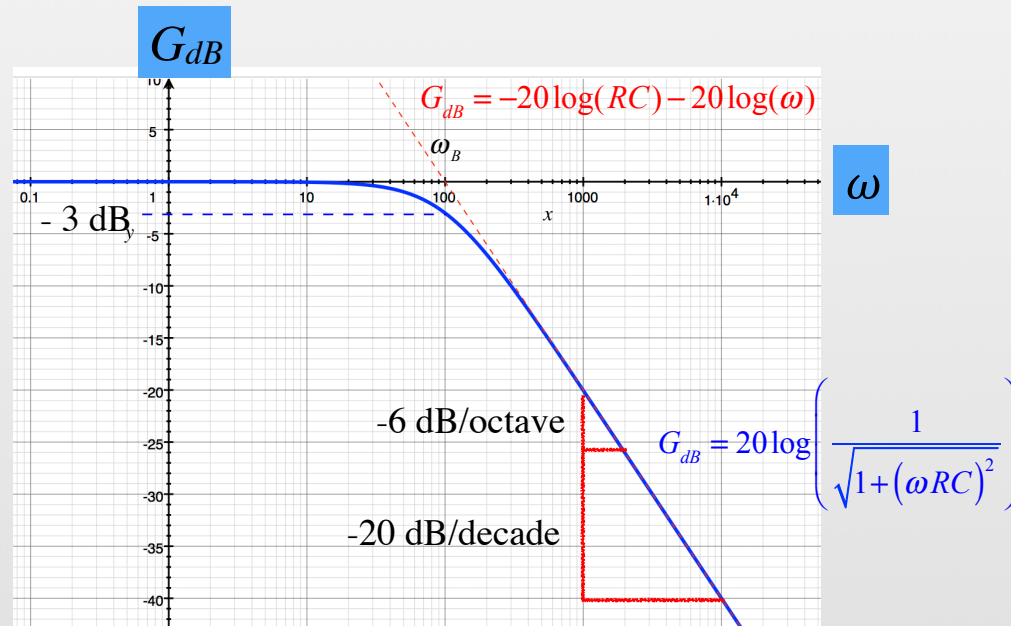

$$RC = 0.01s$$

$$\omega_B = 100 \text{ rad/s}$$