

2) *Base conversion*

a) *B to decimal*

$$a_m \cdots a_2 a_1 a_0 = \sum \underbrace{a_i B^i}_{\text{expressed in decimal}}$$

$$243_6 = 2 \times 6^2 + 4 \times 6^1 + 3 \times 6^0 = 99_{10}$$

b) B to B'

$$(a_m \cdots a_2 a_1 a_0)_B = \sum \underbrace{a_i B^i}_{\text{expressed in base B'}}$$

e.g. decimal to binary:

$$493_{10} = 100 \times (1010)^{10} + 1001 \times (1010)^1 + 11 \times (1010)^0$$

4 in binary 10 in binary 9 3

$100 \times \begin{array}{r} 1010 \\ 1010 \\ \hline 0000 \\ 1010 \\ 0000 \\ 1010 \\ \hline 1100100 \end{array}$	$\begin{array}{r} 1001 \\ 1010 \\ \hline 0000 \\ 1001 \\ 0000 \\ 1001 \\ \hline 1011010 \end{array}$
---	--

$$493_{10} = 110010000 + 1011010 + 11 = 111101101$$

check: $1 + 0 + 4 + 8 + 0 + 32 + 64 + 128 + 256 = 493$

LSB

$$\text{mod}(x, B)$$

$$\cdot \text{mod}\left(\text{int}\left(\frac{x}{B}\right), B\right)$$

$$\cdot \text{mod}\left(\text{int}\left(\frac{\text{int}\left(\frac{x}{B}\right)}{B}\right), B\right)$$

$$\cdot \cdot$$

MSB

$$493_{10} = 111101101_2$$

$$493 / 2 = 246 \quad \text{rem } 1$$

$$246 / 2 = 123 \quad \text{rem } 0$$

$$123 / 2 = 61 \quad \text{rem } 1$$

$$61 / 2 = 30 \quad \text{rem } 1$$

$$30 / 2 = 15 \quad \text{rem } 0$$

$$15 / 2 = 7 \quad \text{rem } 1$$

$$7 / 2 = 3 \quad \text{rem } 1$$

$$3 / 2 = 1 \quad \text{rem } 1$$

$$1 / 2 = 0 \quad \text{rem } 1$$

Octal ↔ Binary

$$a_m \cdots a_1 a_0 = \sum a_i B^i = \sum a_i (1000)^i$$

$$372_8 = (011)(1000)^{10} + 111(1000)^1 + 010$$

$$\begin{array}{r} 011\ 000\ 000 \\ 111\ 000 \\ 010 \\ \hline 011\ 111\ 010 \\ 3\ 7\ 2 \end{array}$$

Each octal digit can be replaced by the equivalent 3-bit binary number.

Hexadecimal ↔ Binary

$$a_m \cdots a_1 a_0 = \sum a_i B^i = \sum a_i (10000)^i$$

$$\$D49 = (1101)(10000)^{10} + 0100(10000)^1 + 1001$$

$$\begin{array}{r} 1101\ 0000\ 0000 \\ 0100\ 0000 \\ 1010 \\ \hline 1101\ 0100\ 1001 \\ D\ 4\ 9 \end{array}$$

Each hex digit can be replaced by the equivalent 4-bit binary number.

Decimal \rightarrow hex \rightarrow binary

Recall $493_{10} = 111101101_2$

$493 / 16 = 30$ rem=13 or D

$30 / 16 = 1$ rem=14 or E

$1 / 16 = 0$ rem=1

\$1ED = 1 1110 1101

1 E D

3) Boolean Algebra

Algebra of two-valued variables (T, F or 1,0)

with 3 fundamental operators: logical AND, OR, NOT

a) logical AND

symbol \cdot


Truth table for $A \cdot B$

A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

Other symbols: \wedge \cap

or no symbol: $A \cdot B = AB$

e.g.

 

Lamp is on if $S1 \cdot S2 = 1$

b) logical OR

(inclusive OR)


symbol +

Truth table for $A+B$

A	B	$A+B$
0	0	0
0	1	1
1	0	1
1	1	1

Other symbols: \vee \cup

e.g.

 

Lamp is on if $A+B = 1$

c) logical NOT (complement)

symbol \bar{A}

Truth table for \bar{A}

A	\bar{A}
0	1
1	0

Other symbols: \neg \sim

$$\bar{1} = 0$$

$$\bar{0} = 1$$

d) Identities

$$A \cdot A = A \quad 1 \cdot 1 = 1 \quad 0 \cdot 0 = 0$$

$$A + A = A \quad 1 + 1 = 1 \quad 0 + 0 = 0$$

$$\bar{A} \cdot A = 0 \quad 0 \cdot 1 = 0 \quad 1 \cdot 0 = 0$$

$$\bar{A} + A = 1 \quad 1 + 0 = 1 \quad 0 + 1 = 1$$

$$A \cdot 1 = A \quad 0 \cdot 1 = 0 \quad 1 \cdot 1 = 1$$

$$A + 1 = 1 \quad 1 + 1 = 1 \quad 0 + 1 = 1$$

$$A \cdot 0 = 0 \quad 0 \cdot 0 = 0 \quad 1 \cdot 0 = 0$$

$$A + 0 = A \quad 0 + 0 = 0 \quad 1 + 0 = 1$$

e) Theorems

(i) Commutative

$$A \cdot B = B \cdot A$$

$$A + B = B + A$$

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

A	B	A·B
0	0	0
0	1	0
1	0	0
1	1	1

(ii) Associative

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

$$(A + B) + C = A + (B + C) \rightarrow$$

A	B	C	A+B	(A+B)+C	(B+C)	A+(B+C)
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	1	0	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

(iii) *Distributive*

$$x \cdot (y + z) = x \cdot y + x \cdot z$$

TABLE 6 Verifying One of the Distributive Laws.

x	y	z	$y + z$	xy	xz	$x(y + z)$	$xy + xz$
1	1	1	1	1	1	1	1
1	1	0	1	1	0	1	1
1	0	1	1	0	1	1	1
1	0	0	0	0	0	0	0
0	1	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	0	1	1	0	0	0	0
0	0	0	0	0	0	0	0

$$(A + B) \cdot (A + C) = A + B \cdot C$$

$$(A + B) \cdot (A + C) = (A + B) \cdot A + (A + B) \cdot C$$

$$= A \cdot A + B \cdot A + A \cdot C + B \cdot C$$

$$= A(1 + B + C) + B \cdot C$$

$$= A + B \cdot C$$

(iii) De Morgan's theorem

Any binary expression is unchanged if

- 1) complement all variables
- 2) replace ORs with ANDs
- 3) replace ANDs with ORs
- 4) complement entire expression

e.g. $A \cdot B = \overline{\overline{A + B}}$

$$A + B = \overline{\overline{A \cdot B}}$$

$$\overline{A + B} = \overline{\overline{\overline{A \cdot B}}} = \overline{A \cdot B}$$

$$\overline{A \cdot B} = \overline{\overline{\overline{A + B}}} = \overline{A + B}$$



break the line
change the sign

Proof of two De Morgan relations

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$


A	B	A+B	$\overline{A+B}$	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

$$\overline{\bar{A} \cdot \bar{B}} = \bar{\bar{A}} + \bar{\bar{B}}$$


A	B	A·B	$\overline{A \cdot B}$	\bar{A}	\bar{B}	$\bar{\bar{A}} + \bar{\bar{B}}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

4) Binary gates

a) NOT

 

A	\bar{A}
0	1
1	0

 

V_A	V_F
0	5 V
5 V	0.1 V

positive logic:


0 \rightarrow ~ 0 V

1 \rightarrow ~ 5V


If the input is high, the transistor turns on, grounding the output.

If the input is low, the transistor turns off, leaving the output high.

b) OR

 

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

 

V_A	V_B	V_F
0	0	0
0	5V	4.4V
5V	0	4.4V
5V	5V	4.4V

positive logic:


0 \rightarrow 0V

1 \rightarrow ~5V

A high on either input turns on the respective diode, raising the output high.

If both inputs are low, the diodes are both off, so no current flows, and the output is low.


Transistor OR Gate

 

If either transistor turns on (i.e. if either A or B is high) then the output is tied to $V_{cc} = 6\text{ V}$.

If both transistors are off (i.e. if both A and B are low) then there is no current through R, so the output is low (\sim zero).

extends easily to multiple inputs:

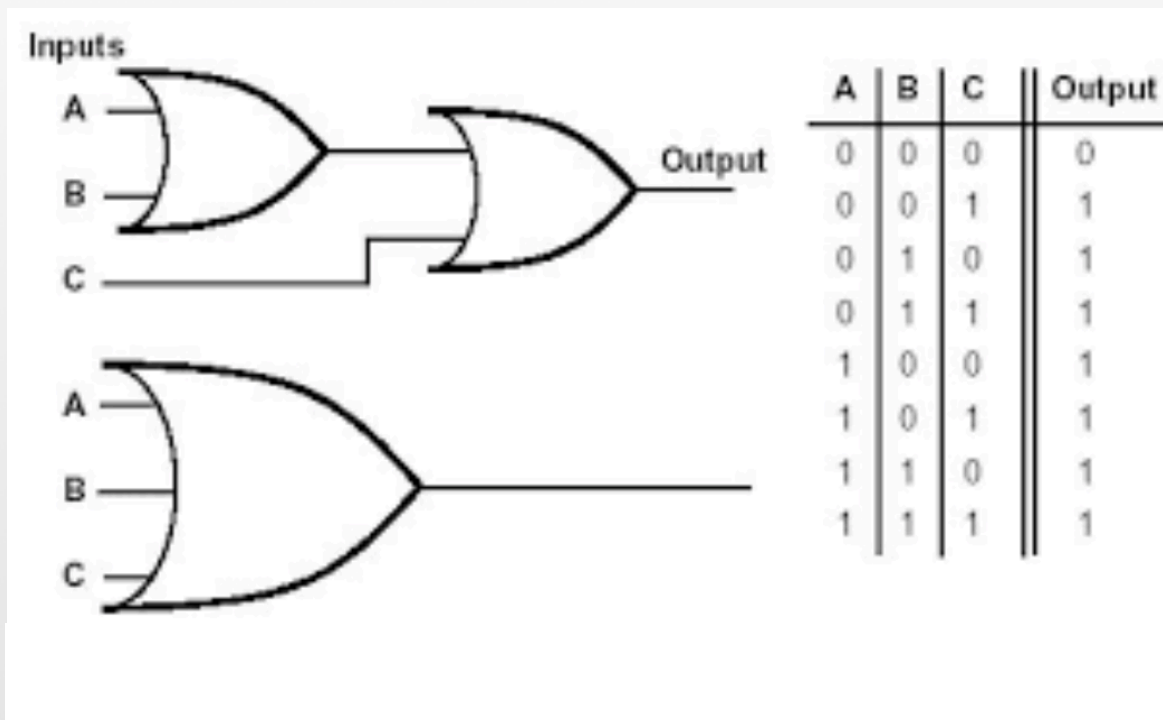


c) AND



Input		Output
A	B	$F = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

Diode AND Gate

 

V_A	V_B	V_F
0	0	.6 V
0	5V	.6 V
5V	0	.6 V
5V	5V	5 V


positive logic:

0 \rightarrow $\sim 0V$ ($< \sim .6V$)

1 \rightarrow $\sim 5V$

A low on either input turns on the respective diode, bringing the output to low.


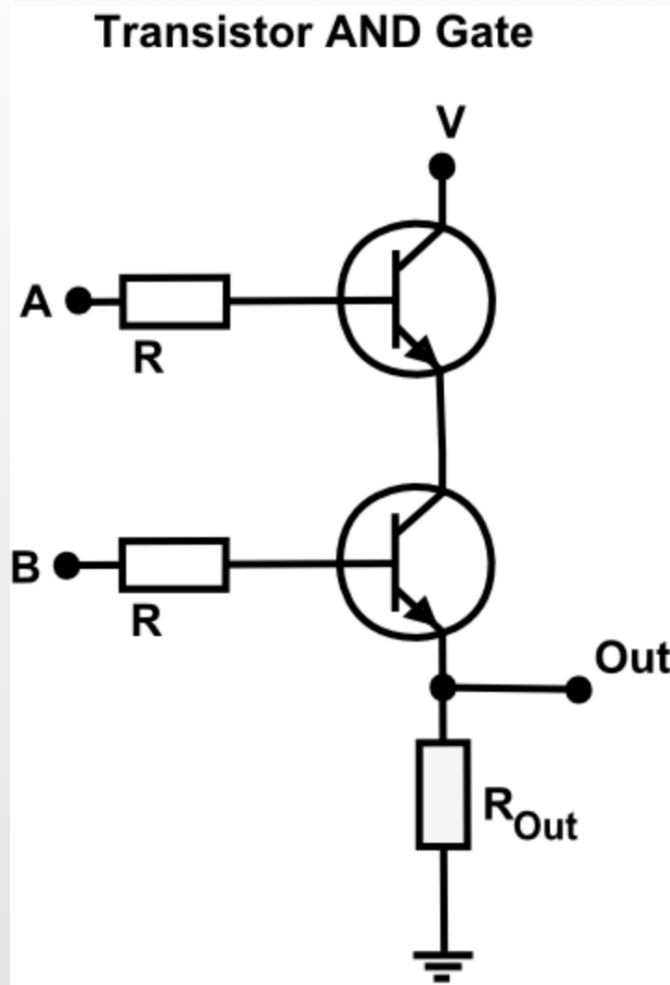
If both inputs are high, the diodes are both off, so no current flows, and the output is high.



If both transistors turn on
(i.e. if both A and B are high)
then the output is tied to V_{cc} (high).



If either transistor is off
(i.e. if either A or B is low)
then there is no current through R ,
so the output is low (\sim zero).

extends easily to multiple inputs:

  

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

d) NOR (NOT OR)

 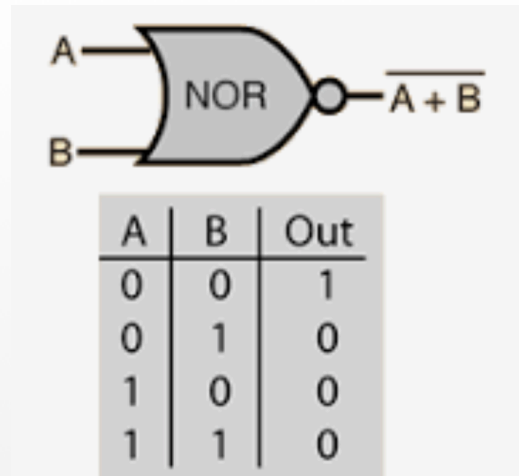

V_A	V_B	V_F
0	0	5 V
0	5V	0.1 V
5V	0	0.1 V
5V	5V	0.1V


If either input is high, the respective transistor turns on, and the output is switched to ground (low).

If both inputs are low, both transistors turn off, so no current flows and the output is high.

NOR gate as universal gate:


NOT

$$\bar{A} = \overline{A + A}$$

 

OR


$$A + B = \overline{\overline{A + B}}$$

 



AND

$$A \cdot B = \overline{\overline{A + B}}$$

De Morgan

 

e) NAND (NOT AND)

  

V_A	V_B	V_F
0	0	5 V
0	5V	5 V
5V	0	5 V
5V	5V	0.1V


If either input is low, the respective transistor turns off, so no current flows, and the output is high.

If both inputs are high, both transistors turn on, and the output is switched to ground (low).

NAND gate as universal gate:


NOT

$$\bar{A} = \overline{A \cdot A}$$

 


OR
 
$$A + B = \overline{\overline{A} \cdot \overline{B}}$$




AND
 
$$A \cdot B = \overline{\overline{A \cdot B}}$$



f) Exclusive OR (XOR)

 

check:

A	B	$A+B$	$A \cdot B$	$\overline{A \cdot B}$	$(A+B) \cdot \overline{(A \cdot B)}$
0	0	0	0	1	0
0	1	1	0	1	1
1	0	1	0	1	1
1	1	1	1	0	0

A	B	$F = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

- either, but not both

$$A \oplus B = (A+B) \cdot \overline{(A \cdot B)}$$

$$\begin{aligned} A \oplus B &= (A+B) \cdot \overline{(A \cdot B)} \\ &= A \cdot \overline{A \cdot B} + B \cdot \overline{A \cdot B} \\ &= A \cdot (\overline{A} + \overline{B}) + B \cdot (\overline{A} + \overline{B}) \\ &= 0 + A \cdot \overline{B} + B \cdot \overline{A} + 0 \end{aligned}$$


dist.

De Morgan

$$A \cdot \overline{A} = 0$$


$$A \oplus B = A \cdot \overline{B} + B \cdot \overline{A}$$
 
$$A \oplus B = A \cdot \bar{B} + B \cdot \bar{A}$$




- can be constructed with all NOR or all NAND gates.

Controllable inverter:

 

Control: high \rightarrow inverter
low \rightarrow leave as is

g) Exclusive NOR

 

A	B	$A \oplus B$	$\overline{A \oplus B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

$$\overline{A \oplus B} = \overline{A \cdot \overline{B} + \overline{A} \cdot B}$$

$$= \overline{A \cdot \overline{B}} \cdot \overline{\overline{A} \cdot B}$$

$$= (\overline{A} + B) \cdot (A + \overline{B})$$

$$= \overline{A} \cdot A + \overline{A} \cdot \overline{B} + B \cdot A + B \cdot \overline{B}$$

De Morgan


De Morgan

dist.

$$\overline{A \oplus B} = \overline{A} \cdot \overline{B} + A \cdot B$$

$$A \cdot \overline{A} = 0$$
 
$$\overline{A \oplus B} = \overline{A} \cdot \overline{B} + A \cdot B$$



6) *TTL Logic*




Transistor - transistor logic

TTL: transistor used for logic and amplification

Others:

- DL - diode logic
- RTL - resistor transistor logic
- DTL - diode transistor logic)


a) two emitter transistor

   

If either b-e junction is on:

- minority carriers injected into base
- transistor on
- V_{CE} low

b) basic TTL NAND gate

 


A	B	$Q1 = A \cdot B$	$Q = \overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

- If A and B are high VT1 is off
 - Then Q1 is high
- Otherwise VT1 is on
 - and Q1 is low
- VT2 is the familiar NOT gate


High output impedance (R2):

- slow to turn off (go high)
- output current limited
- reducing R2 consumes power

 
c) TTL NAND gate with totem pole output stage



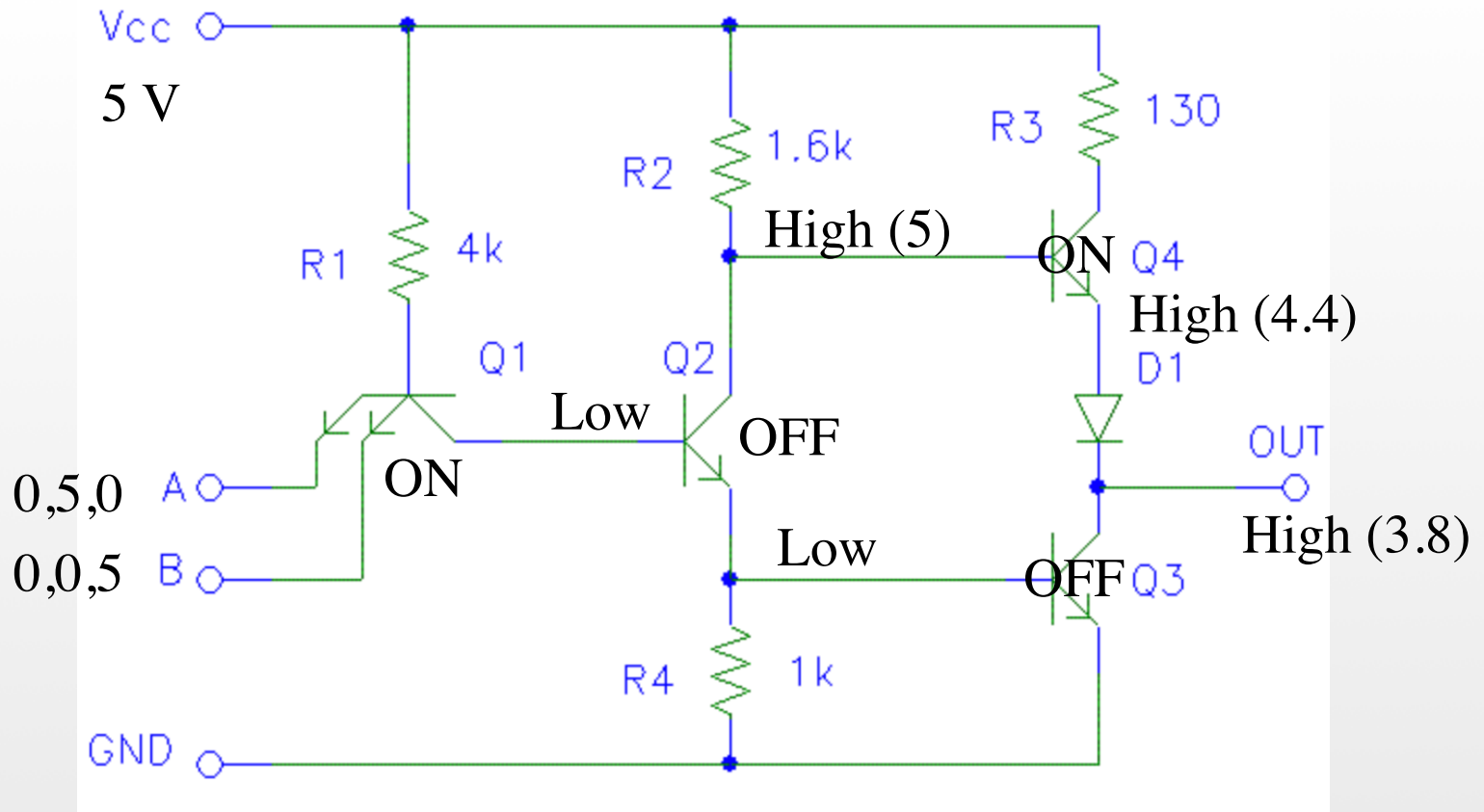- Output signal amplified for more speed
- Output load capacitance is charged and discharged through active transistors instead of resistors



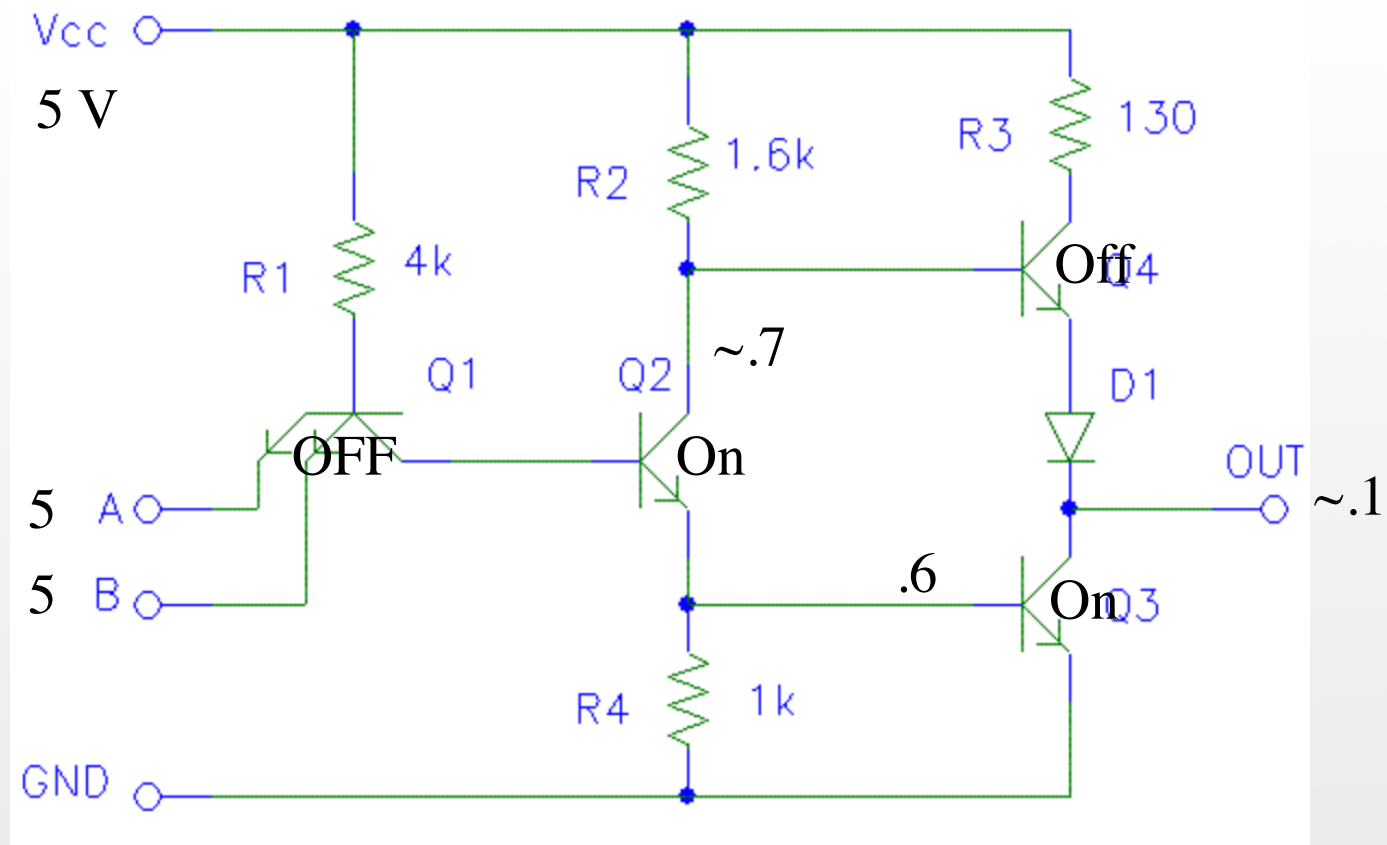Q2 off \rightarrow Vc2 high \rightarrow Q4 on \rightarrow Ve4 high (through R3; faster) \rightarrow OUT high
 \rightarrow Vb3 low \rightarrow Q3 off \rightarrow leaves OUT high



$Q2 \text{ on} \rightarrow Q3 \text{ on} \rightarrow V_{c3} \sim .1 \text{ V}$
 $\rightarrow V_{b3} = .6 \text{ V} \rightarrow V_{c2} \sim .7 \text{ V} \rightarrow Q4 \text{ off}$
 (because of diode)



d) TTL logic

logic 0: < 0.8 V; ideally 0; typically 0.1

logic 1: > 2.0 V; ideally 5; typically 3.6

regular TTL: 7400

Schottky TTL: 74S00

  

Schottky diode: semiconductor - metal
- fast, lower power

low power Schottky: 74LS00

7) Digital Addition

a) Binary addition

$$\begin{array}{r}
 1 \quad 111 \quad 1 \\
 110011010 \\
 010111011 \\
 \hline
 1001010101
 \end{array}$$

Define addition for
2 1-bit variables:



A	B	Sum $A \oplus B$	Carry $A \cdot B$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Define addition for
3 1-bit variables:

A	B	C	S_{AB} $A \oplus B$	Carry 1 $A \cdot B$	$S_{ABC} = \text{sum}(S_{AB}, C)$ $A \oplus B \oplus C$	Carry 2 $(A \oplus B) \cdot C$	Carry $(A \oplus B) \cdot C + A \cdot B$
0	0	0	0	0	0	0	0
0	0	1	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	1	0	0	1	1
1	0	0	1	0	1	0	0
1	0	1	1	0	0	1	1
1	1	0	0	1	0	0	1
1	1	1	0	1	1	0	1

b) Half adder add 2 1-bit variables

A	B	Sum $A \oplus B$	Carry $A \cdot B$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

  



c) 1-bit Full adder



Adds column with carry from previous column





A	B	C	S_{AB} $A \oplus B$	Carry 1 $A \cdot B$	$S_{ABC} = \text{sum}(S_{AB}, C)$ $A \oplus B \oplus C$	Carry 2 $(A \oplus B) \cdot C$	Carry $(A \oplus B) \cdot C + A \cdot B$
0	0	0	0	0	0	0	0
0	0	1	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	1	0	0	1	1
1	0	0	1	0	1	0	0
1	0	1	1	0	0	1	1
1	1	0	0	1	0	0	1
1	1	1	0	1	1	0	1



Inputs			Outputs	
A	B	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

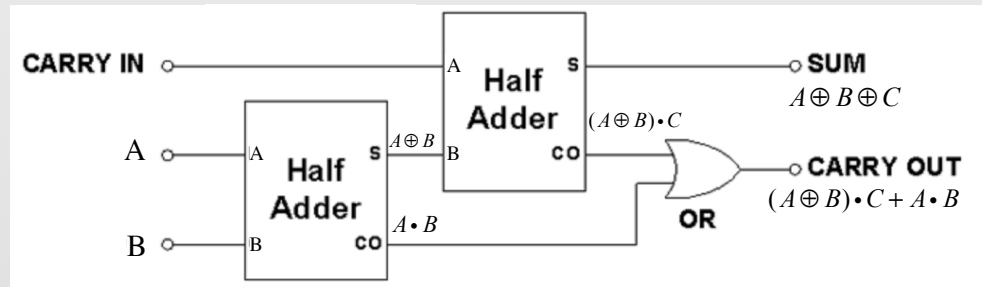 


 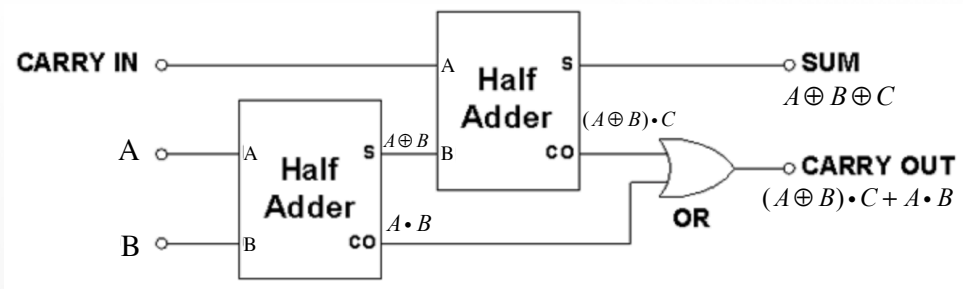

 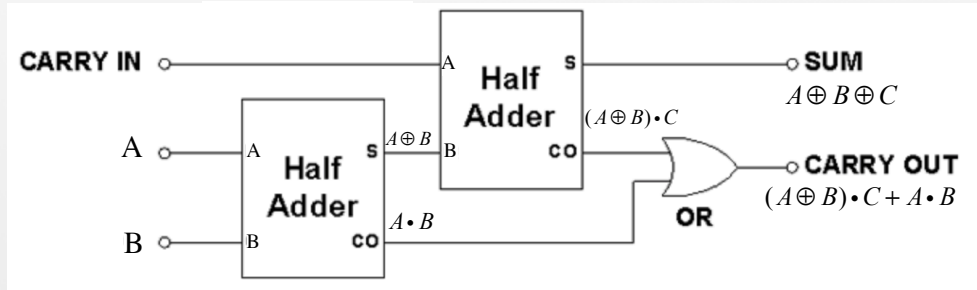 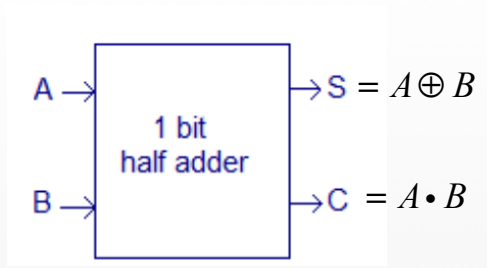

d) Parallel Addition

A	1	0	1	1
B	1	1	1	0

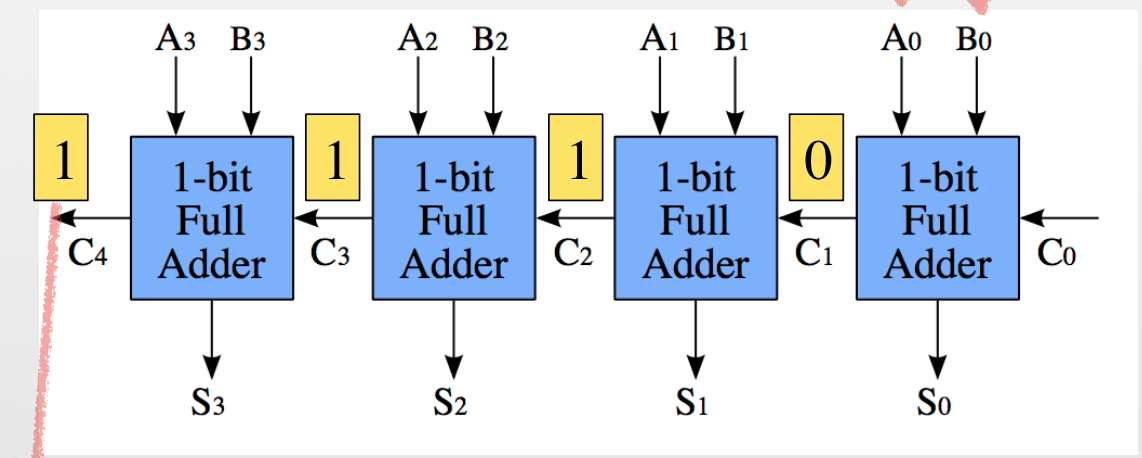

SUM	1	1	0	0	1
-----	---	---	---	---	---

8) *Digital Subtraction*

Two possible methods:

- 1) 1/2 subtractor and full subtractor (with borrow)
- ✓ 2) using 2's complement

a) Ones' complement: each bit is complemented

$$\text{e.g. } X = 1011 \rightarrow X_1 = 0100$$

$$\text{Note: } X + X_1 = 1111$$

b) Two's complement: add 1 to ones' complement

procedure: leave all right bits as is up to and including first 1,
and complement the rest

$$X_2 = X_1 + 1$$

$$\text{e.g. } X = 1011 \rightarrow X_1 = 0100 \rightarrow X_2 = 0101$$

$$\text{Since } X + X_1 = 1111, \quad X + \underbrace{X_1 + 1}_{X_2} = 10000 = 10^4 \text{ (or } 2^4 \text{ in decimal)}$$

So,

$$X^2 = 2^N - X$$

where N is the number of bits

c) Two's complement as negative

$$\text{Recall } X_2 = 2^N - X$$

$$\rightarrow X_2 + X = 2^N$$

$$\rightarrow X_2 + X = 0 \text{ (ignoring the carry, or considering only } N \text{ bits)}$$

$$\rightarrow X_2 = -X \text{ or } X = -X_2$$

$$\text{So, } Y - X = Y + (-X) = Y + X_2$$

i.e. subtract X by adding X_2

(and ignore the carry)

Problem: if $X > Y$, how to recognize negative value?

d) Subtraction using 2's complement

$$X_2 = 2^N - X \quad \rightarrow \quad X = 2^N - X_2$$

$$Y - X = Y - (2^N - X_2)$$

$$= (Y + X_2) - 2^N$$

$$= -[2^N - (Y + X_2)]$$

$$= -(Y + X_2)_2 \quad ??$$

but 2^N has no representation in N bits,
and Z_2 is not defined if $Z > 2^N$

$$Y - X$$

$$= (Y + X_2) - 2^N$$

$$= -(Y + X_2)_2 \quad ??$$

but 2^N has no representation in N bits,
and Z_2 is not defined if $Z > 2^N$

Consider 3-bit numbers ($N = 3$)

e.g. $Y = 3 = 011$; $X = 2 = 010$; $X_2 = 110 (=6)$

$$Y - X = (Y + X_2) - 2^N$$

$$3 - 2 = (3 + 6) - 8 = 1$$

$$\begin{array}{r} 011 - 010 = 011 \\ \underline{110} \\ (1)001 \end{array} \left. \vphantom{\begin{array}{r} 011 \\ 110 \\ (1)001 \end{array}} \right\} - 1000 = 1$$

For every $Y > X$, $Y + X_2 > 2^N$ so the carry is 1

→ If $Y > X$ (or if the carry is 1),

$$Y - X = Y + X_2$$

to 3 bits

(In this case, $(Y + X_2)_2$ is not defined)

$$Y - X$$

$$= (Y + X_2) - 2^N$$

$$= -(Y + X_2)_2 \quad ??$$

but 2^N has no representation in N bits,
and Z_2 is not defined if $Z > 2^N$

Consider 3-bit numbers ($N = 3$)

if the carry is 1

$Y - X = Y + X_2$ to 3 bits

e.g. $Y = 2 = 010$; $X = 3 = 011$; $X_2 = 101 (=5)$

$$Y - X = (Y + X_2) - 2^N$$

$$2 - 3 = (2 + 5) - 8 = -1$$

$$010 - 011 = 010$$

$$\begin{array}{r} 101 \\ \hline 111 \end{array}$$

} - 1000 = -1

$$- 1000 = -1$$

$$Y - X = -(Y + X_2)_2 \quad ??$$

$$010 - 011 = -(111)_2 = - (001)$$

For every $Y < X$, $Y + X_2 < 2^N \rightarrow$ carry is 0

\rightarrow If $Y < X$ (or if the carry is 0), $Y - X = -(Y + X_2)_2$

$Y - X$

$= Y + X_2$

if the carry is 1

$= -(Y + X_2)_2$

if the carry is 0

e) *Positive and Negative representation*

4-bit $\rightarrow 2^4 = 16$ numbers

0 to 15 (regular binary representation)

-8 to +7

-7 to +8

Options: 1) sign, magnitude: low 3 bits for magnitude, high bit for sign

\rightarrow subtraction has a conditional as above

2) 2's complement for negative

- high bit for sign (1 negative)

- positive: low 3 bits in binary

- negative: 4-bit 2's complement of absolute value

2) 2's complement for negative

- high bit for sign (1 negative)
- positive: low 3 bits in binary
- negative: 4-bit 2's complement of absolute value

x	X	sign-magnitude
7	0111	0111
6	0110	0110
5	0101	0101
4	0100	0100
3	0011	0011
2	0010	0010
1	0001	0001
0	0000	0000=1000
-1	1111	1001
-2	1110	1010
-3	1101	1011
-4	1100	1100
-5	1011	1101
-6	1010	1110
-7	1001	1111
-8	1000	

If $X = A_3A_2A_1A_0$ is a 4-bit representation of x , then

$$x = \begin{cases} X_b & \text{if } A_3 = 0 \\ -X_2 & \text{if } A_3 = 1 \end{cases}$$

Then,

$$y - x = Y + X_2 \quad \text{if } y > x$$

$$y - x = -(Y + X_2)_2 \quad \text{if } y < x$$

but

$$-(Y + X_2)_2 = Y + X_2$$

so

$$y - x = Y + X_2$$

without conditionals

x	X	sign-magnitude
7	0111	0111
6	0110	0110
5	0101	0101
4	0100	0100
3	0011	0011
2	0010	0010
1	0001	0001
0	0000	0000=1000
-1	1111	1001
-2	1110	1010
-3	1101	1011
-4	1100	1100
-5	1011	1101
-6	1010	1110
-7	1001	1111
-8	1000	

$$y - x = Y + X_2$$

$$3 - 2 = 1$$

$$0011 - 0010 = 0011$$

$$\begin{array}{r} 0011 \\ - 0010 \\ \hline 0001 \end{array} \left. \vphantom{\begin{array}{r} 0011 \\ - 0010 \\ \hline 0001 \end{array}} \right\} = 1$$

$$2 - 3 = -1$$



$$0010 - 0011 = 0010$$

$$\begin{array}{r} 0010 \\ - 0011 \\ \hline 1101 \end{array} \left. \vphantom{\begin{array}{r} 0010 \\ - 0011 \\ \hline 1101 \end{array}} \right\} = -1$$



9) Flip Flops

- 2 stable states for storing binary information

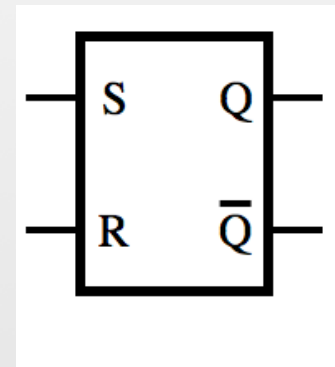 a) *SR flip flop (NOR), S-set; R-reset (SR latch)*




$$R = S = 0$$

  

2 possible states with $R = S = 0$


the state is “read” with $R = S = 0$

$S = 1, R = 0$

 


sets $Q = 1, \bar{Q} = 0$

$S = 0, R = 1$

 


(re)sets $Q = 0, \bar{Q} = 1$

$$S = 1, R = 1$$

 

 both outputs 0
indeterminate when R, S set to 0
not allowed (not used)





Truth table

S	R	Q	\bar{Q}
0	0	NC	NC
1	0	1	0
0	1	0	1
1	1	X	X



no change
(data storage)

not allowed;
indeterminate when
read with 0,0

b) SR NAND latch

  


$$R = S = 0; \bar{R} = \bar{S} = 1$$

  

2 possible states with $R = S = 0$


the state is “read” with $R = S = 0$
 
$$S = 1, R = 0; \bar{S} = 0, \bar{R} = 1$$




sets $Q = 1, \bar{Q} = 0$

$S = 0, R = 1; \bar{S} = 1, \bar{R} = 0$

 


(re)sets $Q = 0, \bar{Q} = 1$
 
$$S = 1, R = 1; \bar{S} = 0, \bar{R} = 0$$



 both outputs 1
indeterminate when R, S set to 0
not allowed




Truth table


S	R	\bar{S}	\bar{R}	Q	\bar{Q}
0	0	1	1	NC	NC
1	0	0	1	1	0
0	1	1	0	0	1
1	1	0	0	X	X

no change
(data storage)


 
not allowed;
indeterminate when
read with 0,0



S	R	\bar{S}	\bar{R}	Q	\bar{Q}
0	0	1	1	NC	NC
1	0	0	1	1	0
0	1	1	0	0	1
1	1	0	0	X	X

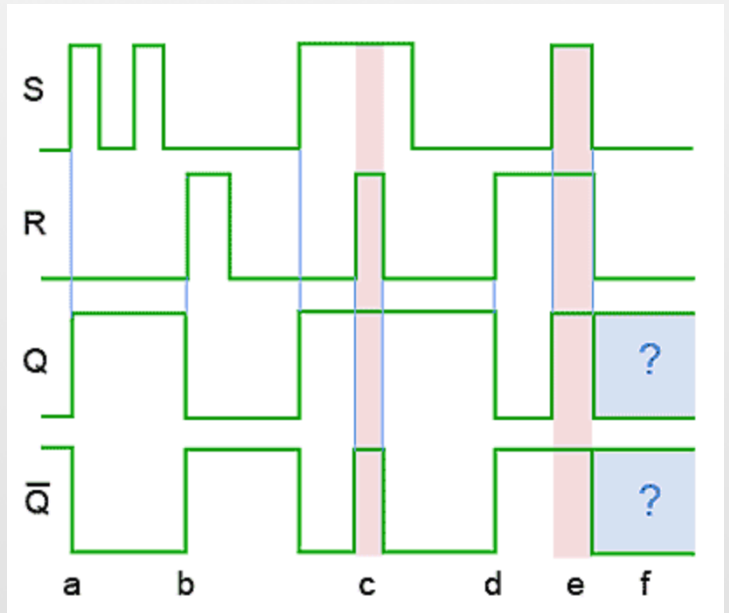


c) Clocked (or gated) SR latch


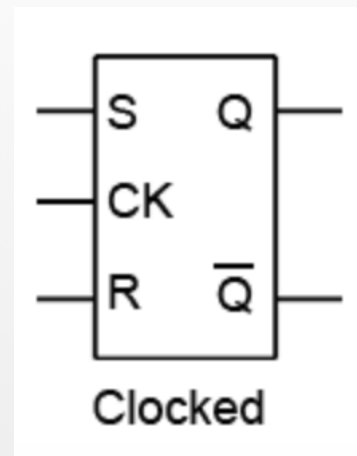
 


Clock must be present (high) to enable R and S

Gated SR latch operation	
E/C	Action
0	No action (keep state)
1	The same as non-clocked SR latch

 

d) D flip-flop (data latch)

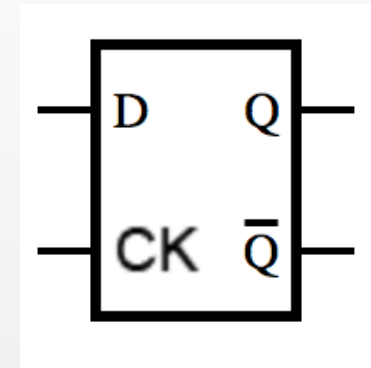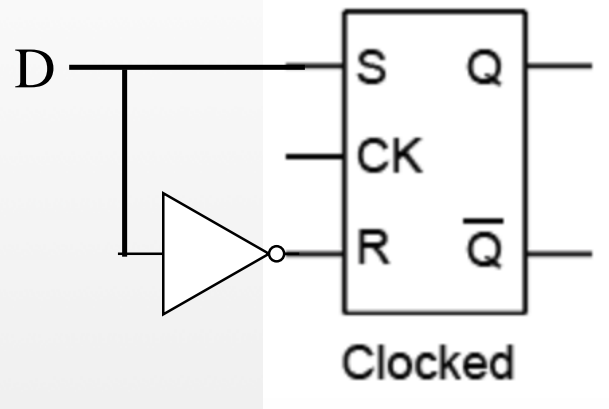 

Stores state of D at last clock high.

Gated D latch truth table

E/C	D	Q	\bar{Q}	Comment
0	X	Q_{prev}	\bar{Q}_{prev}	No change
1	0	0	1	Reset
1	1	1	0	Set