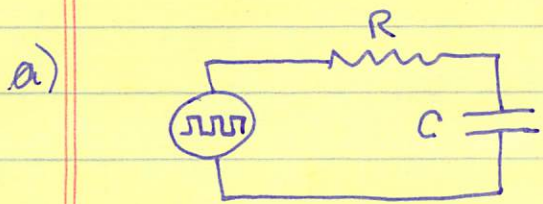


Phys2610 (2019) Prelab exercises for experiment 2

Pre-Lab exercises:


- a) Find the time constant for nominal component values $R = 10 \text{ k}\Omega$, $C = 0.03 \text{ }\mu\text{F}$. What approximate frequency setting f on the function generator would allow for 10 “time constants” of the RC response time to be observed before switching to the opposite polarity of the waveform?
- b) Find the potential difference across the capacitor and resistor as a function of time, for both transitions of the square wave, and check that your solutions satisfy Kirchhoff’s loop theorem.
- c) Draw a sketch of the expected waveforms for the EMF supplied by the function generator, the potential difference across the resistor, and the potential difference across the capacitor, for a frequency such that each half-cycle corresponds to 4 time constants of the RC circuit. Include at least one full cycle of the square waveform. Draw your diagrams to scale.
- d) For the high to low transition, show that the waveform can be simply expressed as $v_C'(t) = v_C'(0)e^{-\frac{t}{RC}}$ where $t = 0$ represents the start of the cycle, and $v_C' = 0$ for $t \rightarrow \infty$. What is the value of $v_C'(0)$ in terms of V_0 ? A graph of $\ln\left(\frac{v_C'(t)}{v_C'(0)}\right)$ vs t should be a straight line with slope $(-1/RC)$. Note the prime here simply represents another variable, not a derivative.
- e) Watch the introductory videos linked to the course web page for this experiment !!!**

Phys 2610 (2019) Pre-lab exercises 2 solutions



For $R = 10\text{k}\Omega$, $C = 0.03\mu\text{F}$,
 $\tau = RC = 3 \times 10^{-4}\text{ s} = \boxed{0.30\text{ ms}}$

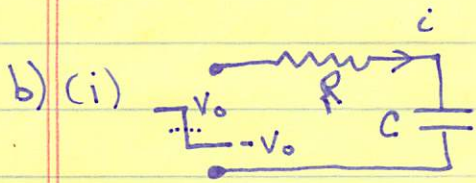For $T = 20\tau$ (i.e. $T/2 = 10\tau$), $f = \frac{1}{T} = \boxed{167\text{ Hz}}$



$i = dq/dt$

loop rule (after transition): $-V_0 - iR - q/C = 0 \rightarrow \underline{\underline{\frac{dq}{dt} + \frac{q}{RC} = -\frac{V_0}{R}}}$

Solution: $q = A e^{-t/RC} - V_0 C$

For $t=0$, $q = V_0 C$, so $A = 2V_0 C$, giving

$q = C V_0 (2 e^{-t/RC} - 1)$, so that

$\underline{\underline{V_C = \frac{q}{C} = V_0 (2 e^{-t/RC} - 1)}}$


and $V_R = iR = \frac{dq}{dt} R$
 $= R (2V_0 C / RC e^{-t/RC})$

or

$\underline{\underline{V_R = -2V_0 e^{-t/RC}}}$

$\therefore V_R + V_C = -V_0$, satisfying K.L.

(2)

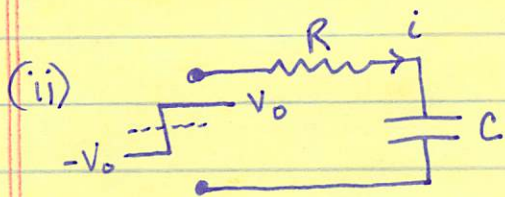

$$i = dq/dt$$

$$\text{Here } V_0 - iR - q/c = 0 \Rightarrow \underline{\underline{\frac{dq}{dt} + \frac{q}{RC} = \frac{V_0}{R}}}$$



$$\text{Solution: } q = A e^{-t/RC} + V_0 C$$

5 For $t=0$, $q = -V_0 C$, so $A = -2V_0 C$, giving

$$q = C V_0 (1 - 2e^{-t/RC}), \text{ so that}$$


$$\boxed{V_C = \frac{q}{C} = V_0 (1 - 2e^{-t/RC})} \text{ and } \boxed{V_R = iR = 2V_0 e^{-t/RC}}$$

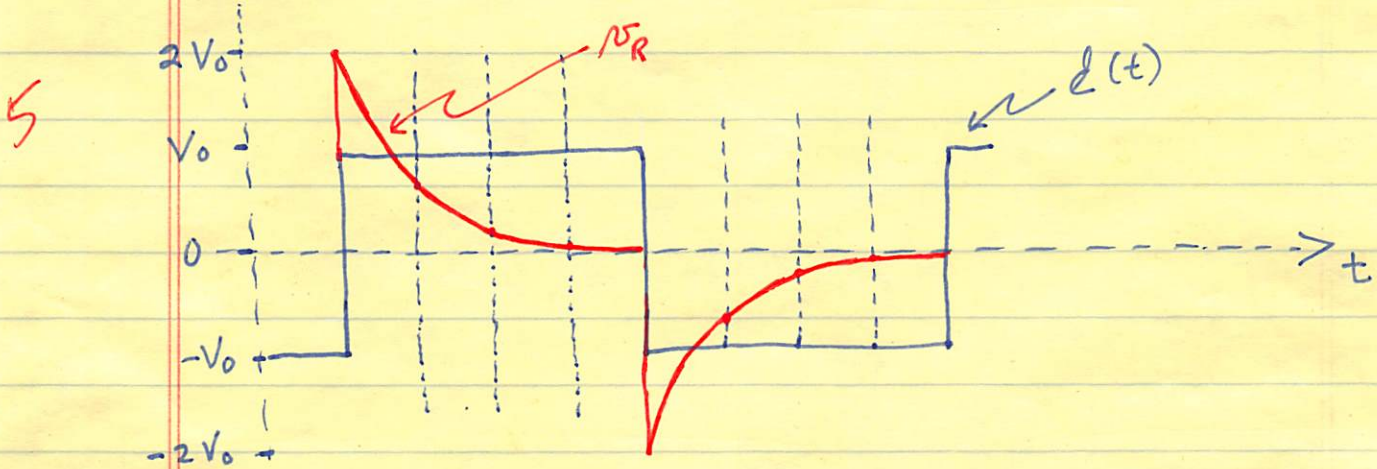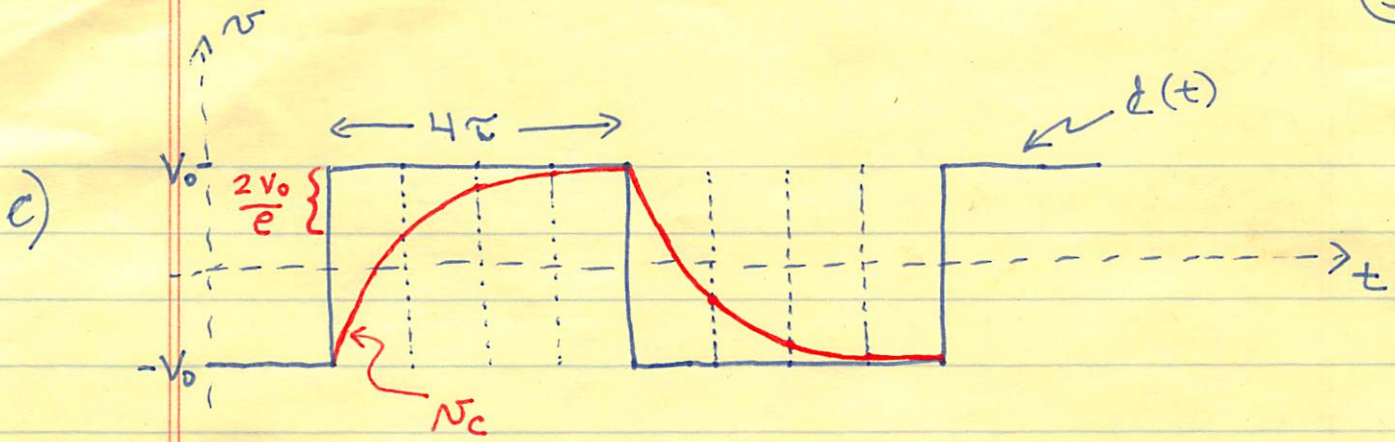$\therefore V_C + V_R = +V_0$ satisfying K.L.




d) Consider $v' = v_c + V_0 = 2V_0 e^{-t/RC}$

Then $v'(0) = 2V_0$ and $v'(\infty) = 0$

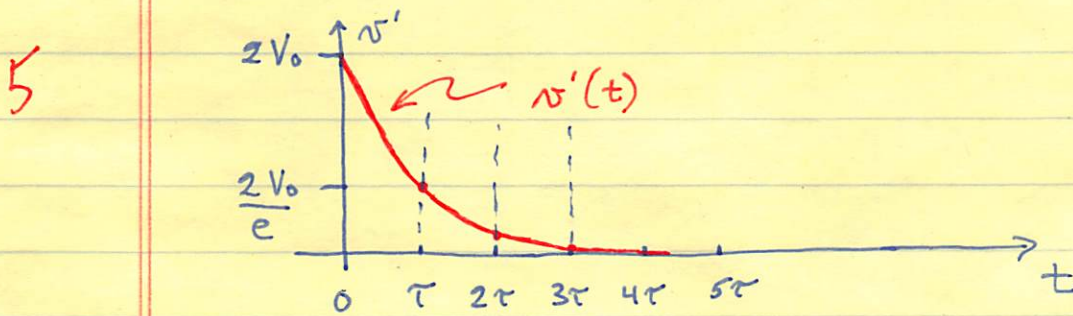

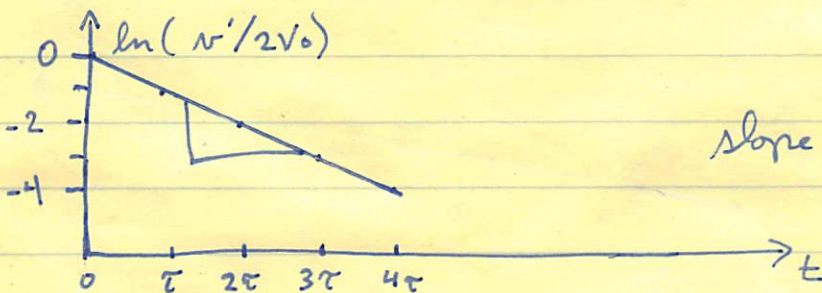Also $\ln v' = \ln(2V_0) - t/RC \rightarrow \ln\left(\frac{v'}{2V_0}\right) = -t/RC$



slope = $-1/RC$

25