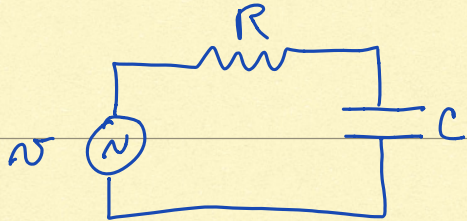


Phys 2610 (2019) Prelab 3 solutions

Pre-Lab exercises:

a) Working with the complex waveforms $\tilde{v}(t) = V_0 e^{j\omega t}$, $v(t) = \text{Re}(\tilde{v})$, use the complex impedance formalism to show that the current in the circuit is given by:

$$i(t) = \frac{V}{\sqrt{R^2 + (1/\omega C)^2}} \cos(\omega t - \theta), \text{ where } \tan \theta = -1/\omega RC.$$



$$\tilde{v} = V_0 e^{j\omega t}$$

The complex impedance is

$$\tilde{z} = R - \frac{j}{\omega C} = |Z| e^{j\theta} \quad \text{where } \tan \theta = -1/\omega RC$$

and $|Z| = \sqrt{R^2 + (1/\omega C)^2}$

Then the (complex) current is

$$\tilde{i} = \frac{\tilde{v}}{\tilde{z}} = \frac{V_0 e^{j\omega t}}{|Z| e^{j\theta}} = \frac{V_0}{|Z|} e^{j(\omega t - \theta)}$$

and the real part is

$$i = \frac{V_0}{\sqrt{R^2 + (1/\omega C)^2}} \cos(\omega t - \theta)$$

$$\text{with } \theta = -\arctan(1/\omega RC)$$

b) Based on the solution to part a), find expressions for the potential differences across the resistor, $v_R(t) = V_R \cos(\omega t + \alpha)$, and capacitor, $v_C(t) = V_C \cos(\omega t + \beta)$, showing the phases (α and β) with respect to the input voltage. The capacitor values will be examined in this experiment.

Resistor Voltage: $\tilde{V}_R = iR = \frac{V_0 R}{Z} \cos(\omega t - \theta)$

so $\tilde{V}_R = V_R \cos(\omega t + \alpha)$ with $\alpha = -\theta = -\arctan(-1/\omega RC)$
 $= \arctan(1/\omega RC)$

and $V_R = \frac{V_0 R}{|Z|} = \frac{V_0}{\sqrt{1 + (1/\omega RC)^2}}$

Capacitor Voltage: $\tilde{V}_C = \tilde{i} \tilde{z}_C$

Using $\tilde{i} = \frac{V_0}{|Z|} e^{j(\omega t - \theta)}$ and $\tilde{z}_C = 1/j\omega C = (1/\omega C) e^{-j\pi/2}$ gives:

$\tilde{V}_C = \frac{V_0}{\omega C |Z|} e^{j(\omega t - \theta - \pi/2)}$

$\rightarrow V_C = V_C \cos(\omega t + \beta)$ with $\beta = -\theta - \pi/2 = \arctan(1/\omega RC) - \pi/2$

and $V_C = \frac{V_0}{\omega C |Z|} = \frac{V_0}{\sqrt{1 + (\omega RC)^2}}$

or

Using the voltage divider eq'n $\tilde{V}_C = \tilde{V} \frac{\tilde{z}_C}{R + \tilde{z}_C}$:

$\tilde{V}_C = \frac{V_0 e^{j\omega t}}{j\omega C (R + 1/j\omega C)} = \frac{V_0 e^{j\omega t}}{(1 + j\omega RC)} = \frac{V_0 e^{j\omega t}}{\sqrt{1 + (\omega RC)^2}} e^{j\phi} = \frac{V_0 e^{j(\omega t - \phi)}}{\sqrt{1 + (\omega RC)^2}}$

where $\tan \phi = \omega RC$

Then, $V_C = V_C \cos(\omega t + \beta)$ with $\beta = -\phi = -\arctan(\omega RC)$

and $V_C = V_0 / \sqrt{1 + (\omega RC)^2}$



(Note: $\arctan(1/x) - \pi/2 = -\arctan x$)

c) Organize your results in a table:



Element:	Amplitude	Phase relative to $v(t)$
Resistor	$V_R = V_0 / \sqrt{1 + (1/\omega RC)^2}$	$\alpha = \arctan(1/\omega RC)$
Capacitor	$V_C = V_0 / \sqrt{1 + (\omega RC)^2}$	$\beta = -\arctan(\omega RC)$



d) Sketch graphs of the amplitude and phase relations for the capacitor and resistor as functions of frequency.

Resistor:

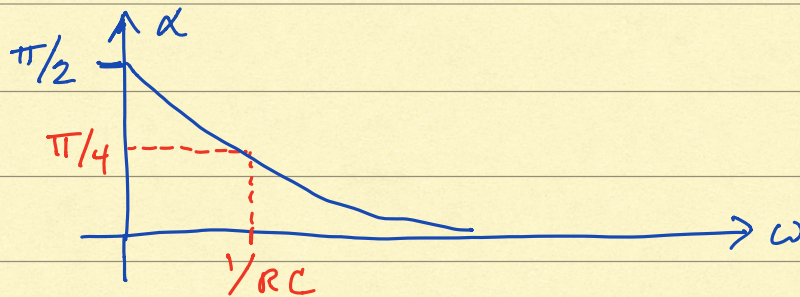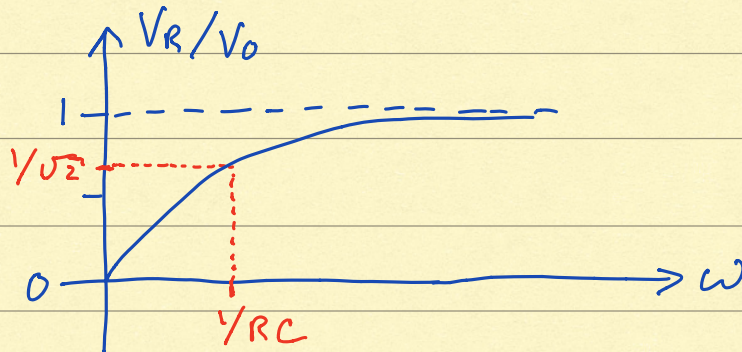

Capacitor

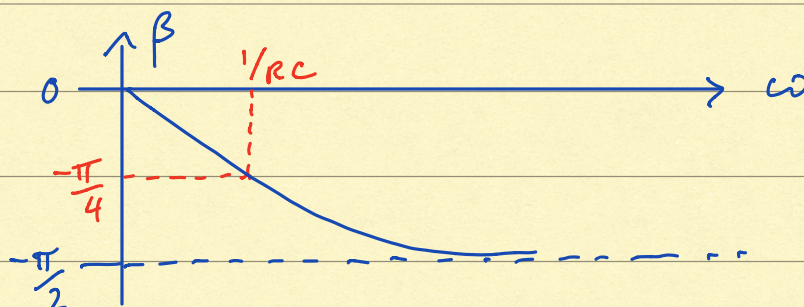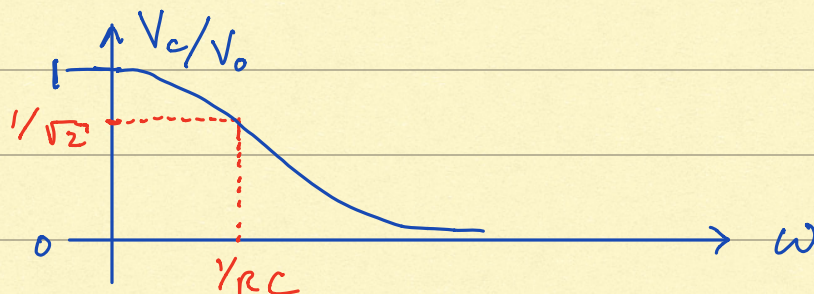

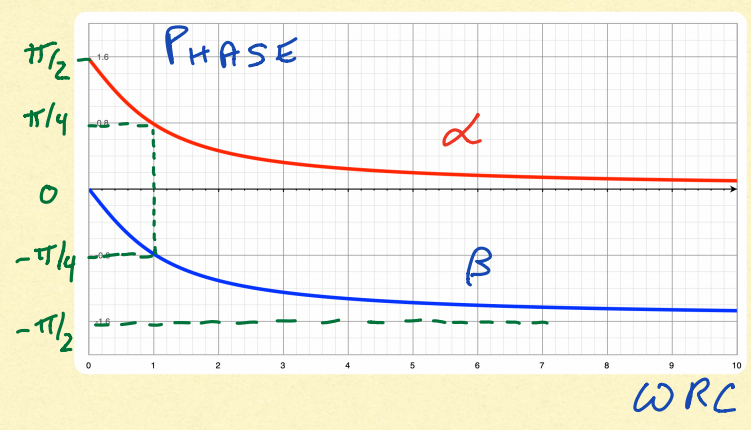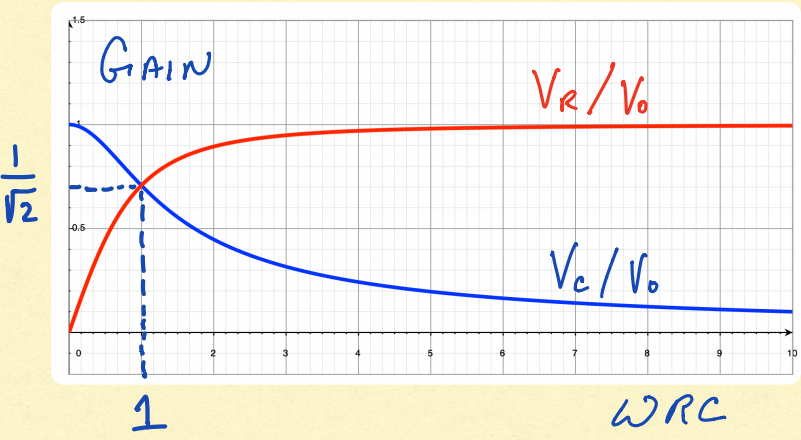

LOG SCALES:

