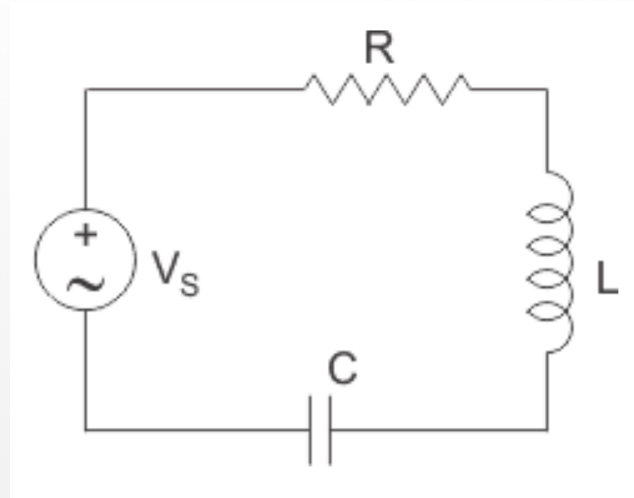


7) Resonance LRC circuit

$$z = R + j\left(\omega L - \frac{1}{\omega C}\right) = |Z|e^{j\theta}$$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \quad \tan\theta = \frac{\omega L - \frac{1}{\omega C}}{R}$$



Using $v = iz$, if

$$v = Ve^{j\omega t}$$

then

$$i = Ie^{j(\omega t - \theta)}$$

with $I = \frac{V}{|Z|}$

$$i = Ie^{j(\omega t - \theta)}$$

$$I = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$\tan \theta = \frac{\omega L - \frac{1}{\omega C}}{R}$$

(a) Resonance

For $\omega \rightarrow \infty$, $|Z| \rightarrow \infty$, $i \rightarrow 0$, $\theta \rightarrow \pi / 2$
 $\omega \rightarrow 0$, $|Z| \rightarrow \infty$, $i \rightarrow 0$, $\theta \rightarrow -\pi / 2$

current approaches zero at high and low frequencies

Maximum occurs when $\omega L = \frac{1}{\omega C}$

frequency dependent terms cancel

Then, $\theta \rightarrow 0$, $|Z| \rightarrow R$, $z \rightarrow R$, so $i = \frac{v}{R}$

i.e. the circuit is purely resistive
 — the effect of L and C cancel

Resonance frequency: $\omega_0 L = \frac{1}{\omega_0 C} \rightarrow \omega_0^2 = \frac{1}{LC}$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$I = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$\tan \theta = \frac{\omega L - \frac{1}{\omega C}}{R}$$

$$\omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\rightarrow I(\omega_0) = I_{\max} = \frac{V}{R}$$


$$\rightarrow \frac{I}{I_{\max}} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)^2}}$$

$$L = 250 \text{ mH}$$

$$C = 0.1 \mu\text{F}$$

$$R = 100 \Omega$$
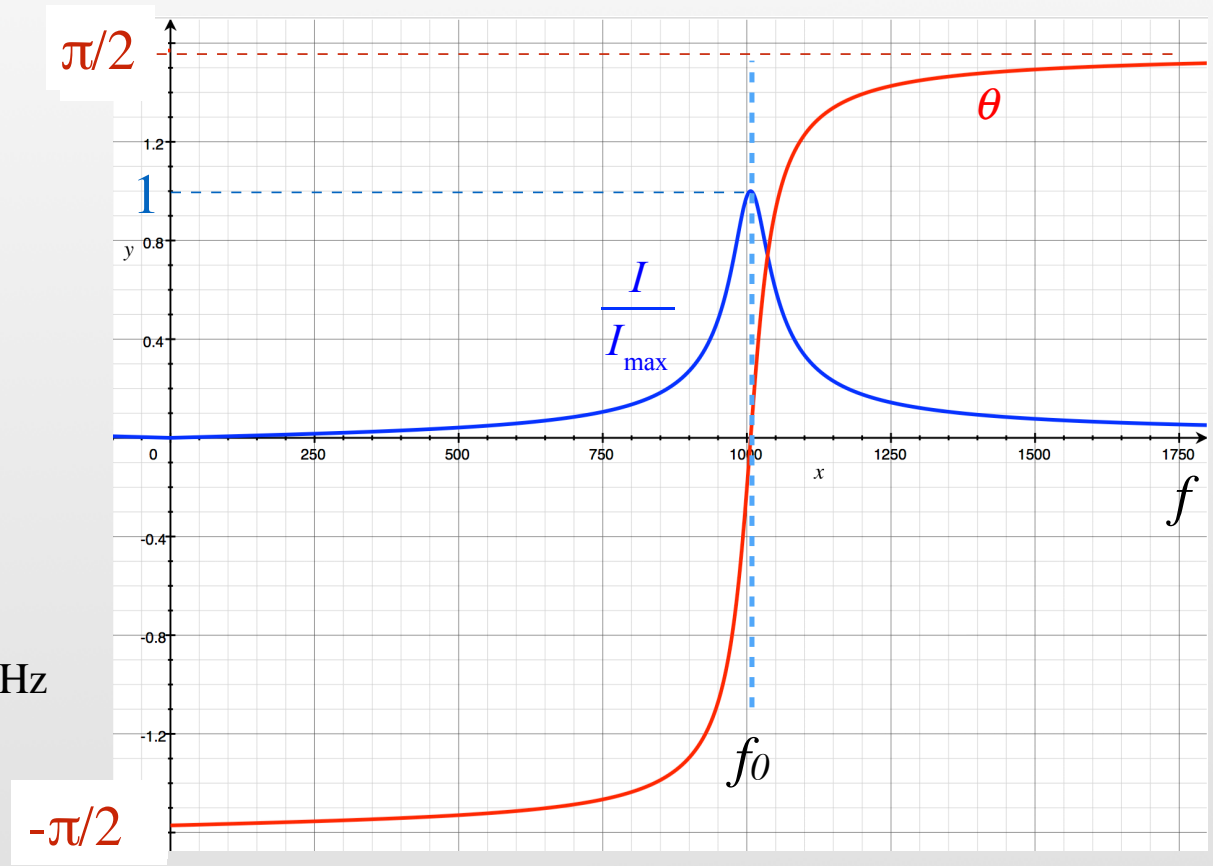
$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}} = 1000 \text{ Hz}$$



(b) Resistor voltage

$$v_R = V_R e^{j(\omega t - \theta)} = \frac{V_R}{|Z|} e^{j(\omega t - \theta)}$$

$$v_R = iR \quad \longrightarrow \quad V_R = IR \quad \longrightarrow \quad V_{R\max} = I_{\max} R$$

$$\longrightarrow \quad \frac{V_R}{V_{R\max}} = \frac{I}{I_{\max}}$$

e.g.

$$R = 100\Omega$$

$$C = 0.1\mu\text{F}$$

$$L = 250\text{ mH}$$


$$V = 10\text{ V}$$

Resonant freq:

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}} = 1006.6\text{ Hz}$$

$$I_{\max} = \frac{V}{R} = 0.10\text{ A}$$

$$V_{R\max} = I_{\max} R = 10\text{ V}$$

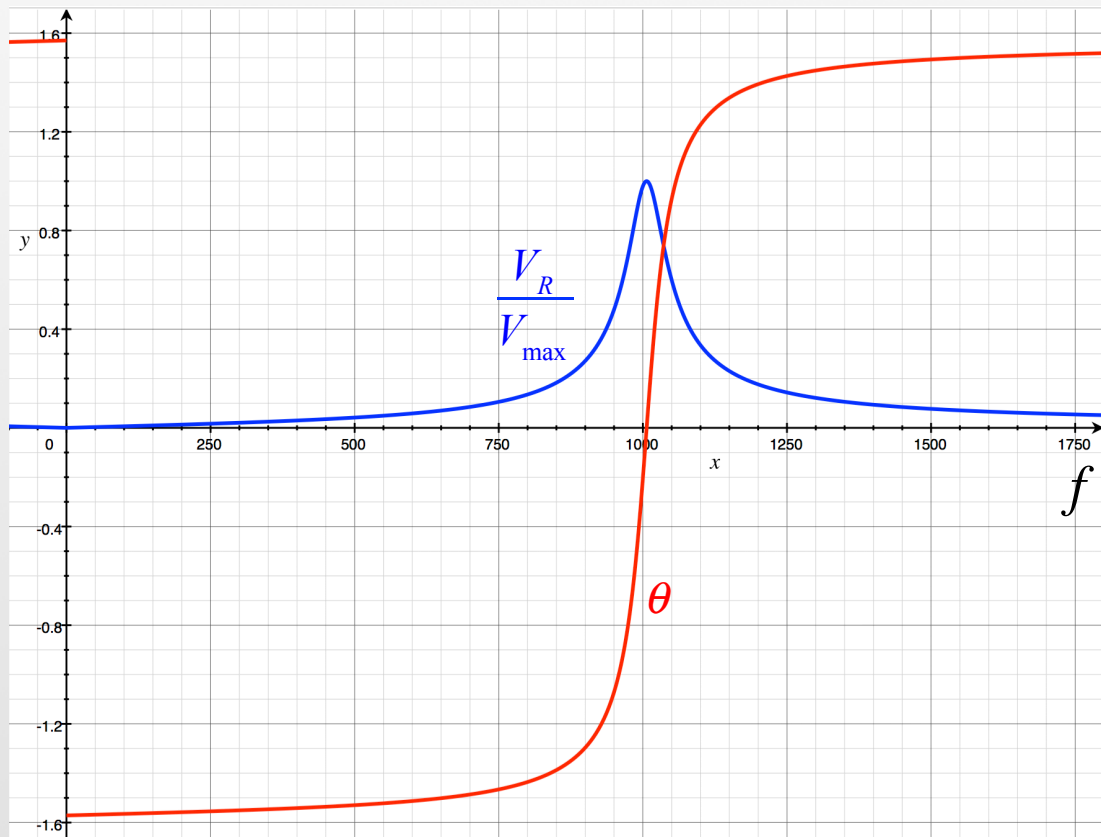


(c) Q-factor

- shape depends on the component values, R in particular
- R cannot be removed (because of L)
- sharper is better for resonance circuit \implies higher Q

$$Q \equiv \frac{\omega_0}{\Delta\omega} \quad (\text{“resolution” in spectroscopy})$$


$\Delta\omega$ is the width at 1/2 power, or $1/\sqrt{2}$ amplitude
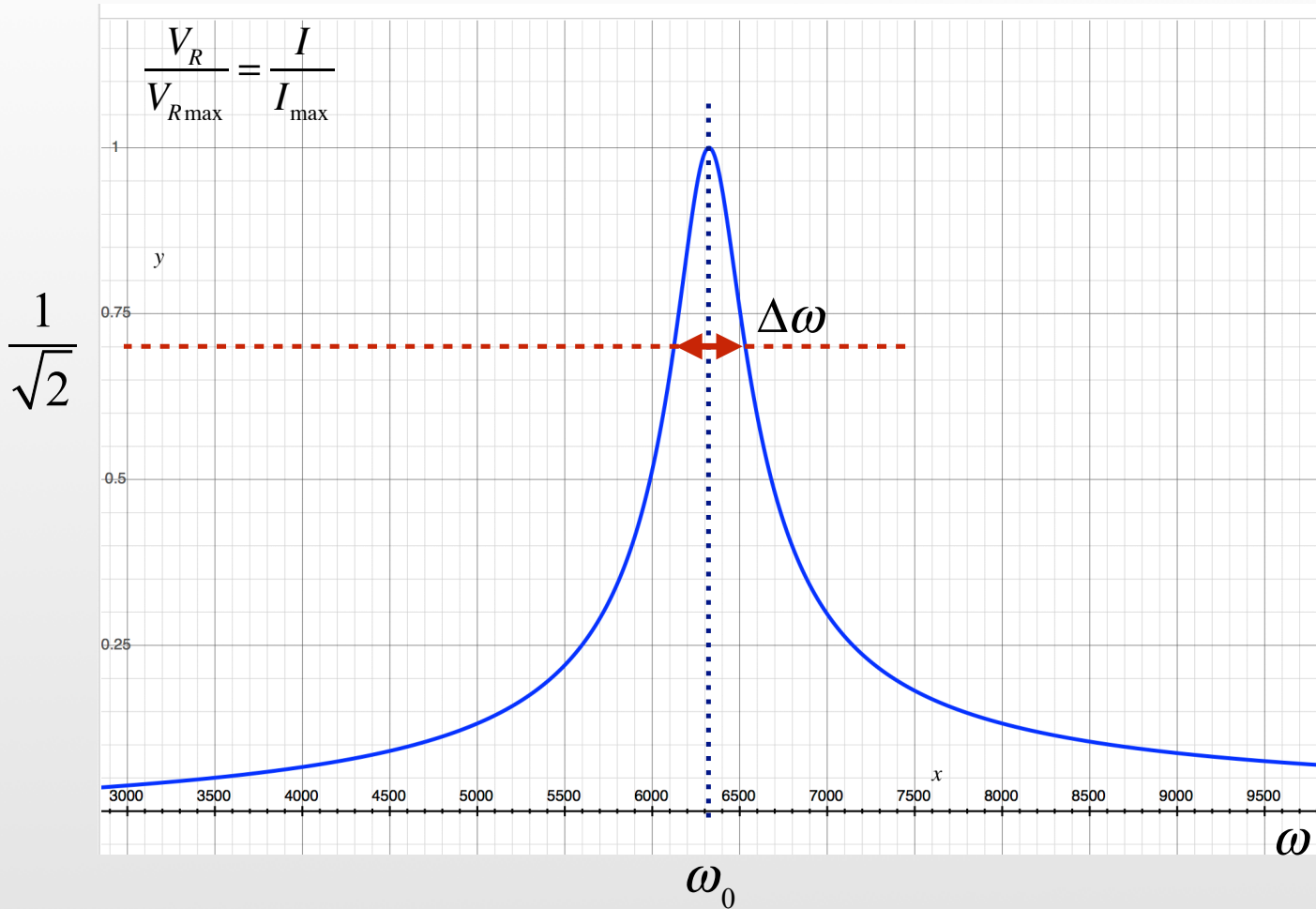
$$Q = \frac{\omega_0}{\Delta\omega} \quad \Delta\omega \text{ is the width at 1/2 power, or } 1/\sqrt{2} \text{ amplitude}$$



To find $Q(R,L,C)$, find frequencies where
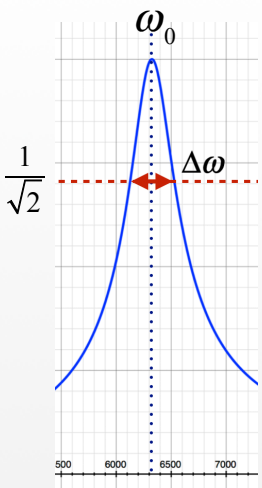
$$\frac{V_R}{V_{R\max}} = \frac{I}{I_{\max}} = \frac{1}{\sqrt{2}}$$



Recall
$$\frac{I}{I_{\max}} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)^2}}$$

so,
$$\frac{I}{I_{\max}} = \frac{1}{\sqrt{2}}$$

when
$$\left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right) = 1$$

$$\frac{\omega L}{R} \left(1 - \frac{1}{\omega^2 LC}\right) = 1 \quad \times \omega^2$$

$$\left(1 - \frac{1}{\omega^2 / \omega_0^2}\right) = \frac{R}{\omega L}$$

$$(\omega^2 - \omega_0^2) = \frac{R\omega}{L}$$

$$\underbrace{(\omega - \omega_0)}_{\frac{\Delta\omega}{2}} \underbrace{(\omega + \omega_0)}_{2\omega} = \frac{R\omega}{L}$$

For $\omega \gg \Delta\omega$, $\omega \cong \omega_0$, $\omega + \omega_0 \cong 2\omega_0$

$$\rightarrow \Delta\omega \cong \frac{R}{L} \quad \rightarrow Q = \frac{\omega_0}{\Delta\omega} = \frac{\omega_0 L}{R}$$

$$\rightarrow Q = \frac{\sqrt{L/C}}{R}$$


$$Q = \frac{\omega_0}{\Delta\omega}$$



$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\frac{1}{\sqrt{2}}$$

L = 250 mH
C = 0.1 μ F
R = 100 Ω

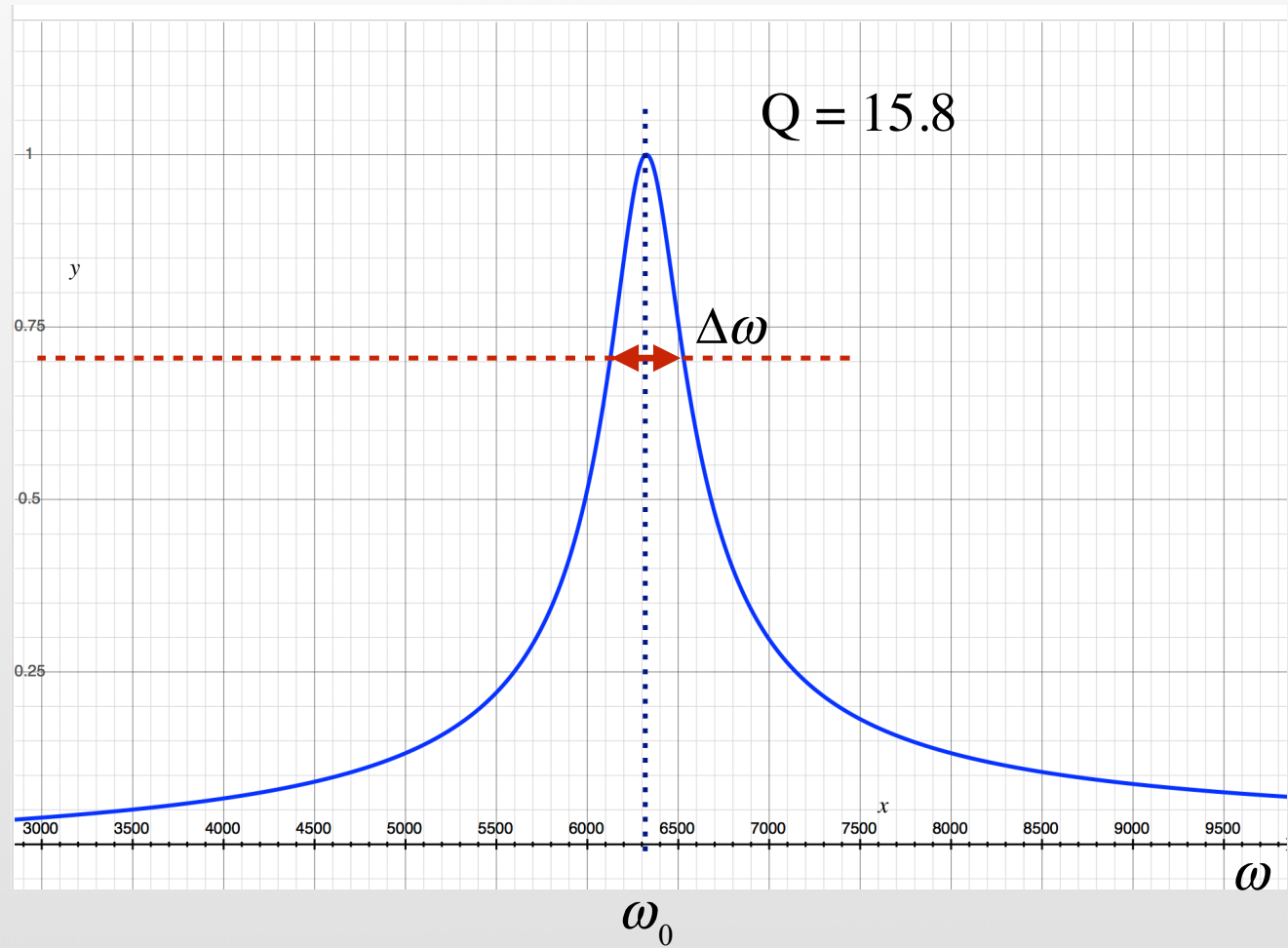

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

smaller R , higher Q , sharper peak

$L = 250 \text{ mH}$


$C = 0.1 \mu\text{F}$

$R = 1000 \Omega$

$R = 100 \Omega$

$R = 10 \Omega$

$R = 1 \Omega$

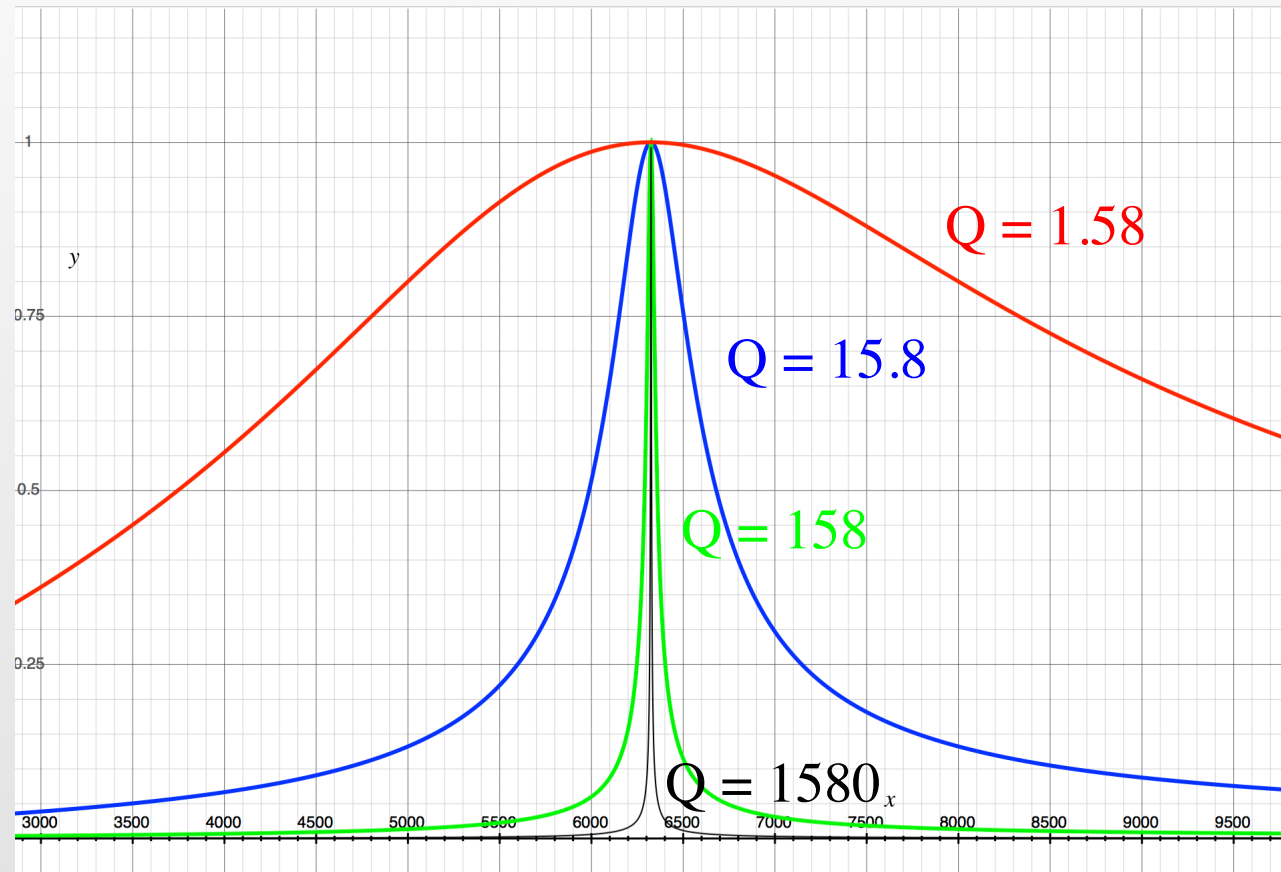

(d) Capacitor voltage

Peak Value (numerically):

$$V_{c \max} = I_{\max} X_C = \frac{I_{\max}}{\omega_0 C} = \frac{0.10 \text{ A}}{2\pi(1000 \text{ Hz})(0.1 \mu\text{F})} = 158 \text{ V}$$

function of time:

$$v_C = iz_C = \frac{v}{z} z_C = \frac{v}{j\omega C z}$$

but $z = |Z|e^{j\theta}$, $j\omega C = \omega C e^{j\pi/2}$

so
$$v_C = \frac{V e^{j\omega t}}{\omega C |Z| e^{j(\theta + \pi/2)}}$$

$$v_C = \frac{V}{\omega C |Z|} e^{j(\omega t - \theta - \pi/2)}$$

$\underbrace{\hspace{1.5cm}}_{\beta}$

$$v_c = \frac{V}{\omega C |Z|} e^{j(\omega t - \theta - \pi/2)}$$

$\underbrace{\hspace{10em}}_{\beta}$

Amplitude:

$$V_c = \frac{V}{\omega C |Z|} = \frac{V}{\sqrt{(\omega RC)^2 + (1 - \omega^2 LC)^2}}$$


At resonance, $\frac{V_c}{V} = \frac{1}{\omega_0 RC} = \frac{1}{R} \sqrt{\frac{L}{C}} = Q$

$$v_C = \frac{V}{\omega C |Z|} e^{j(\omega t - \underbrace{\theta - \pi/2}_{\beta})}$$

$$\tan \theta = \frac{\omega L - \frac{1}{\omega C}}{R}$$

Phase:

$$\beta = -\theta - \pi / 2$$

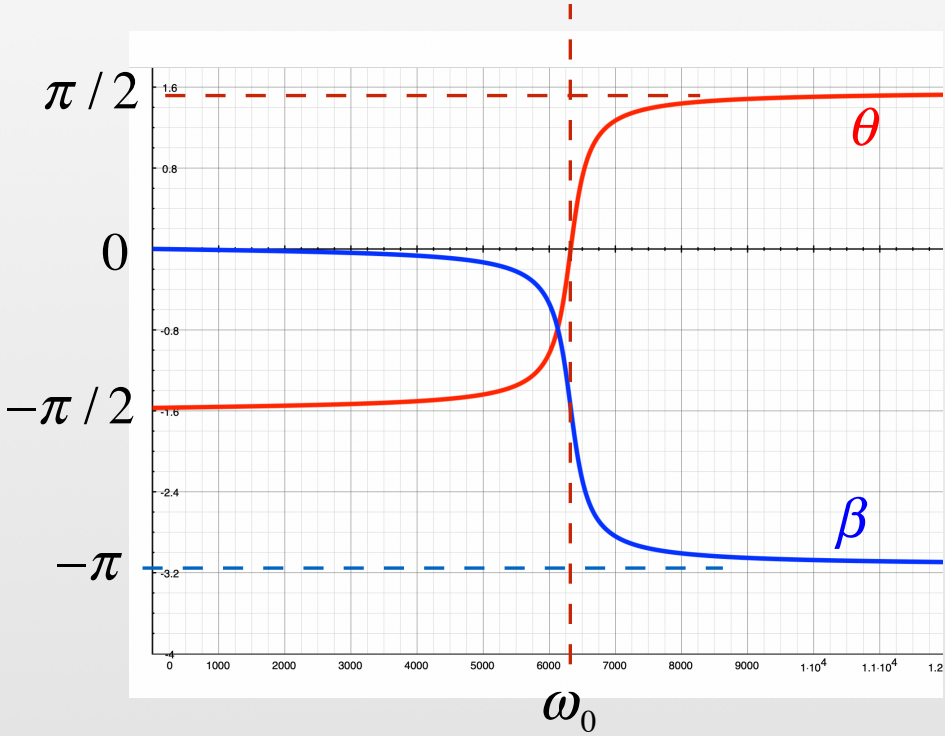


$$v_C = \frac{V}{\omega C |Z|} e^{j(\omega t - \theta - \pi/2)}$$

$$\tan \theta = \frac{\omega L - \frac{1}{\omega C}}{R}$$


Capacitor resonance:

Recall, for the resistor, $v_R = \frac{V}{|Z|} e^{j(\omega t - \theta)}$ has max amplitude when $\frac{1}{|Z|}$ is max

Similarly, v_C has max amplitude when $\frac{1}{\omega C |Z|}$ is max

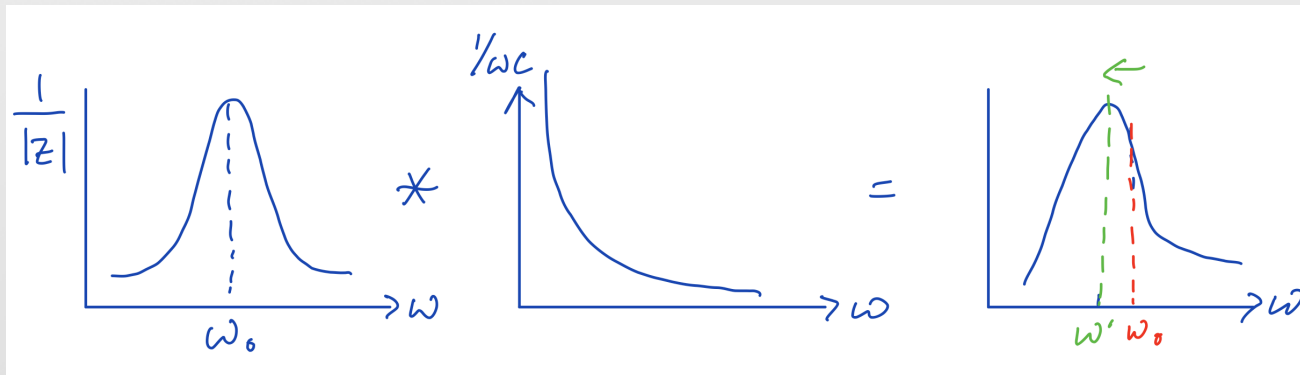

Similarly, v_C has max amplitude when $\frac{1}{\omega C |Z|}$ is max

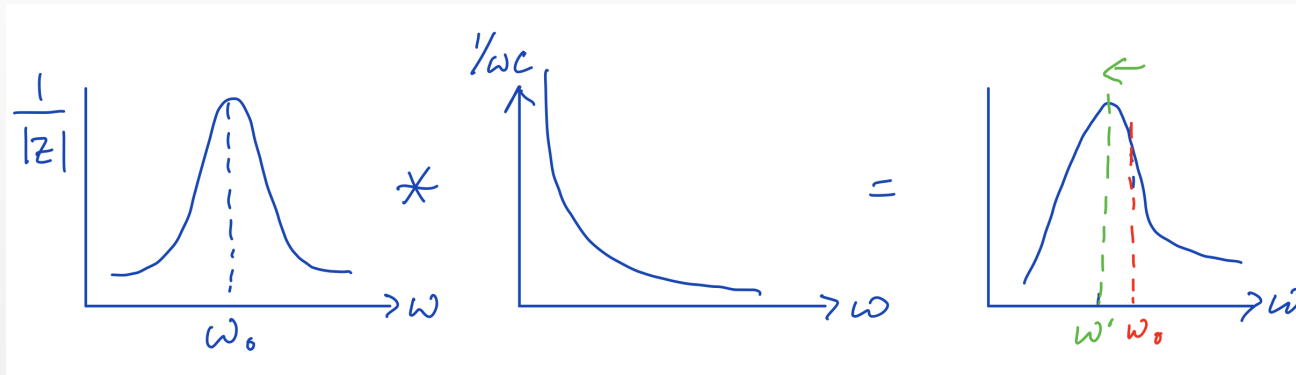

To find ω' , set $\frac{d}{d\omega} \frac{1}{\omega C |Z|} = 0 \Rightarrow \omega'^2 = \omega_0^2 - \frac{R^2}{2L^2}$

e.g.

$R = 100\Omega$
 $C = 0.1\mu\text{F}$
 $L = 250\text{ mH}$
 $V = 10\text{ V}$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}} = 1006.6\text{ Hz}$$

$$f' = \frac{\omega'}{2\pi} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}} = 1005.6\text{ Hz}$$

(e) Inductor voltage

Peak Value (numerically):

$$V_{L\max} = I_{\max} X_L = \omega_0 L I_{\max} = 2\pi(1000\text{Hz})(250\text{mH})(0.10\text{A}) = 158 \text{ V}$$

function of time:

$$v_L = iz_L = \frac{v}{z} j\omega L \quad \text{but} \quad z = |Z|e^{j\theta}, \quad j\omega L = \omega L e^{j\pi/2}$$

$$\text{so} \quad v_L = V e^{i\omega t} \frac{\omega L}{|Z|} e^{j(-\theta+\pi/2)}$$

$$v_L = \frac{V}{|Z| / (\omega L)} e^{j(\omega t - \theta + \pi/2)}$$

$\underbrace{\hspace{10em}}_{\alpha}$

$$v_L = \frac{V}{|Z| / (\omega L)} e^{j(\omega t - \theta + \pi/2)}$$

$\underbrace{\hspace{10em}}_{\alpha}$

Amplitude:

$$V_L = \frac{V}{|Z| / (\omega L)} = \frac{V}{\sqrt{\left(\frac{R}{\omega L}\right)^2 + \left(1 - \frac{1}{\omega^2 LC}\right)^2}}$$


At resonance, $\frac{V_L}{V} = \frac{\omega_0 L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}} = Q$

$$v_L = \frac{V}{|Z| / (\omega L)} e^{j(\omega t - \theta + \pi/2)}$$

$\underbrace{\hspace{10em}}_{\alpha}$

$$\tan \theta = \frac{\omega L - \frac{1}{\omega C}}{R}$$

Phase: $\alpha = -\theta + \pi / 2$

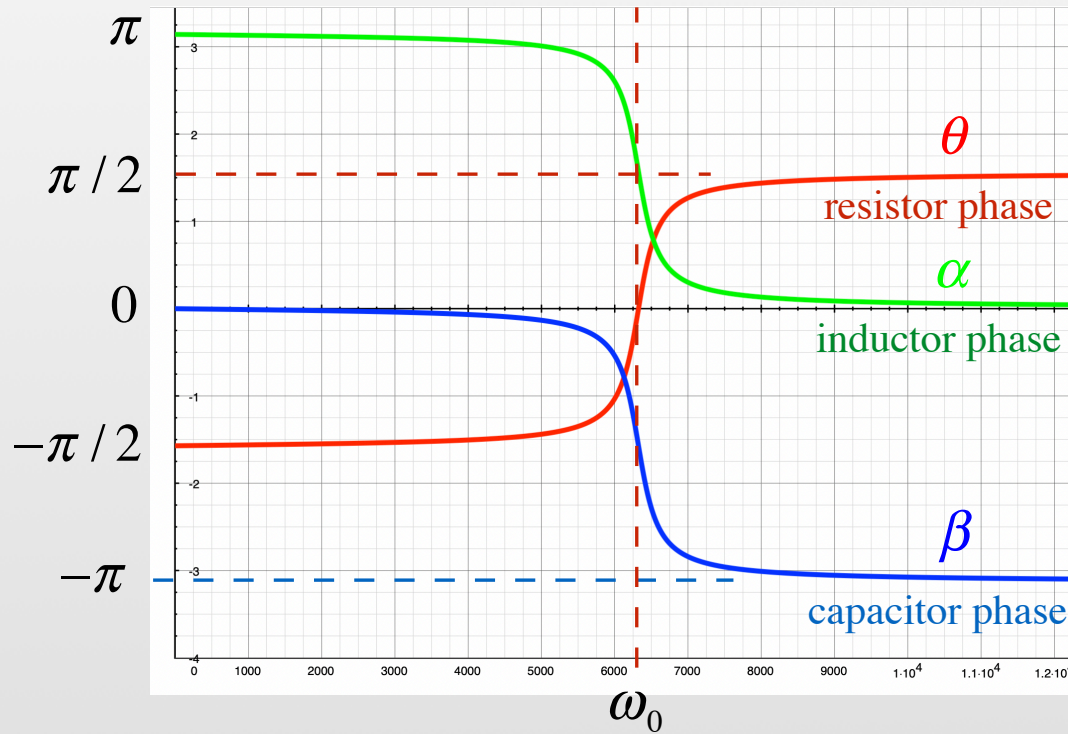

$$\alpha - \beta = \pi$$

capacitor and inductor voltage always 180° out of phase

At resonance, the amplitudes are the same, so

$$v_C + v_L = 0$$


$$v_L = \frac{V}{|Z| / (\omega L)} e^{j(\omega t - \theta + \pi/2)}$$

$$\tan \theta = \frac{\omega L - \frac{1}{\omega C}}{R}$$


Inductor resonance:

Recall, for the resistor, $v_R = \frac{V}{|Z|} e^{j(\omega t - \theta)}$ has max amplitude when $\frac{1}{|Z|}$ is max

Similarly, v_L has max amplitude when $\frac{1}{|Z| / (\omega L)} = \frac{\omega L}{|Z|}$ is max

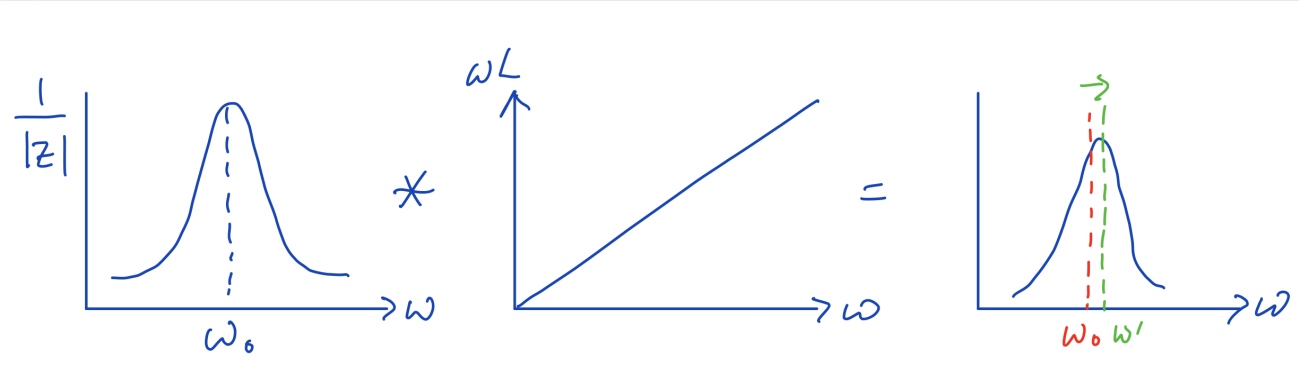

Similarly, v_L has max amplitude when $\frac{1}{|Z|/(\omega L)} = \frac{\omega L}{|Z|}$ is max

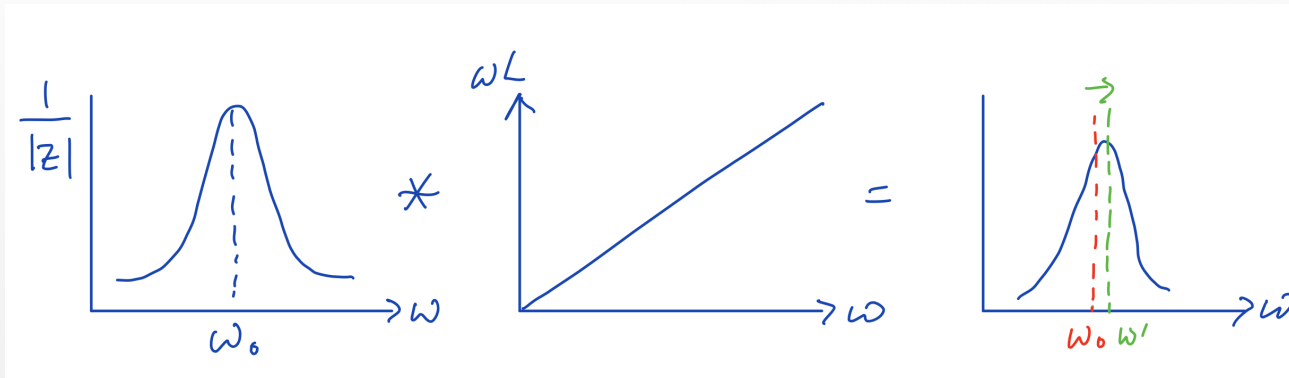

To find ω' , set $\frac{d}{d\omega} \frac{\omega L}{|Z|} = 0 \Rightarrow \omega' = \frac{1}{\sqrt{\frac{1}{\omega_0^2} - \frac{(RC)^2}{2}}}$

e.g.

$R = 100\Omega$

$C = 0.1\mu\text{F}$


$L = 250\text{ mH}$

$V = 10\text{ V}$

$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}} = 1006.6\text{ Hz}$

$f' = \frac{\omega'}{2\pi} = \frac{1}{2\pi} \frac{1}{\sqrt{\frac{1}{\omega_0^2} - \frac{(RC)^2}{2}}} = 1007.6\text{ Hz}$

$$v = Ve^{j\omega t}$$

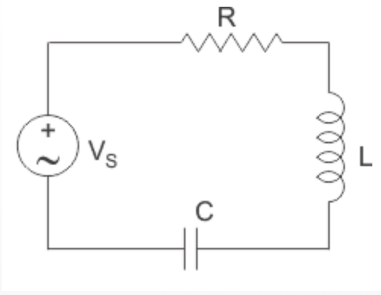


$$i = \frac{V}{|Z|} e^{j(\omega t - \theta)}$$


$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\tan \theta = \frac{\omega L - \frac{1}{\omega C}}{R}$$


$$v_R = \frac{VR}{|Z|} e^{j(\omega t - \theta)}$$

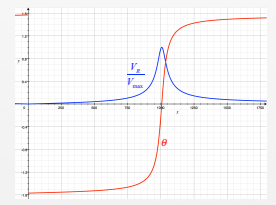

$$v_C = \frac{V}{\omega C |Z|} e^{j(\omega t - \theta - \pi/2)}$$

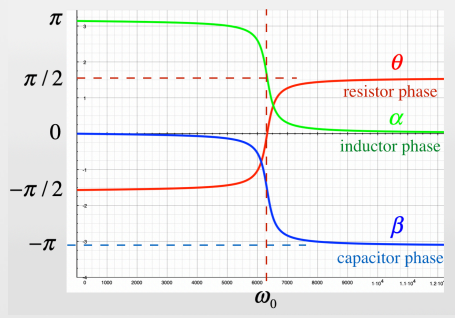


$$v_L = \frac{V}{|Z|} (\omega L) e^{j(\omega t - \theta + \pi/2)}$$

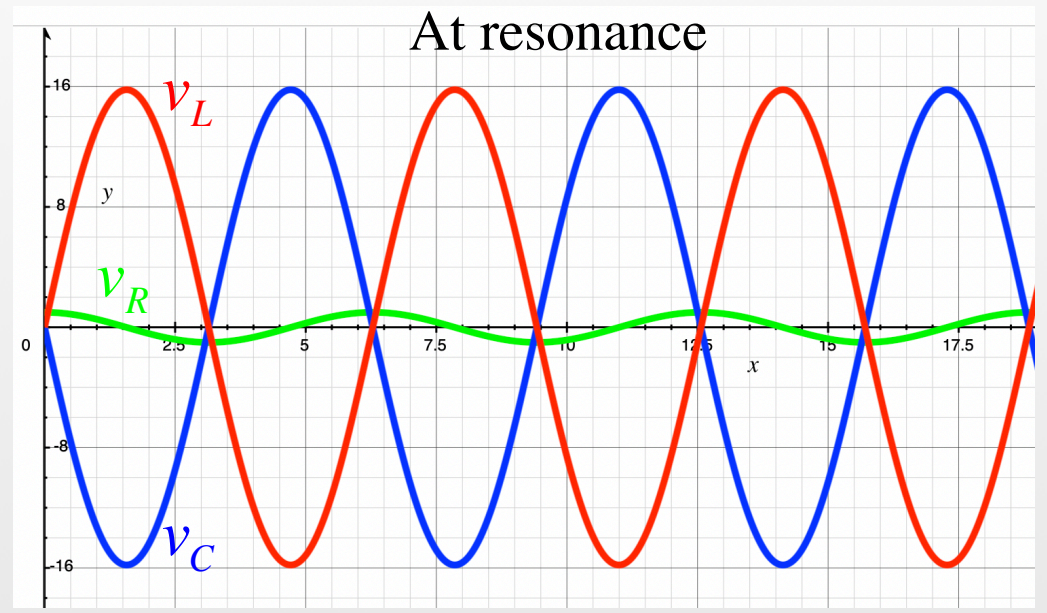

(f) Notch filter (band stop filter)

(g) parallel resonance

8) LC Oscillations

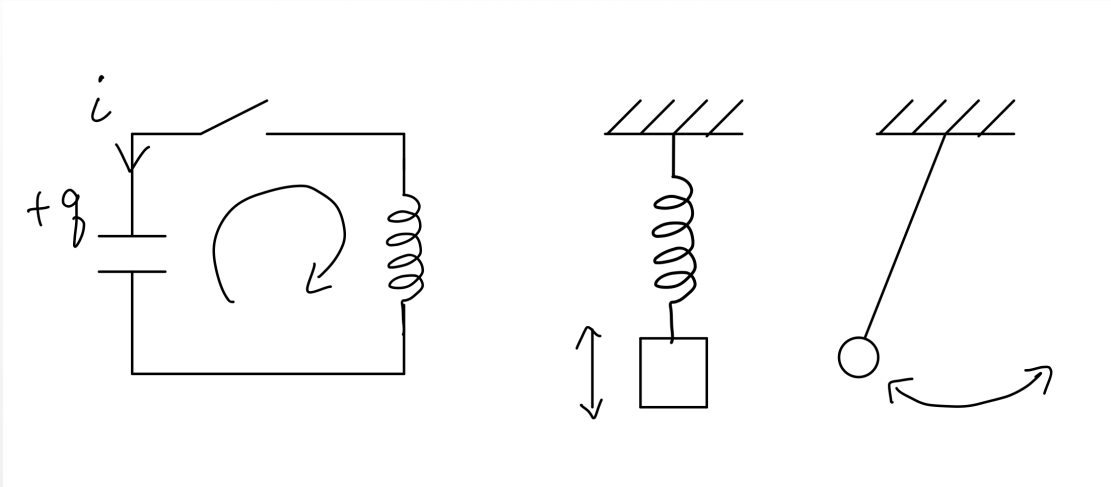

Mass on a spring:

$$F = -kx = m\ddot{x} \quad \Rightarrow \quad \ddot{x} + \frac{k}{m}x = 0$$

Solution: $x = X \cos(\omega t + \varphi)$


where $\omega = \sqrt{k/m}$


Total energy: $U = \frac{1}{2}mv^2 + \frac{1}{2}kx^2$

If there is no energy dissipation, $\frac{dU}{dt} = 0$

$$\Rightarrow \quad m\cancel{v} \frac{dv}{dt} + kx \frac{dx}{dt} = 0$$
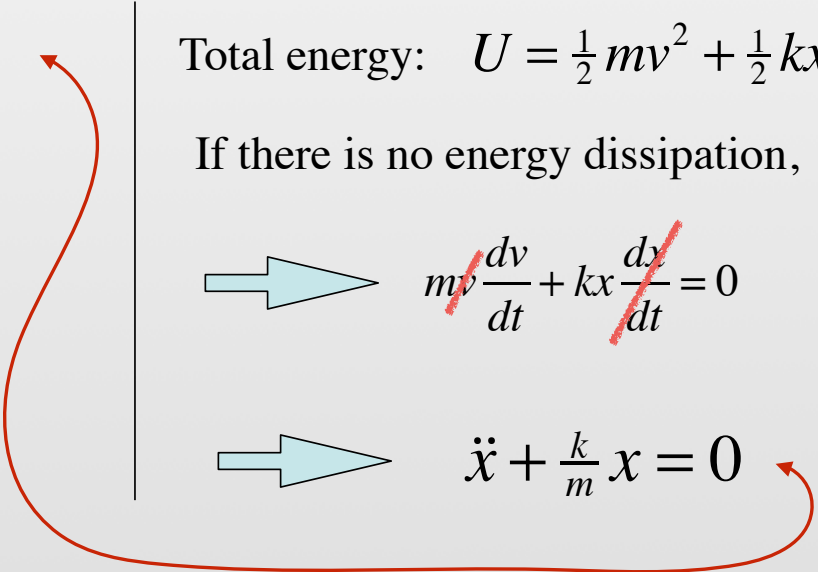
$$\Rightarrow \quad \ddot{x} + \frac{k}{m}x = 0$$



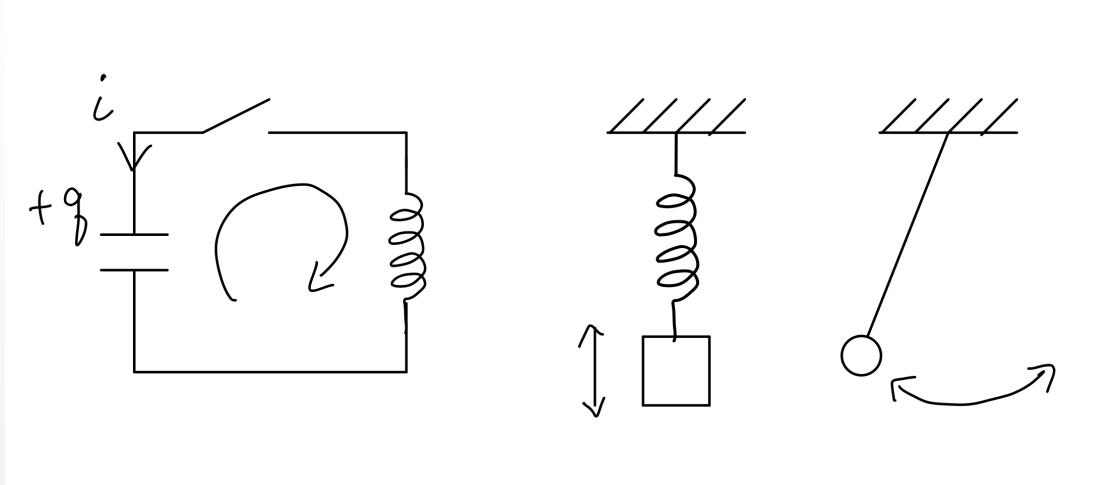

LC oscillator:

$$\frac{q}{C} + L \frac{di}{dt} = 0 \quad \longrightarrow \quad \ddot{q} + \frac{1}{LC} q = 0$$

Solution: $q = Q \cos(\omega t + \varphi)$

where $\omega = \frac{1}{\sqrt{LC}}$


$$\frac{1}{2} C v^2 = \frac{1}{2} C \left(\frac{q}{C} \right)^2 = \frac{1}{2} \frac{q^2}{C}$$


Total energy: $U = \frac{1}{2} L i^2 + \frac{1}{2} \frac{q^2}{C}$

If there is no energy dissipation, $\frac{dU}{dt} = 0$

$$\longrightarrow \quad L \cancel{\frac{di}{dt}} + \frac{q}{C} \cancel{\frac{dq}{dt}} = 0$$
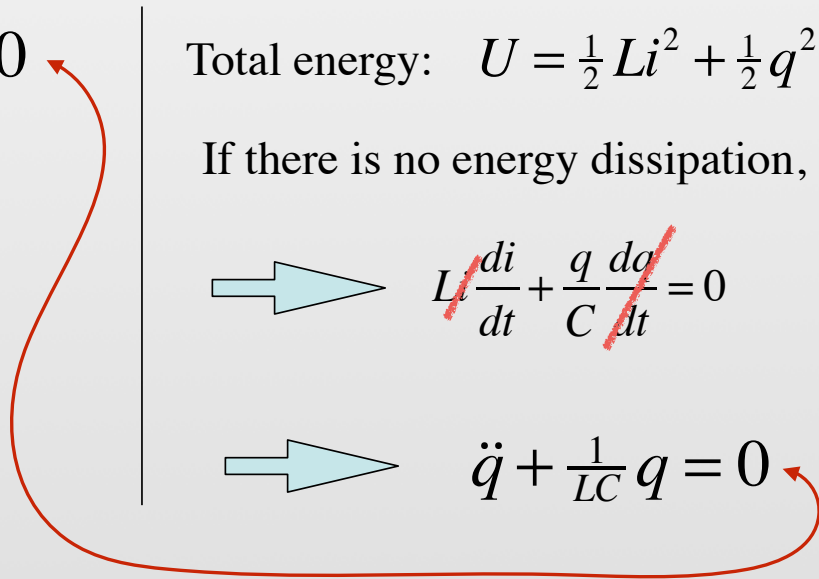
$$\longrightarrow \quad \ddot{q} + \frac{1}{LC} q = 0$$



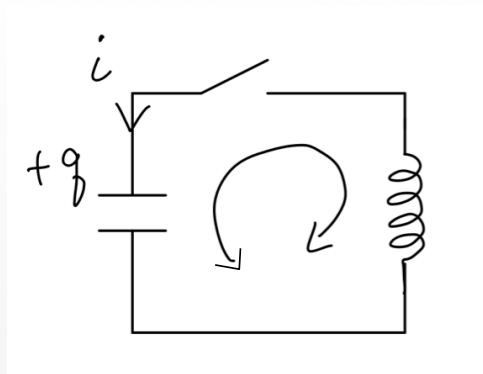


$$q = Q \cos(\omega t + \varphi)$$

$$\omega = \frac{1}{\sqrt{LC}}$$


$$\rightarrow i = \frac{dq}{dt} = -Q\omega \sin(\omega t + \varphi)$$

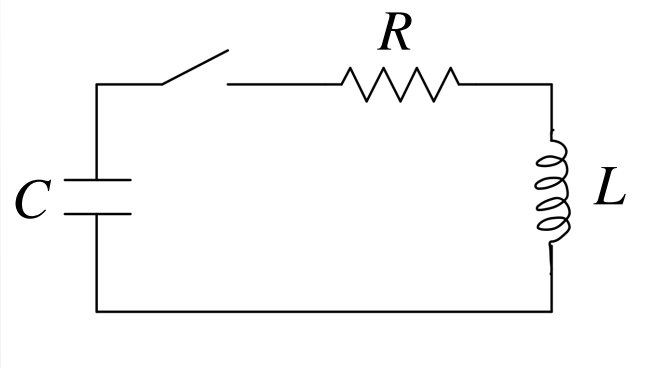9) Transient response of LRC circuit (damped harmonic oscillator)




$$\text{K.L.} \quad \frac{q}{C} + L \frac{di}{dt} + iR = 0$$
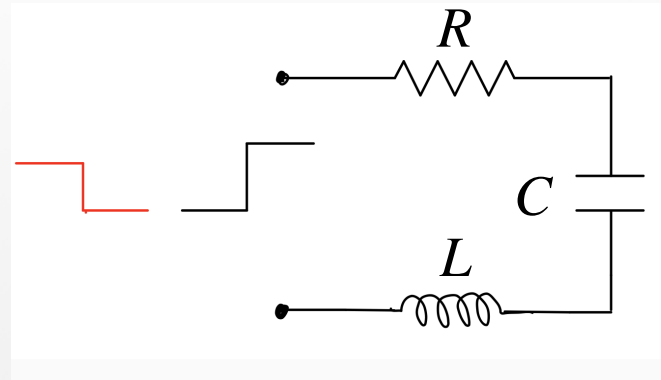
$$\ddot{q} + \frac{R}{L} \dot{q} + \frac{q}{LC} = 0$$



$$\text{Define } \gamma = \frac{R}{L} \quad \text{and use } \omega_0 = \frac{1}{\sqrt{LC}}$$
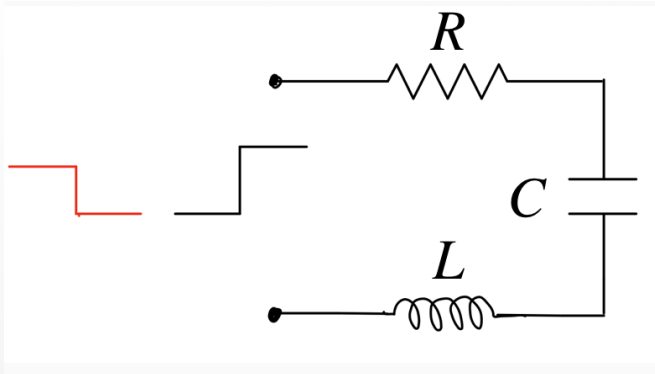
$$\ddot{q} + \gamma \dot{q} + \omega_0^2 q = 0$$



$$\ddot{q} + \gamma \dot{q} + \omega_0^2 q = 0$$

Solution: $q = Qe^{\lambda t}$

Then $\dot{q} = Q\lambda e^{\lambda t} = \lambda q$

and $\ddot{q} = \lambda^2 q$

so $\lambda^2 q + \lambda \gamma q + \omega_0^2 q = 0$

$$\lambda^2 + \lambda \gamma + \omega_0^2 = 0 \quad \Rightarrow \quad \lambda = -\frac{\gamma}{2} \pm \sqrt{\left(\frac{\gamma}{2}\right)^2 - \omega_0^2}$$

$$q = Qe^{\lambda t}$$

$$\lambda = -\frac{\gamma}{2} \pm \sqrt{\left(\frac{\gamma}{2}\right)^2 - \omega_0^2}$$

Define attenuation: $\alpha = \frac{\gamma}{2} = \frac{R}{2L}$ (also called neper frequency)

Define damping factor: $\zeta = \frac{\alpha}{\omega_0} = \frac{R}{2} \sqrt{\frac{C}{L}}$ $\left(= \frac{1}{2Q} \right)$

$$\lambda = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

represents 2 particular solutions

$$q = Qe^{\lambda t}$$

$$\lambda = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Case 1: Underdamped $\alpha < \omega_0$, $\zeta < 1$

$$\lambda = -\alpha \pm j\omega_1 \quad \omega_1 = \sqrt{\omega_0^2 - \alpha^2} \quad (= \omega_0 \sqrt{1 - \zeta^2})$$


General solution: $q = e^{-\alpha t} (Q_1 e^{j\omega_1 t} + Q_2 e^{-j\omega_1 t})$

or $q = e^{-\alpha t} (A_1 \cos \omega_1 t + A_2 \sin \omega_1 t)$


or $q = Q_3 e^{-\alpha t} \sin(\omega_1 t + \varphi)$


exponential
decay

oscillation

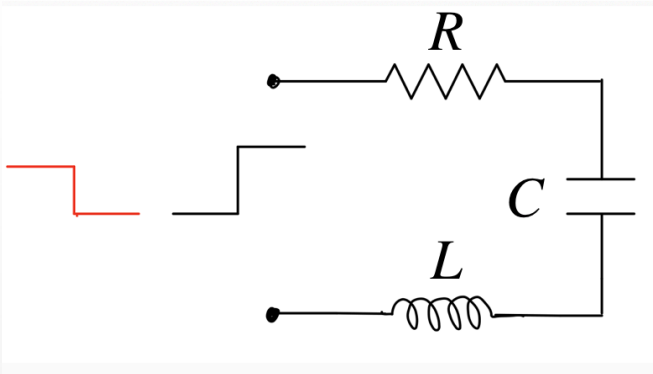
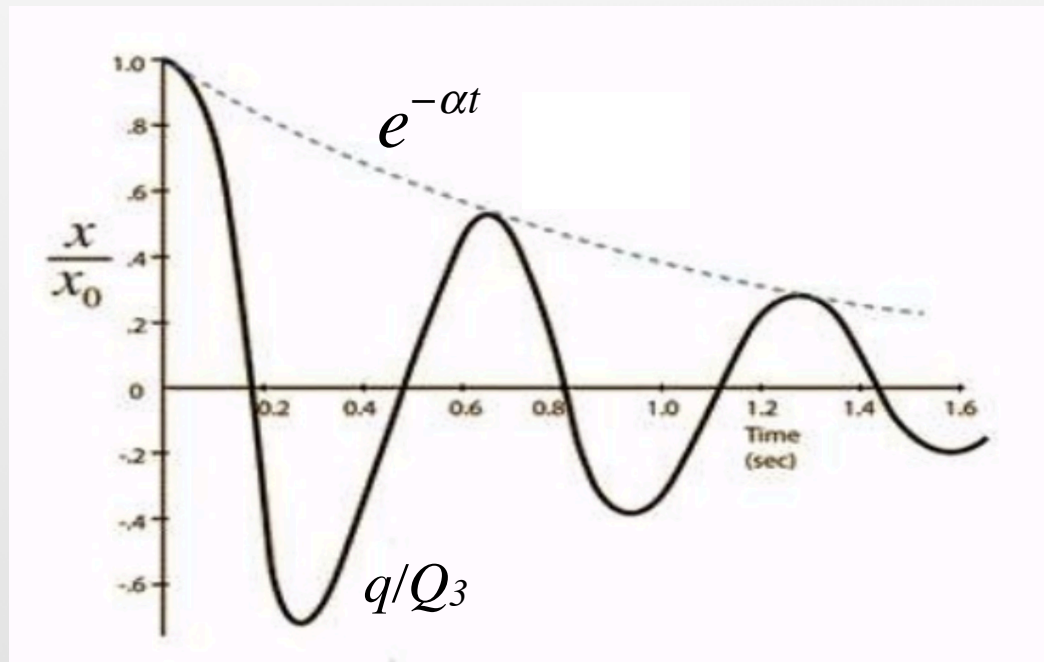
$$q = Q_3 e^{-\alpha t} \sin(\omega_1 t + \varphi)$$



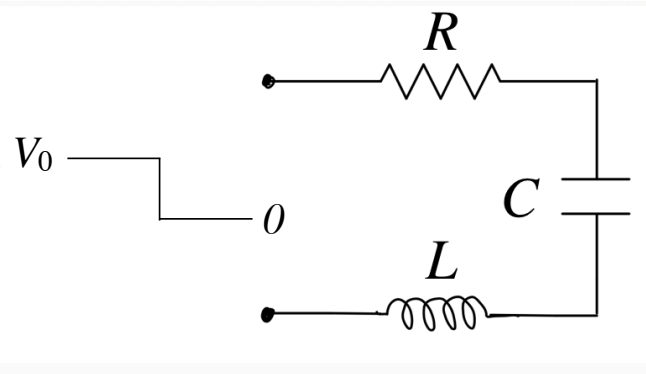

$$q = Q_3 e^{-\alpha t} \sin(\omega_1 t + \varphi)$$

$$\omega_1 = \sqrt{\omega_0^2 - \alpha^2}$$

$$\alpha = \frac{R}{2L}$$

$$i = \frac{dq}{dt} = Q_3 \left(-\alpha e^{-\alpha t} \sin(\omega_1 t + \varphi) + e^{-\alpha t} \omega_1 \cos(\omega_1 t + \varphi) \right)$$


Boundary conditions give Q_3 and φ

$$t = 0 \rightarrow q = CV_0 \quad \text{and} \quad i = 0$$

Then $CV_0 = Q_3 \sin \varphi$


and $0 = -\alpha \sin \varphi + \omega_1 \cos \varphi \rightarrow$
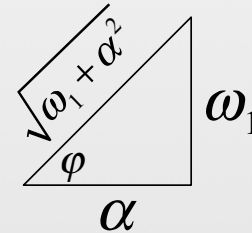
$$\tan \varphi = \frac{\omega_1}{\alpha}$$



$$\Rightarrow Q_3 = \frac{CV_0}{\sin \varphi} = CV_0 \frac{\sqrt{\omega_1^2 + \alpha^2}}{\omega_1}$$
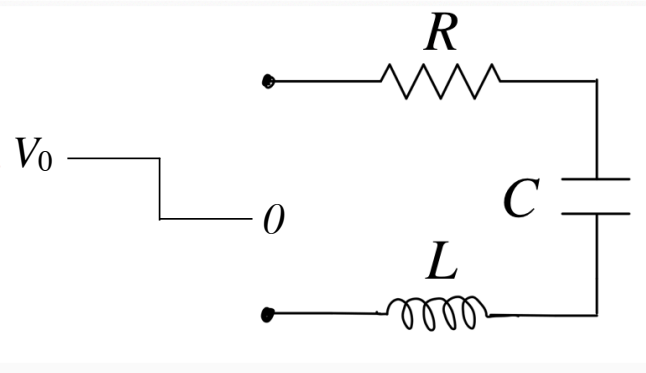
$$Q_3 = CV_0 \sqrt{1 + (\alpha / \omega_1)^2}$$



$$q = Q_3 e^{-\alpha t} \sin(\omega_1 t + \varphi)$$

$$\omega_1 = \sqrt{\omega_0^2 - \alpha^2}$$

$$\alpha = \frac{R}{2L}$$

$$Q_3 = CV_0 \sqrt{1 + (\alpha / \omega_1)^2}$$

$$\tan \varphi = \frac{\omega_1}{\alpha}$$


For $\alpha \ll \omega_0$ ($\zeta \ll 1$), $\omega_1 = \sqrt{\omega_0^2 - \alpha^2} \rightarrow \omega_0$

$\tan \varphi \rightarrow \infty$, $\varphi \rightarrow \pi / 2$

$$q \cong CV_0 e^{-\alpha t} \cos \omega_0 t$$

or
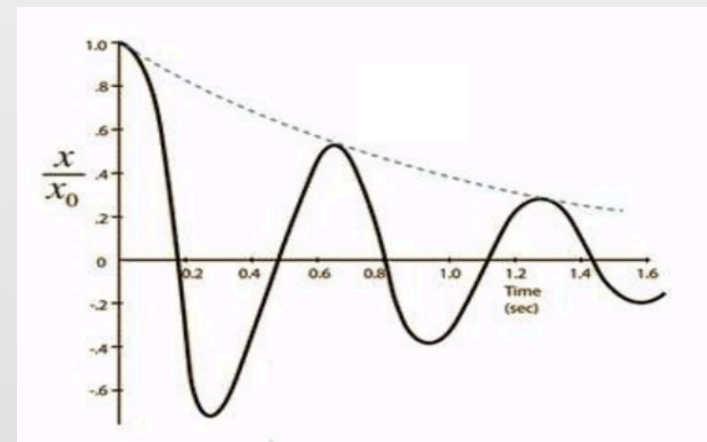
$$v_C \cong V_0 e^{-\alpha t} \cos \omega_0 t$$



$$q = Qe^{\lambda t}$$

$$\lambda = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Case 2: Overdamped

$$\alpha > \omega_0, \quad \zeta > 1 \quad \Rightarrow \quad \begin{aligned} \lambda &= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \\ \lambda &= -\alpha \pm \beta \end{aligned}$$

General solution: $q = Q_1 e^{-(\alpha+\beta)t} + Q_2 e^{-(\alpha-\beta)t}$ Both terms are negative exponential \Rightarrow decaying exponential

Boundary conditions: $t = 0 \rightarrow q = CV_0$ and $i = 0$ gives 2 equations for Q_1 and Q_2

$$q = \frac{CV_0}{2} e^{-\alpha t} \left[\left(1 - \frac{\alpha}{\beta}\right) e^{-\beta t} + \left(1 + \frac{\alpha}{\beta}\right) e^{\beta t} \right]$$

For $\alpha \gg \omega_0$, $\beta \rightarrow \alpha$

$$q = CV_0 e^{-(\alpha-\beta)t}$$

or

$$v_C = V_0 e^{-(\alpha-\beta)t}$$

$$q = Qe^{\lambda t}$$

$$\lambda = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Case 3: Critical damping $\alpha = \omega_0$, $\zeta = 1 \Rightarrow \lambda = -\alpha$ represents only one solution

General solution then includes a linear term (see e.g. Boas for justification):

$$q = (A + Bt)e^{-\alpha t} \Rightarrow i = Be^{-\alpha t} - (A + Bt)\alpha e^{-\alpha t}$$

Boundary conditions: $t = 0 \rightarrow q = CV_0$ and $i = 0$

$$\begin{aligned} CV_0 &= A \\ 0 &= B - \alpha A \rightarrow B = \alpha CV_0 \end{aligned}$$

$$q = CV_0(1 + \alpha t)e^{-\alpha t}$$

or

$$v_C = V_0(1 + \alpha t)e^{-\alpha t}$$

represents the fastest decay
without oscillation

$$\alpha < \omega_0, \quad \zeta < 1$$

$$q = Q_3 e^{-\alpha t} \sin(\omega_1 t + \varphi)$$

underdamped

$$\alpha = \omega_0, \quad \zeta = 1$$


$$q = CV_0 (1 + \alpha t) e^{-\alpha t}$$

critically damped

$$\alpha > \omega_0, \quad \zeta > 1$$

$$q = CV_0 e^{-(\alpha - \beta)t}$$

overdamped

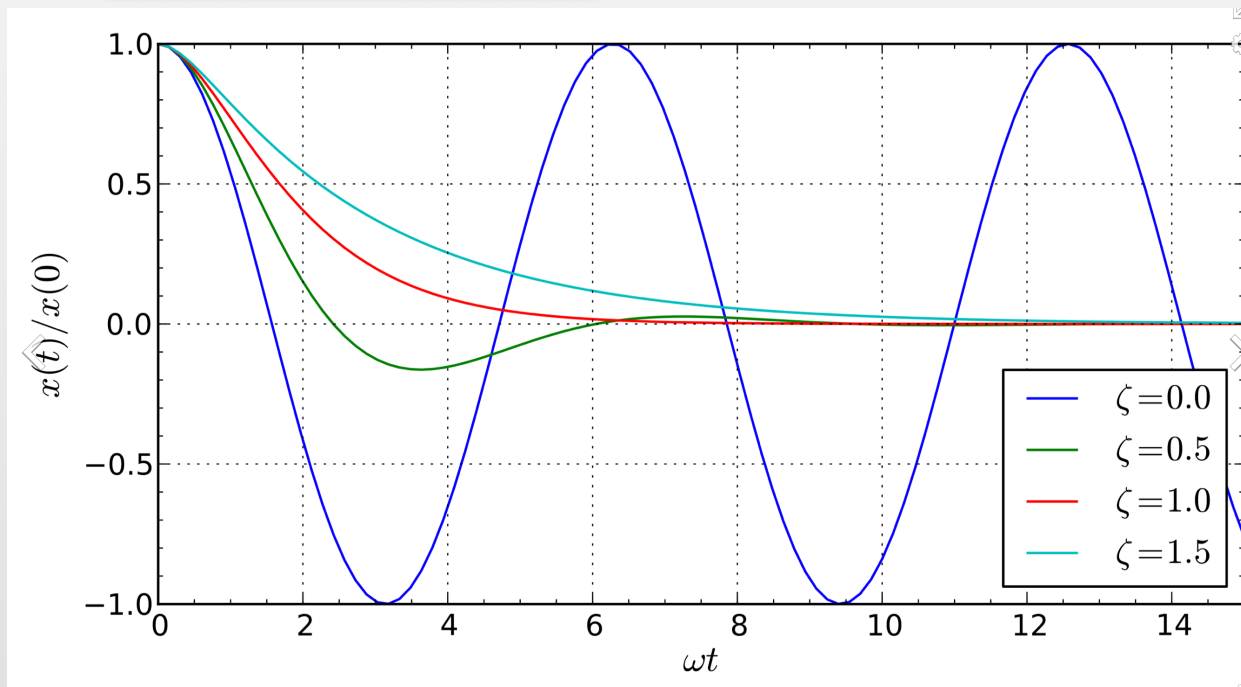

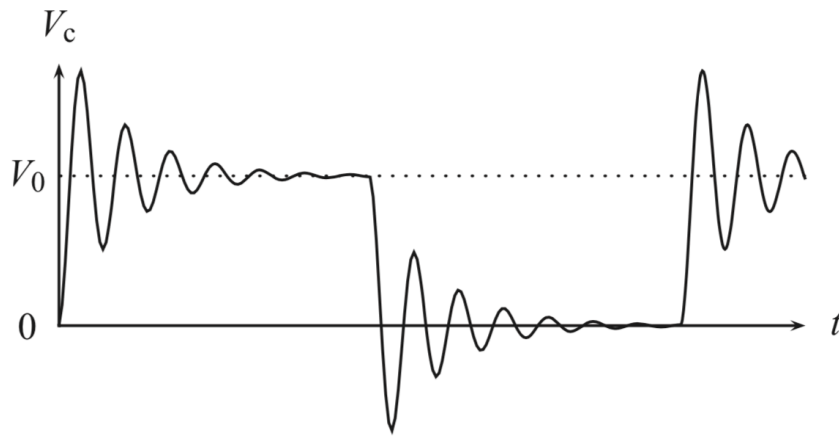


Figure 2.25 Underdamped response of a switched LRC circuit.

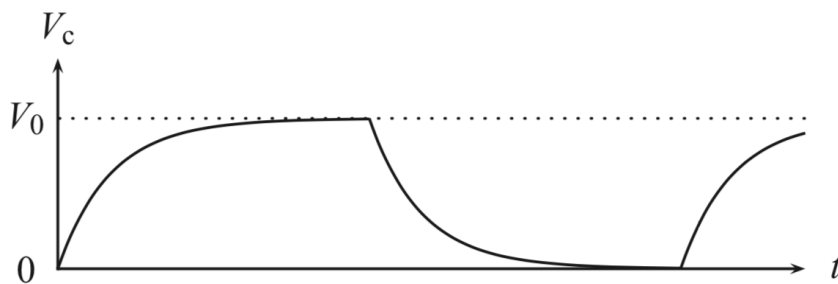


Figure 2.26 Overdamped response of a switched LRC circuit.

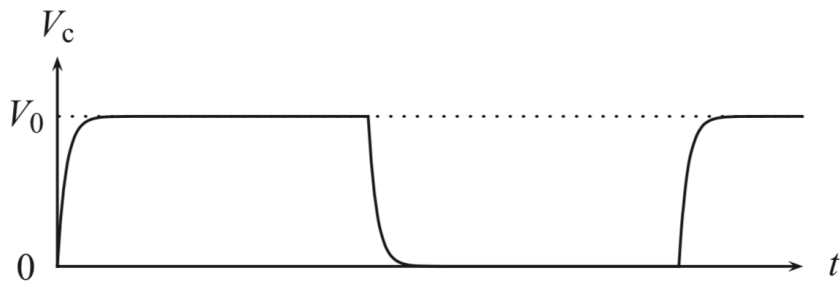


Figure 2.27 Critically damped response of a switched LRC circuit.