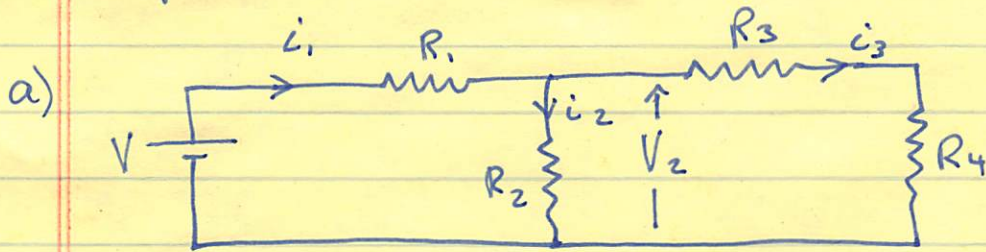


Phys 2610 (2017) Pre-lab exercise 1 solution



$$R_{\text{eff}} = R_1 + R_{\parallel} = R_1 + R_2 \parallel (R_3 + R_4) = R_1 + \frac{R_2(R_3 + R_4)}{R_2 + R_3 + R_4}$$

5

$$\left(\text{where } R_{\parallel} = \left(\frac{1}{R_2} + \frac{1}{R_7} \right)^{-1}, \text{ and } R_7 = R_3 + R_4 \right)$$

Using nominal values $R_1 = 1 \text{ k}\Omega$, $R_2 = 3.3 \text{ k}\Omega$,
 $R_3 = 2.2 \text{ k}\Omega$, and $R_4 = 10 \text{ k}\Omega$,

$$R_7 = 12.200 \text{ k}\Omega, \quad R_{\parallel} = 2.597 \text{ k}\Omega$$

to give $R_{\text{eff}} = 3.597 \text{ k}\Omega$

b) Using $R_{eff} = R_1 + R_{11}$, $\delta R_{eff}^2 = \delta R_1^2 + \delta R_{11}^2$

Now, $\frac{1}{R_{11}} = \frac{1}{R_2} + \frac{1}{R_7}$ ($R_{11} = \frac{R_2 R_7}{R_2 + R_7} = \frac{R_2 (R_3 + R_4)}{R_2 + R_3 + R_4}$)

To use the simple rule, the terms must be independent, so

$$\delta(1/R_{11})^2 = \delta(1/R_2)^2 + \delta(1/R_7)^2$$

but $\frac{\delta(1/x)}{(1/x)} = \frac{\delta x}{x}$ since relative errors add (in quadrature) for division

5

so $\delta x = x^2 \delta(1/x)$ and $\delta(1/x) = \frac{\delta x}{x^2}$, giving

$$\delta R_{11}^2 = R_{11}^4 \delta(1/R_{11})^2 = R_{11}^4 \left(\delta(1/R_2)^2 + \delta(1/R_7)^2 \right)$$

$$= R_{11}^4 \left(\frac{\delta R_2^2}{R_2^4} + \frac{\delta R_7^2}{R_7^4} \right), \text{ and}$$

$$\delta R_{eff}^2 = \delta R_1^2 + R_{11}^4 \left(\frac{\delta R_2^2}{R_2^4} + \frac{\delta R_3^2 + \delta R_4^2}{(R_3 + R_4)^4} \right) \quad (\text{using } R_7 = R_3 + R_4)$$

With the above nominal values, and with 0.25% uncertainty, $\delta R_1 = 0.0025 R_1 = 2.5 \Omega$, $\frac{\delta R_2}{R_2} = 0.0025$, $\delta R_3 = 5.5 \Omega$, $\delta R_4 = 25 \Omega$.

Substituting gives $\delta R_{eff} = 5.8 \Omega$ so $R_{eff} = \underline{3.597 \pm 0.006 k \Omega}$, for a

per cent error $\frac{\delta R_{eff}}{R_{eff}} \times 100 = 0.17\%$ //

(3)

Note that the same result for δR_{11} can be obtained using the general formula:

$$R_{11} = \left(\frac{1}{R_2} + \frac{1}{R_7} \right)^{-1}$$

$$\rightarrow \delta R_{11} = \left(\frac{\partial R_{11}}{\partial R_2} \right)^2 \delta R_2^2 + \left(\frac{\partial R_{11}}{\partial R_7} \right)^2 \delta R_7^2$$



$$\text{Here } \frac{\partial R_{11}}{\partial R_2} = (-1) \left(\frac{1}{R_2} + \frac{1}{R_7} \right)^{-2} (-1) R_2^{-2} = \frac{R_{11}^2}{R_2^2},$$

$$\frac{\partial R_{11}}{\partial R_7} = \frac{R_{11}^2}{R_7^2}, \quad \text{so}$$

$$\delta R_{11}^2 = R_{11}^4 \left(\frac{\delta R_2^2}{R_2^4} + \frac{\delta R_7^2}{R_7^4} \right)$$

Note also that combining uncertainties for the numerator & denom. in $R_{11} = R_2 R_7 / (R_2 + R_7)$ tends to exaggerate the uncertainty because the numerator & denominator are not independent.

4

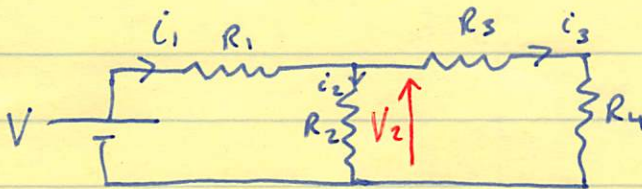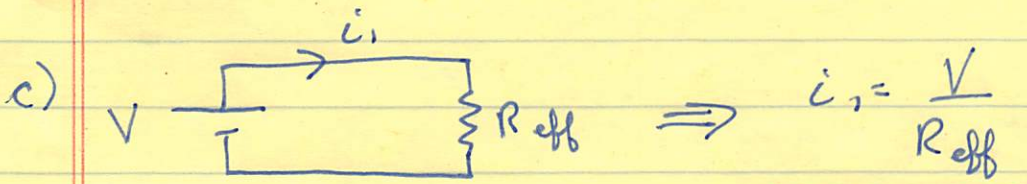

The voltage across R_2 is $V_2 = i_1 R_{11} = \frac{V}{R_{eff}} \left(\frac{R_2(R_3+R_4)}{R_2+R_3+R_4} \right)$

so $i_2 = \frac{V_2}{R_2} = \frac{V}{R_{eff}} \frac{(R_3+R_4)}{(R_2+R_3+R_4)}$

and

$i_3 = \frac{V_2}{R_3+R_4} = \frac{V}{R_{eff}} \left(\frac{R_2}{R_2+R_3+R_4} \right)$